

Chapter 4 Combinational Logic


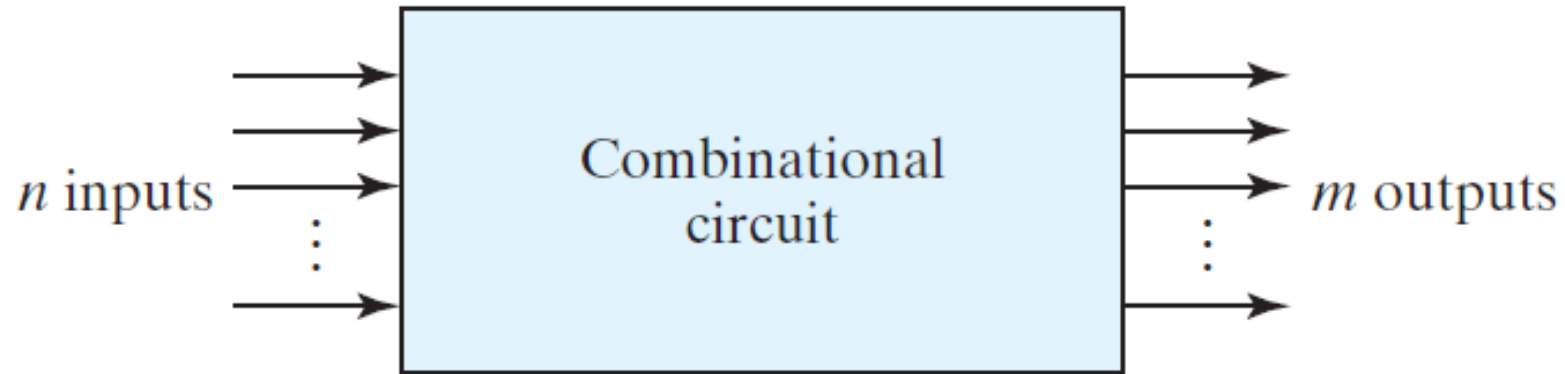


FIGURE 4.1

Block diagram of combinational circuit

Sequential Logic

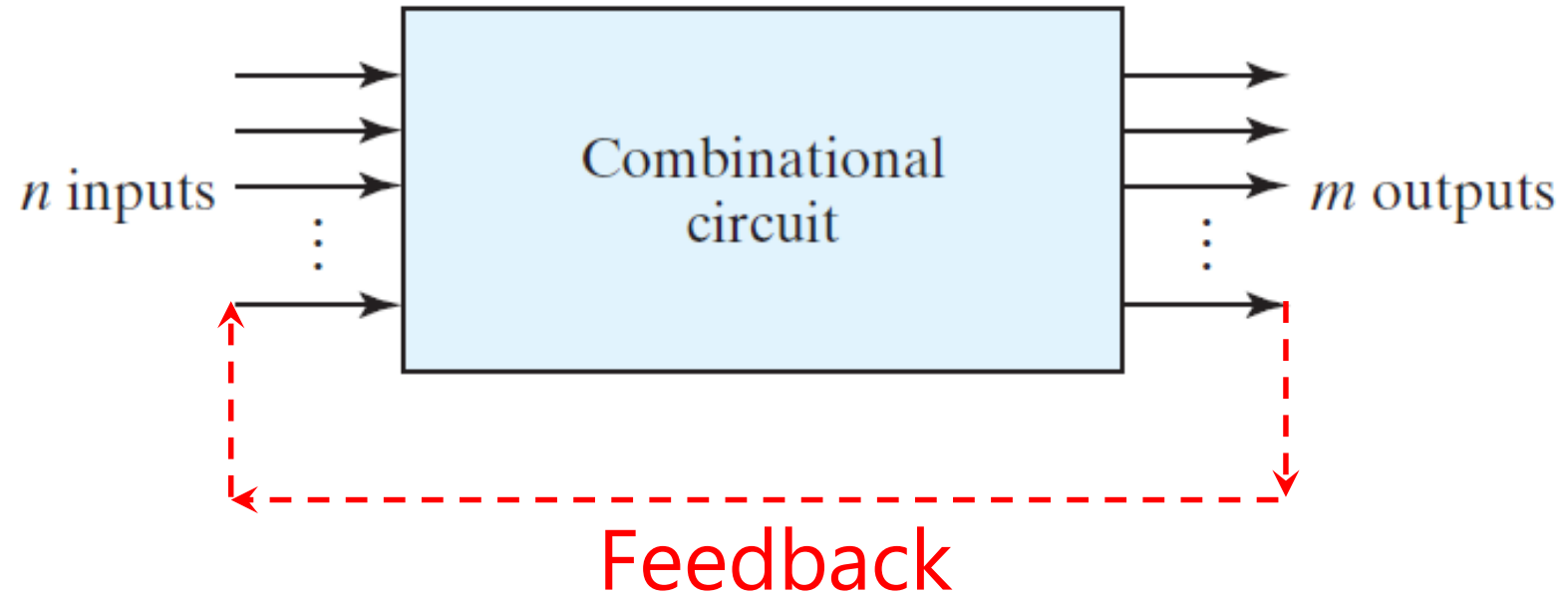



Combinational Logic

aka. Combinational Circuit

Combination of logic gates on the present inputs → the outputs *at any time!*


A combinational circuit performs an operation that can be specified logically by a set of Boolean functions.

Voltage

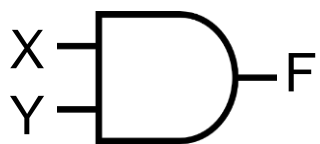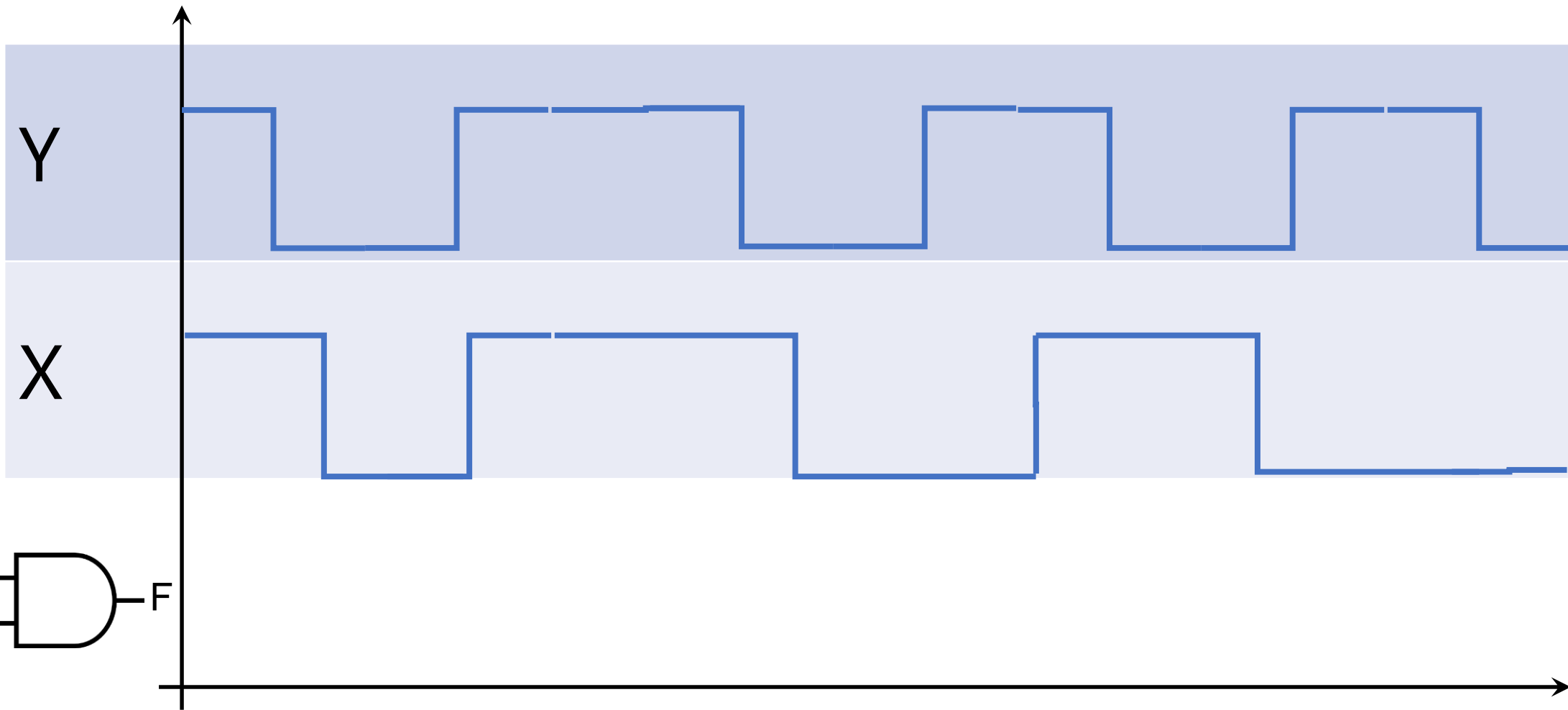

Time


Voltage

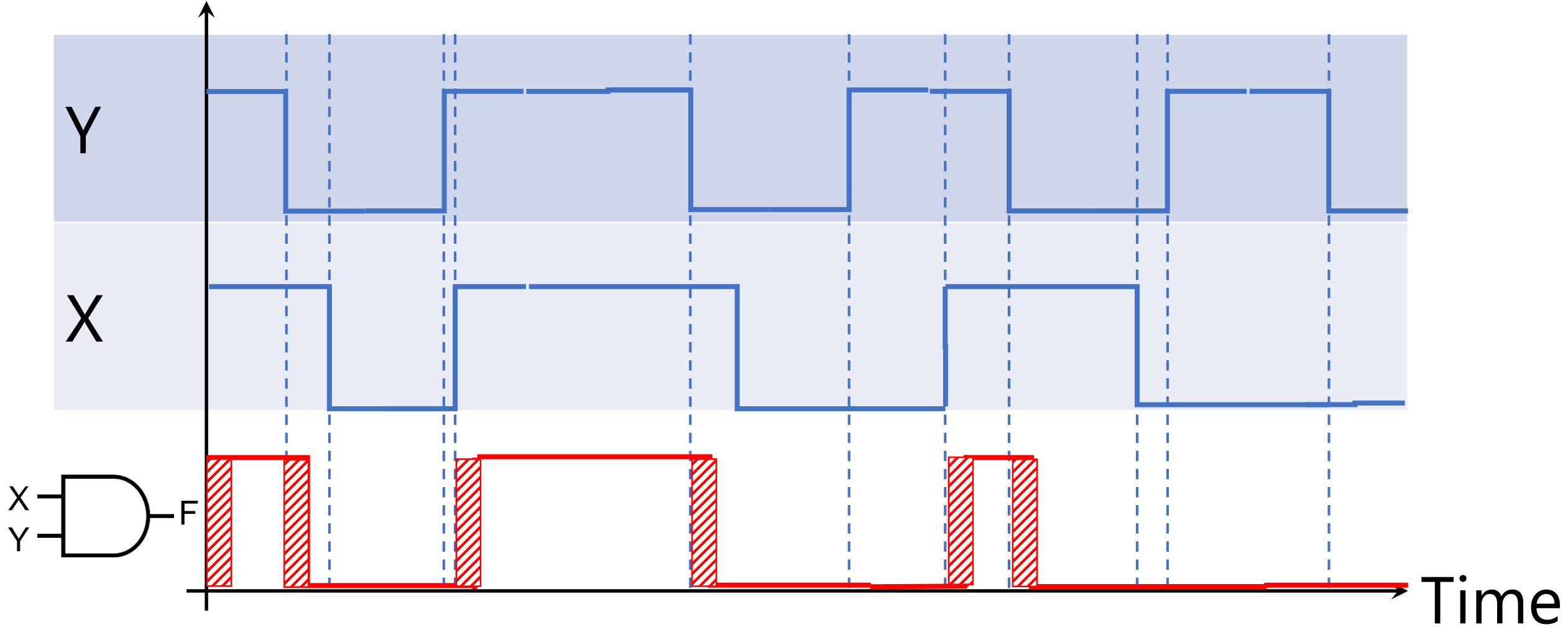

Propagation Delay (Gate Delay) $\approx \Delta t$

https://en.wikipedia.org/wiki/Propagation_delay#Electronics

Voltage

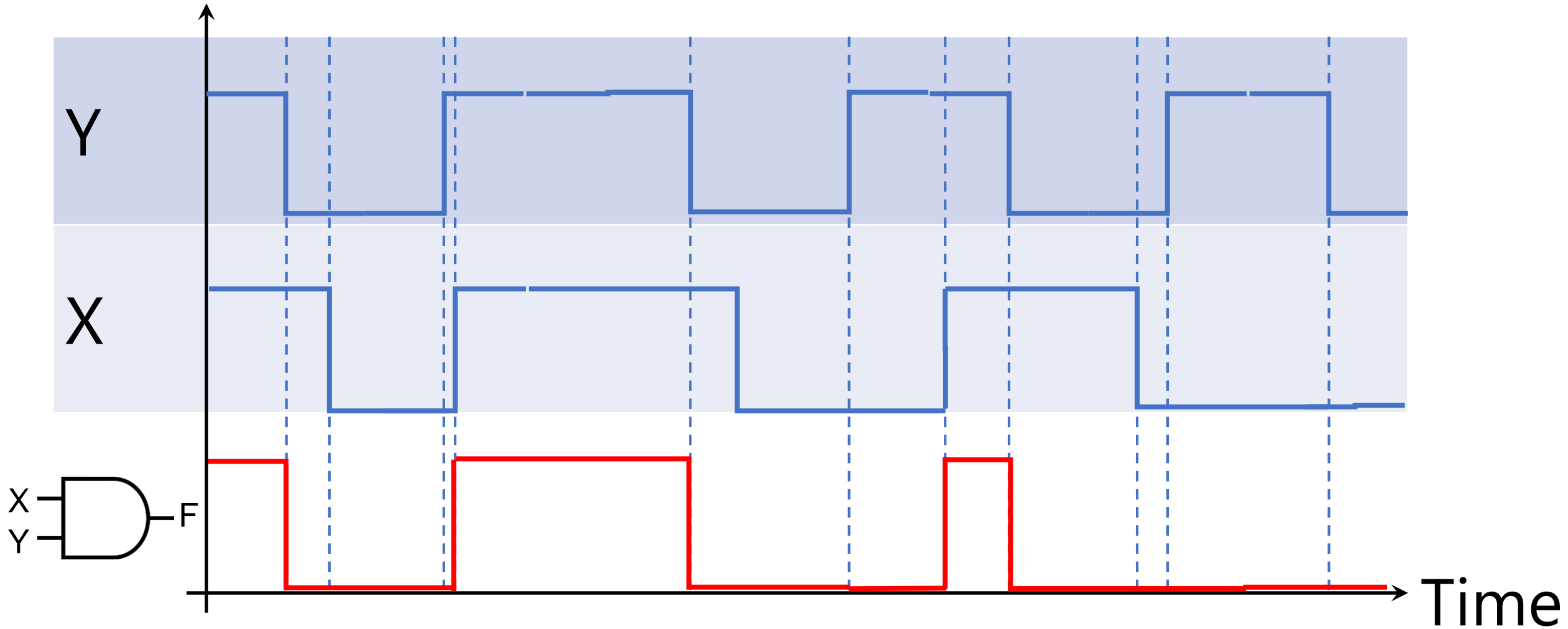

Propagation Delay (Gate Delay) $\approx \Delta t \approx 0$


https://en.wikipedia.org/wiki/Propagation_delay#Electronics


What we've done so far

Combinational Logic aka. Combinational Circuit

Design a combinational logic circuit:

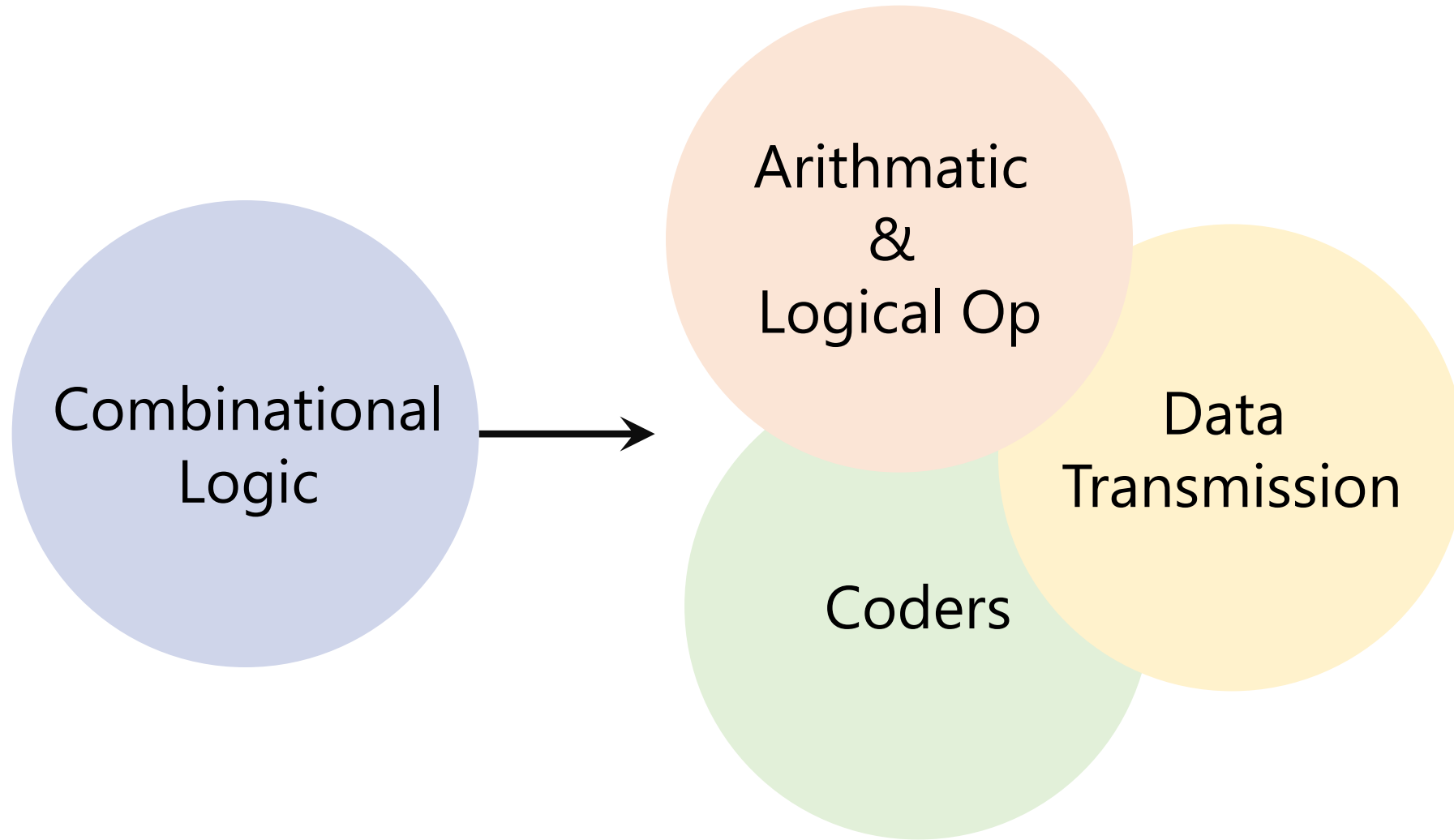1. Truth Table
2. Boolean Function (Algebraic Expression)
3. Minimization
 - Boolean Algebra
 - Karnaugh Map (K-Map)
 - Quine-McCluskey Algorithm
4. Logic Diagram



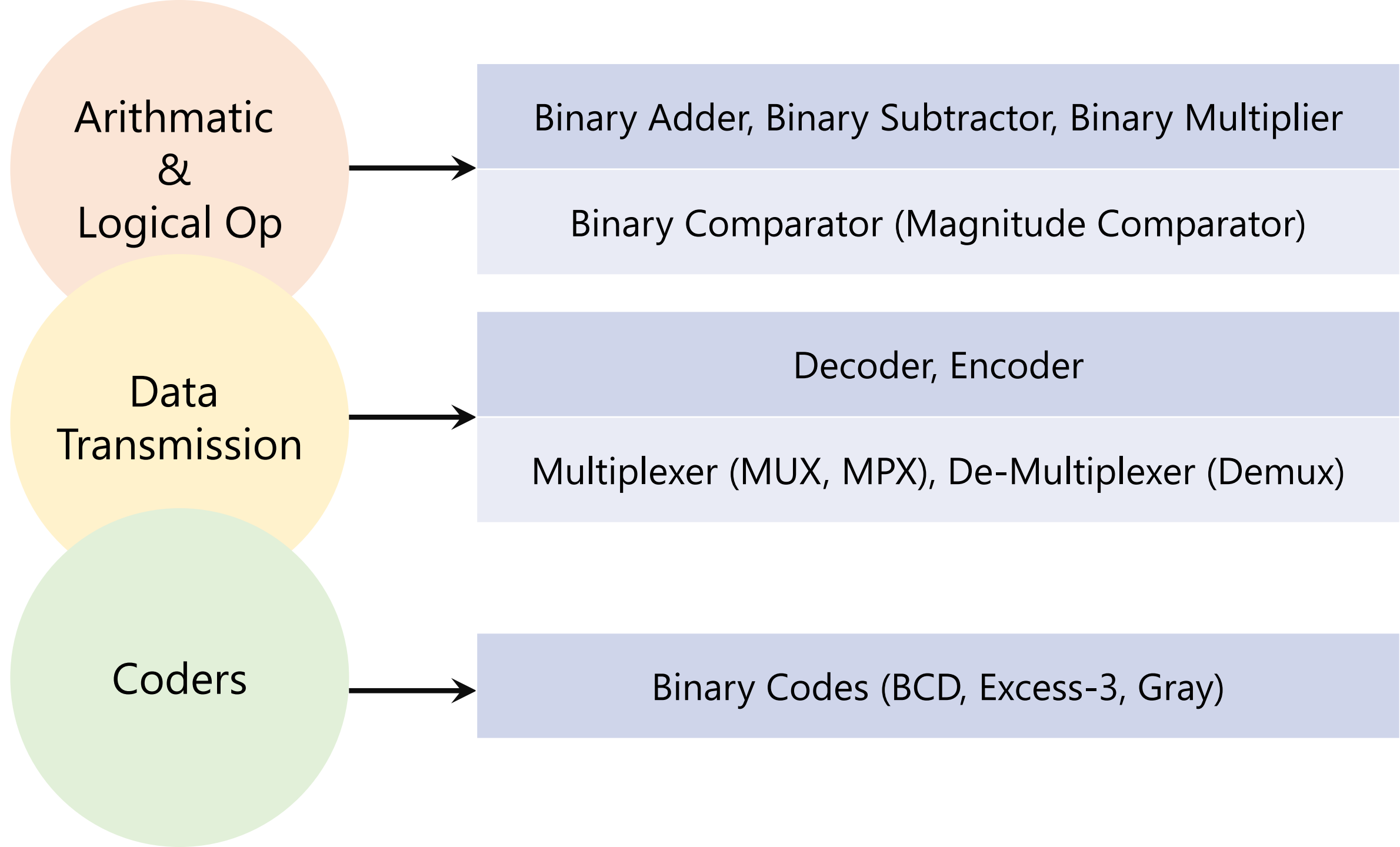

Arithmetic
&
Logical Op

```
graph LR; A((Arithmetic & Logical Op)) --> B[Binary Adder, Binary Subtractor, Binary Multiplier]; A --> C[Binary Comparator (Magnitude Comparator)];
```

The diagram consists of an orange circle on the left containing the text 'Arithmetic & Logical Op'. A black arrow points from the right side of this circle to a light blue rectangular box on the right. This box is divided into two horizontal sections. The top section contains the text 'Binary Adder, Binary Subtractor, Binary Multiplier' in bold, and the bottom section contains the text 'Binary Comparator (Magnitude Comparator)'.

Binary Adder, Binary Subtractor, Binary Multiplier

Binary Comparator (Magnitude Comparator)

Binary Adder

Design a logic circuit that
adds two binary digits (bit).

Range of inputs:
2 bits

Input binary variables:
X and Y

Range of outputs?

	0	0	1	1
+	0	1	0	1
	0	1	1	C=1 0


	0	0	1	1
+	0	1	0	1
	<div>C=0</div> 0	<div>C=0</div> 1	<div>C=0</div> 1	<div>C=1</div> 0

$$\begin{array}{r} X \\ Y \\ + \\ \hline C \quad S \end{array}$$


Range of outputs?
2 bits

Output binary variables:
Carry and Sum

Y	X	$F_2 = C(Y, X) = YX$	$F_1 = S(Y, X) = Y'X + YX'$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

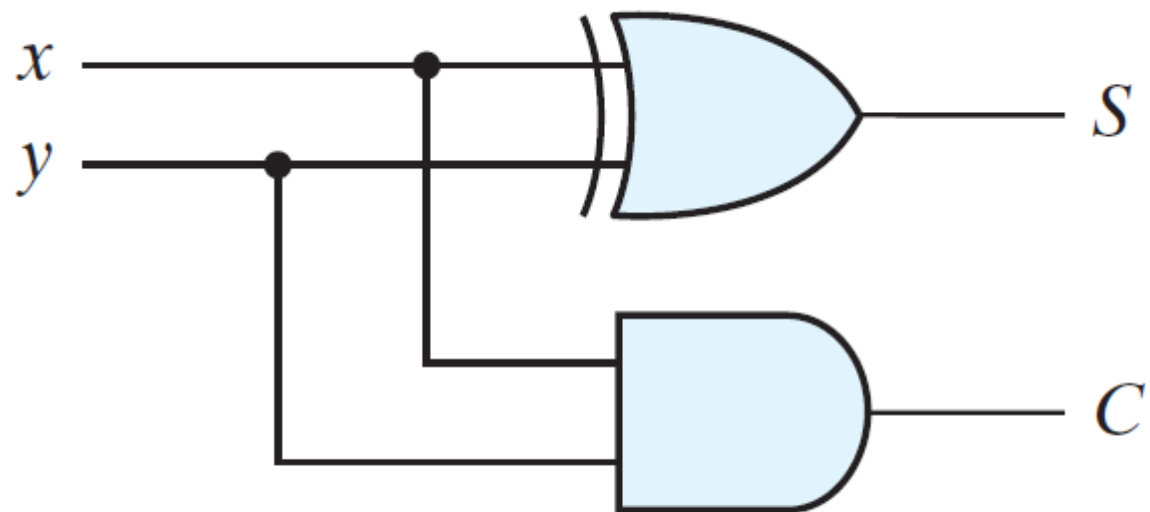



$$S = x \oplus y$$
$$C = xy$$

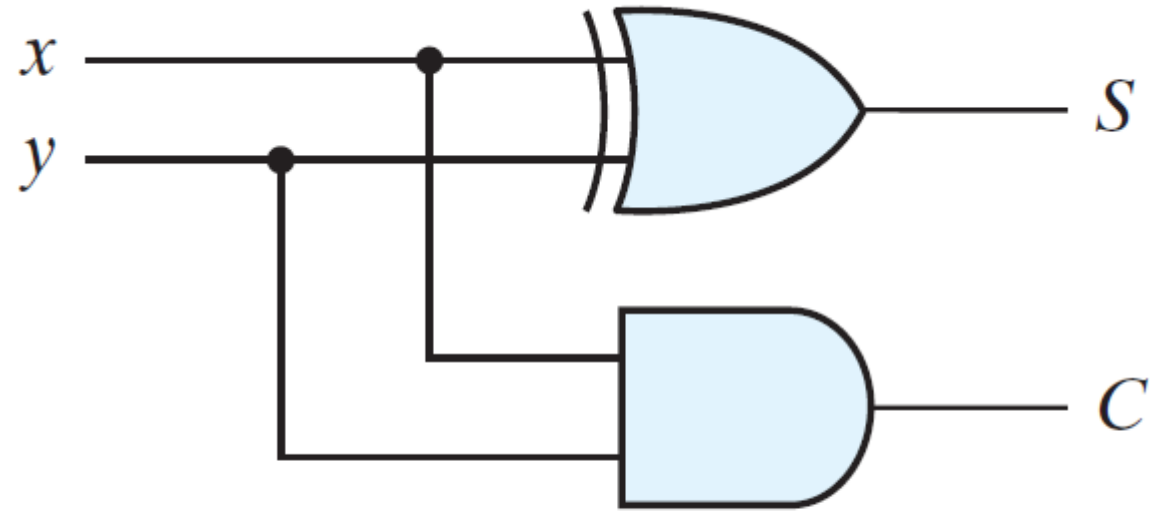

$$S = x \oplus y$$
$$C = xy$$

Half Adder: Just 2 bits: $X+Y$

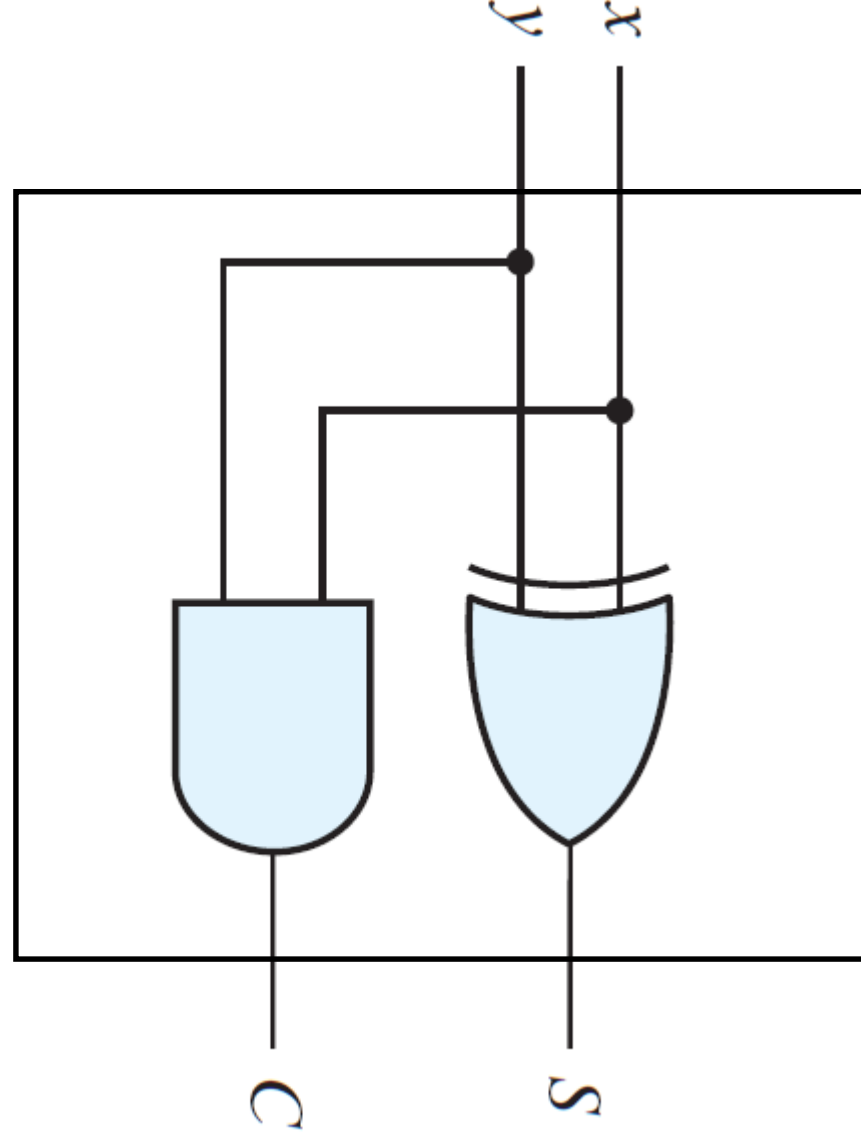

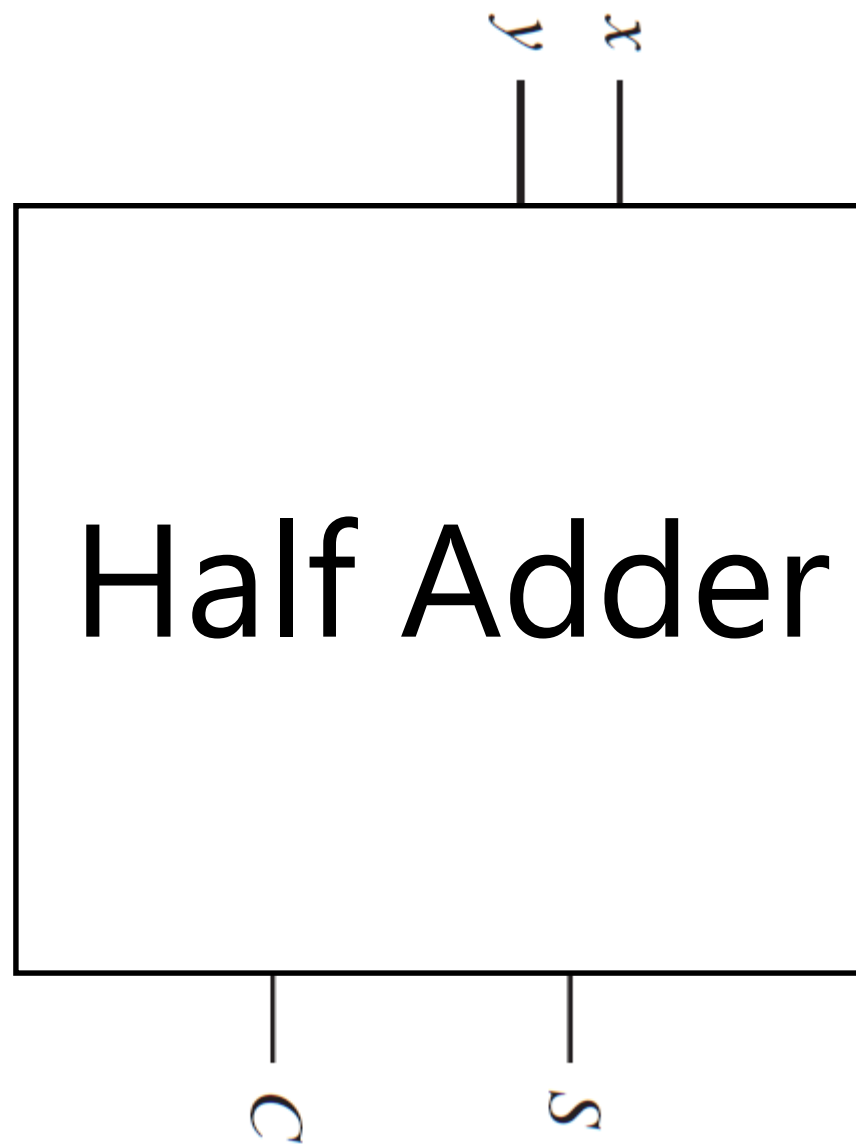

Design a logic circuit that
adds two binary **numbers**!

Range of inputs:
2 binary numbers in range
 $[00, 11]_2$

Input binary variables:

$$X = X_2X_1 \text{ and } Y = Y_2Y_1$$

Range of outputs?

	00	00	00	...	11
+	00	01	10	...	11
	<div>C=0</div> 00	<div>C=0</div> 01	<div>C=0</div> 10		<div>C=1</div> 10

$$\begin{array}{r}
 X_2 X_1 \\
 + \quad Y_2 Y_1 \\
 \hline
 \text{C} \quad S_2 S_1
 \end{array}$$

Range of outputs?
Carry, S_2 , S_1

Y ₂	Y ₁	X ₂	X ₁	F ₁ =C(Y ₁ ,Y ₂ ,X ₂ ,X ₁)	F ₂ =S ₁ (Y ₁ ,Y ₂ ,X ₂ ,X ₁)	F ₃ =S ₂ (Y ₁ ,Y ₂ ,X ₂ ,X ₁)
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0



Y_2	Y_1	X_2	X_1	$F_1 = C(Y_1, Y_2, X_2, X_1)$	$F_2 = S_1(Y_1, Y_2, X_2, X_1)$	$F_3 = S_2(Y_1, Y_2, X_2, X_1)$
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	0
0	0	1	1	0	0	1
0	1	0	0	0	0	1
0	1	0	1	0	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	0
1	0	0	0	0	1	1
1	0	0	1	0	1	0
1	0	1	0	1	1	0
1	0	1	1	1	1	1
1	1	0	0	0	0	1
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	0



Wait a sec!



Can we re-use the half adder?

Half adder for adding 2 bits.
How about having 2 half adders for adding 2 × 2 bits?
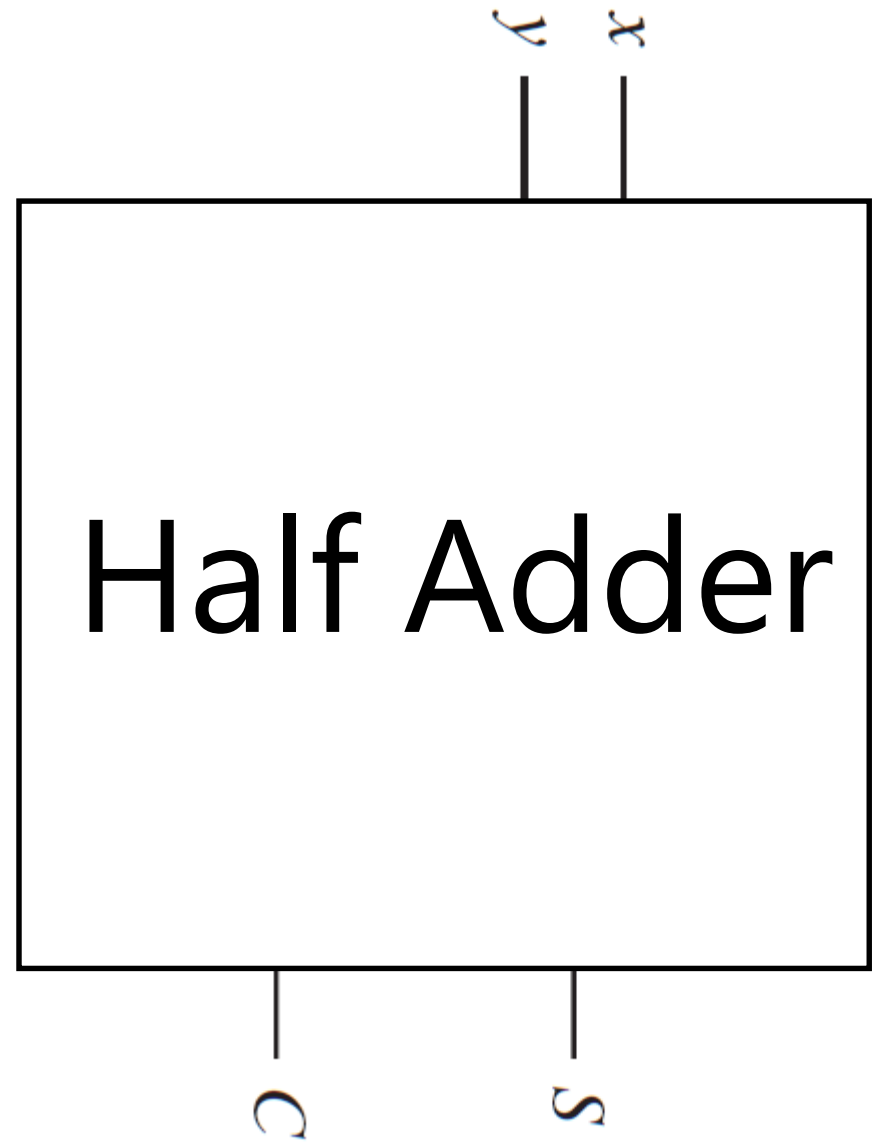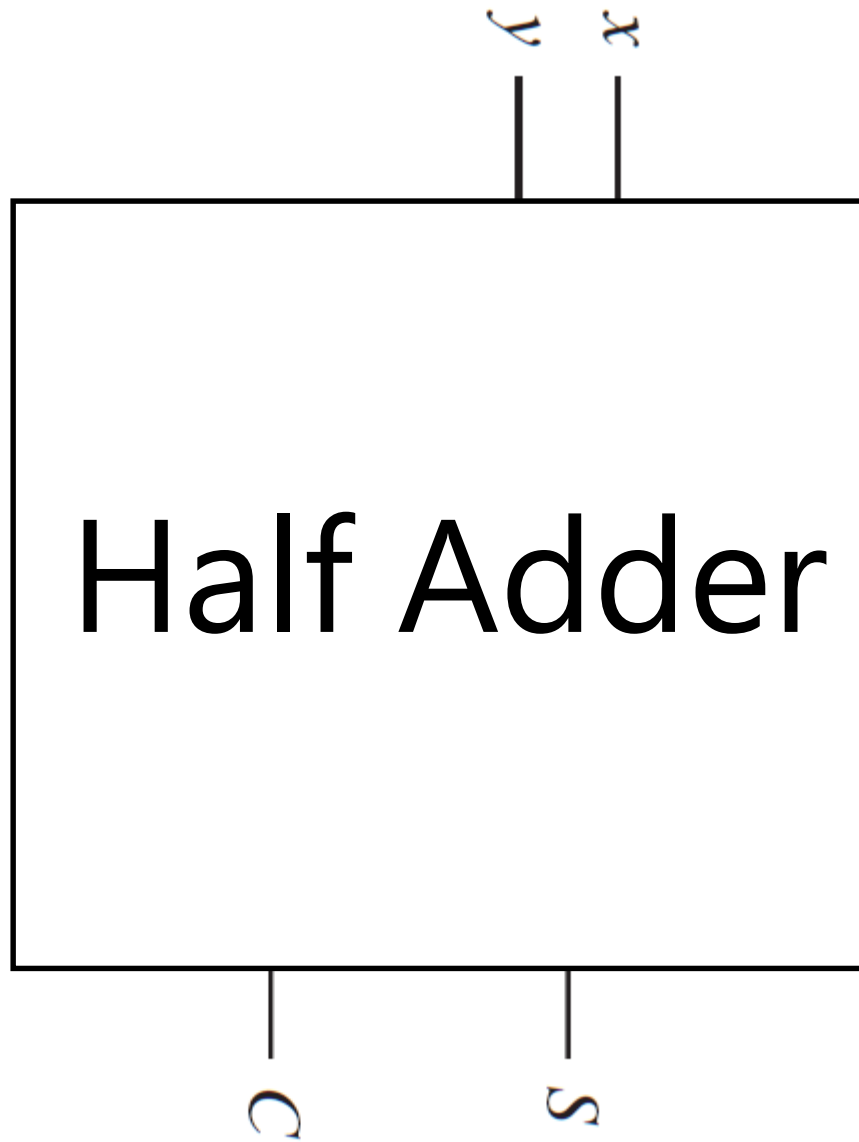
$$\begin{array}{r}
 X_2 X_1 \\
 + \quad Y_2 Y_1 \\
 \hline
 \text{C} \quad S_2 S_1
 \end{array}$$



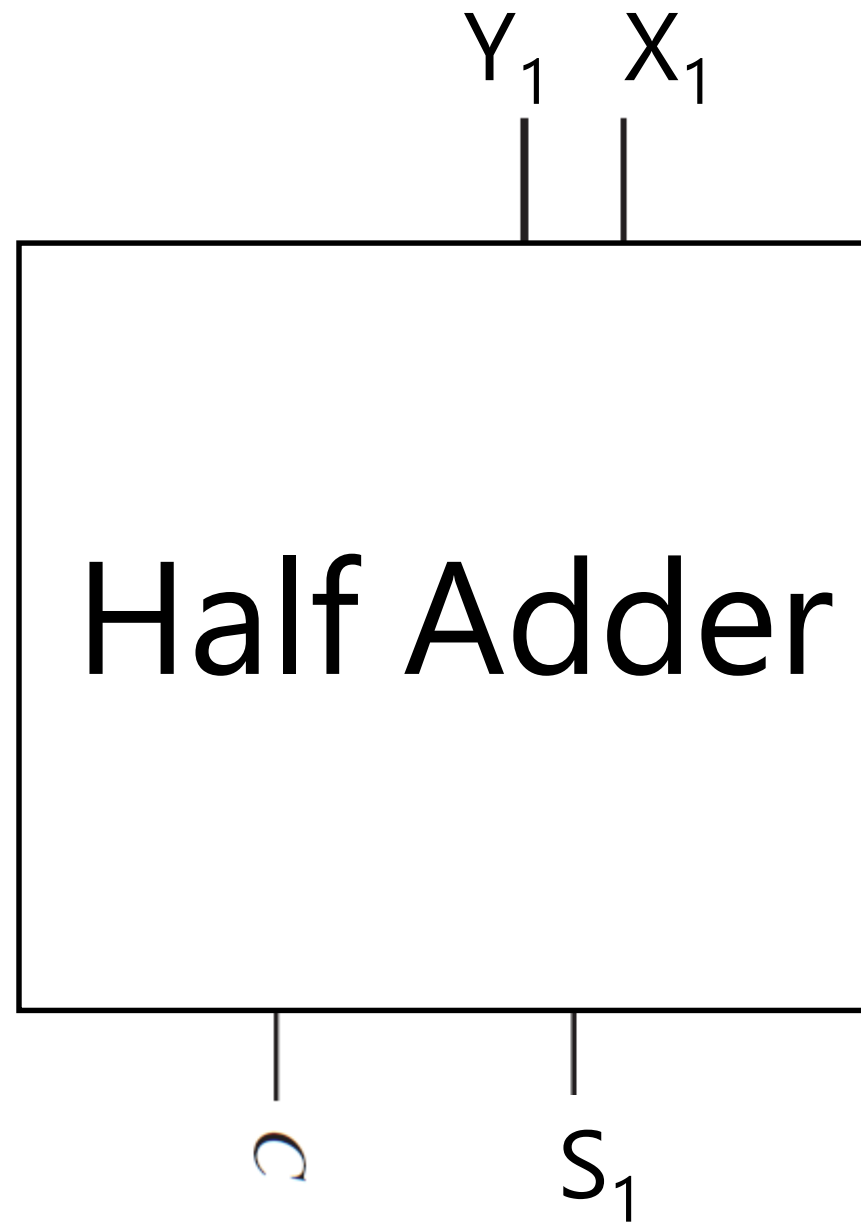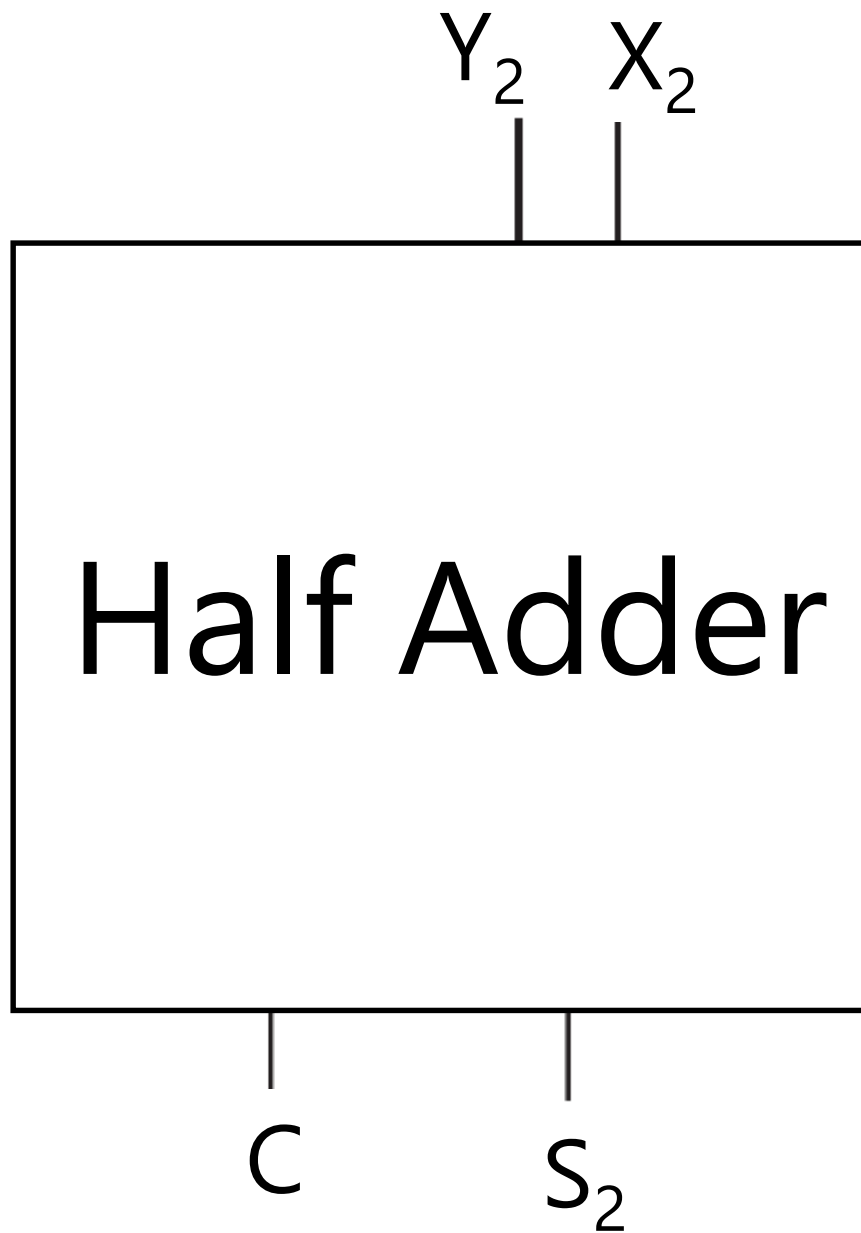

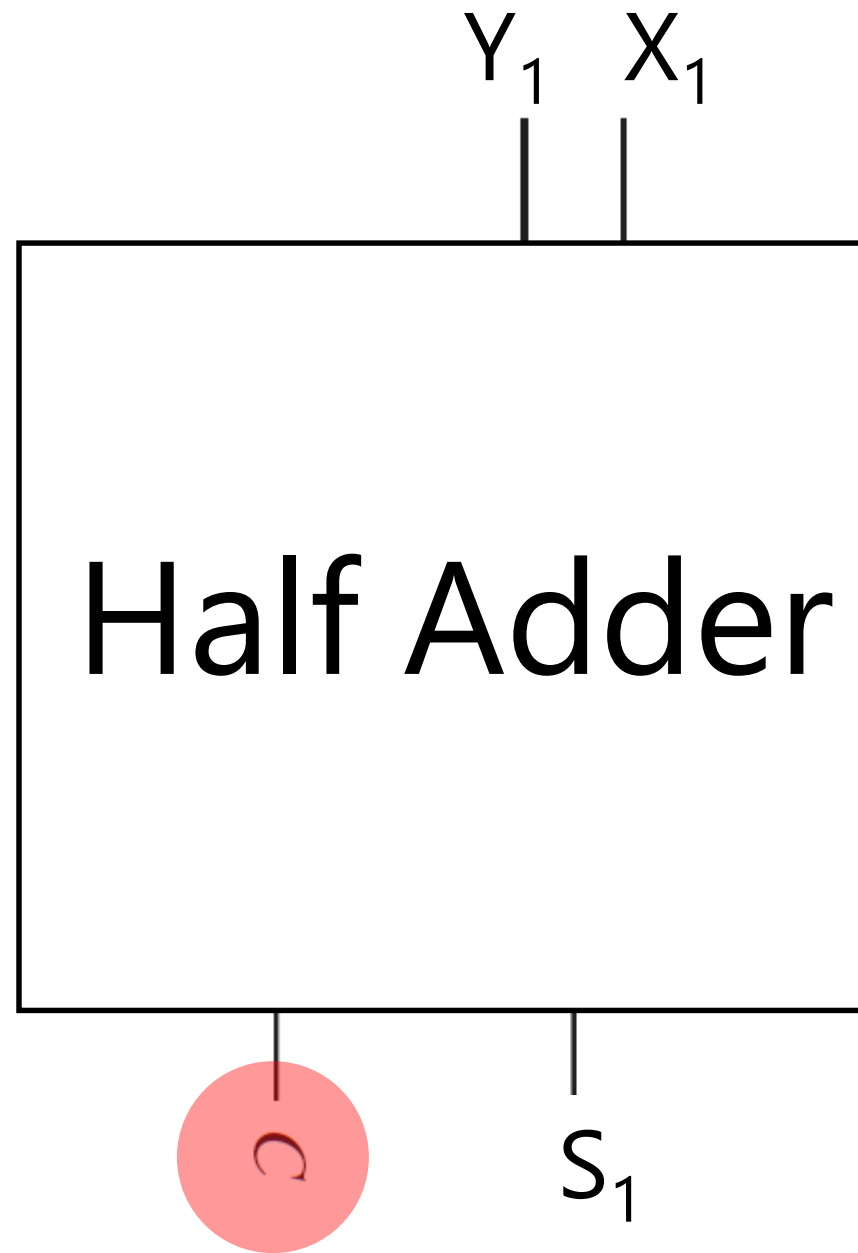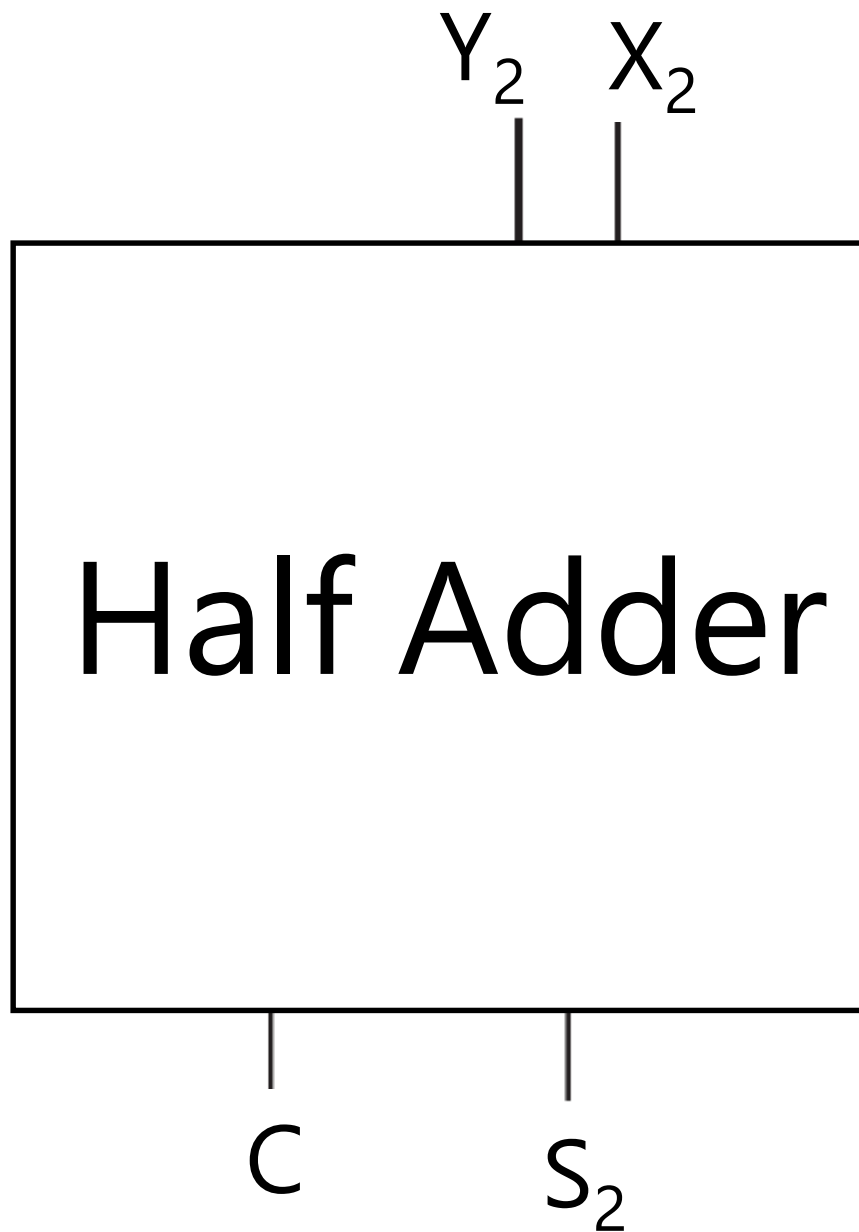



C=1

0 1

+ 0 1

C=0 1 0

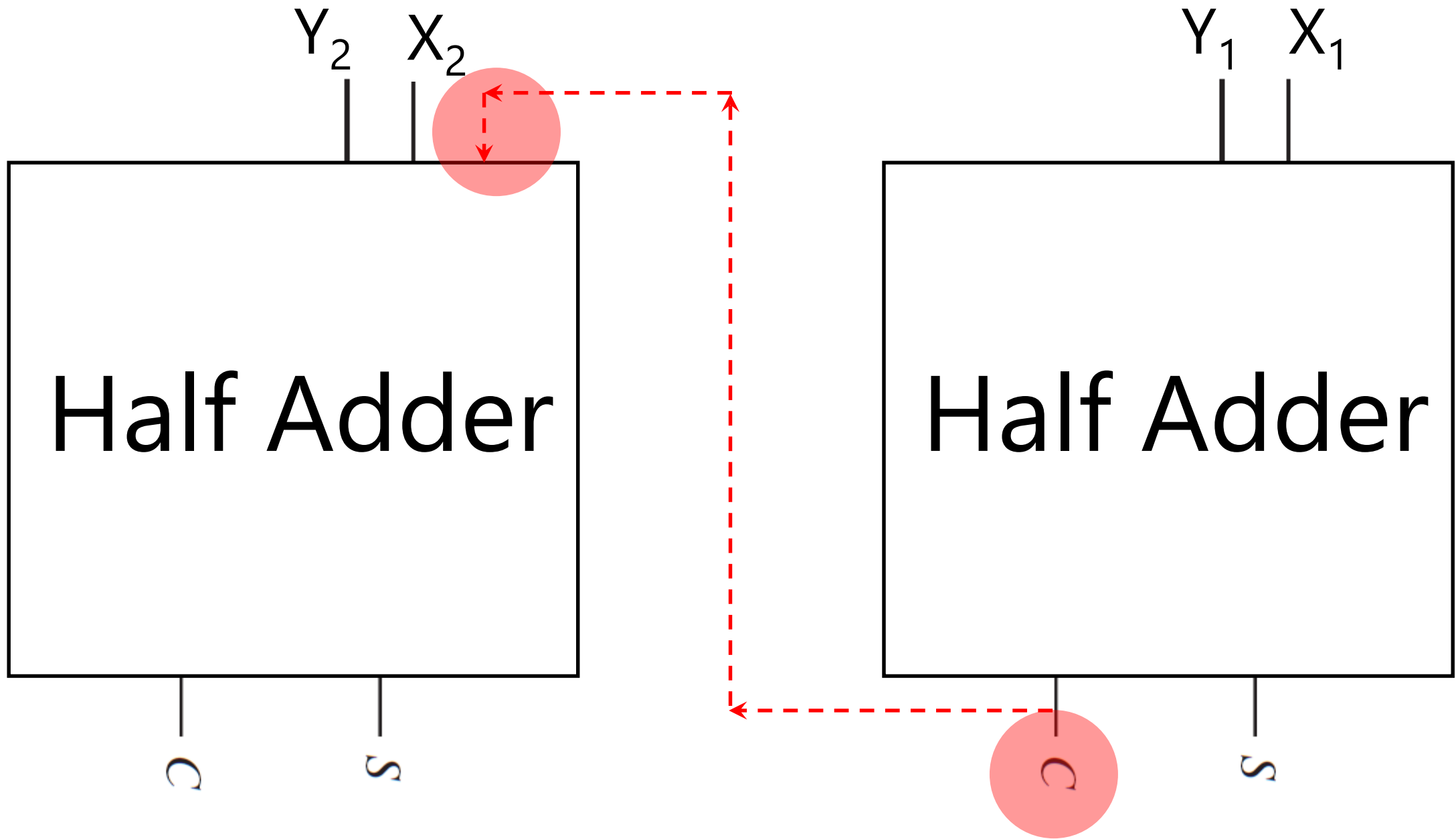

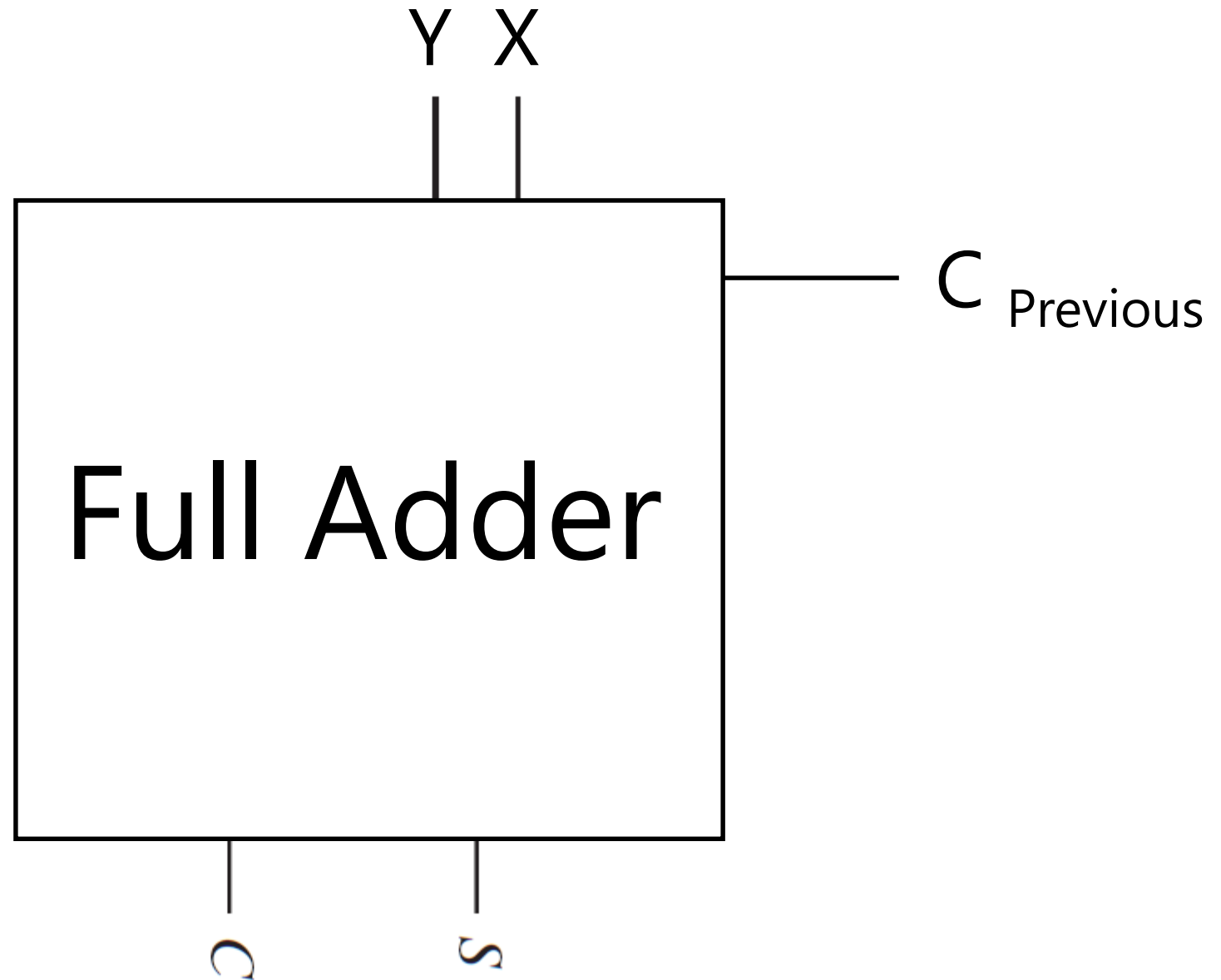

Design a logic circuit that adds two binary digits (bit) and a carry bit.

C _p	Y	X	C=Σm(3,5,6,7)	S=Σm(1,2,4,7)
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$C = \sum m(3, 5, 6, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	0 m_1	1 m_3	0 m_2
	1	0 m_4	1 m_5	1 m_7	1 m_6

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$S = C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX \\
 &= C'_p (Y'X + YX') + C_p (Y'X' + YX)
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX \\
 &= C'_p (Y'X + YX') + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (Y'X' + YX)
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX \\
 &= C'_p (Y'X + YX') + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (X \odot Y)
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C_p' Y' X + C_p' Y X' + C_p Y' X' + C_p Y X \\
 &= C_p' (Y' X + Y X') + C_p (Y' X' + Y X) \\
 &= C_p' (X \oplus Y) + C_p (Y' X' + Y X) \\
 &= C_p' (X \oplus Y) + C_p (X \odot Y) \\
 &= C_p' (X \oplus Y) + C_p (X \oplus Y)'
 \end{aligned}$$

$$\begin{aligned}
 (X \oplus Y)' &= (Y' X + Y X')' \\
 &= (Y' X)' (Y X')' \\
 &= (Y + X') (Y' + X) \\
 &= Y Y' + Y X + X' Y' + X' X \\
 &= 0 + Y X + X' Y' + 0 \\
 &= Y X + X' Y' \\
 &= Y \odot X
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX \\
 &= C'_p (Y'X + YX') + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (X \odot Y) \\
 &= C'_p (X \oplus Y) + C_p (X \oplus Y)' \\
 &= C'_p \alpha + C_p \alpha'
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX \\
 &= C'_p (Y'X + YX') + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (X \odot Y) \\
 &= C'_p (X \oplus Y) + C_p (X \oplus Y)' \\
 &= C'_p \alpha + C_p \alpha' \\
 &= C_p \oplus \alpha
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6

$$\begin{aligned}
 S &= C'_p Y'X + C'_p YX' + C_p Y'X' + C_p YX \\
 &= C'_p (Y'X + YX') + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (Y'X' + YX) \\
 &= C'_p (X \oplus Y) + C_p (X \odot Y) \\
 &= C'_p (X \oplus Y) + C_p (X \oplus Y)' \\
 &= C'_p \alpha + C_p \alpha' \\
 &= C_p \oplus \alpha \\
 &= C_p \oplus (X \oplus Y)
 \end{aligned}$$

$$S = \sum m(1, 2, 4, 7)$$

$$S = C_p \oplus (X \oplus Y)$$


		YX			
		00	01	11	10
C_p	0	0 m_0	1 m_1	0 m_3	1 m_2
	1	1 m_4	0 m_5	1 m_7	0 m_6


\oplus is associative, we can drop (). But let's keep them!


$$C = \sum m(3, 5, 6, 7)$$


		YX			
		00	01	11	10
C_p	0	0 m_0	0 m_1	1 m_3	0 m_2
	1	0 m_4	1 m_5	1 m_7	1 m_6



$$C = YX + C_p X + C_p Y$$

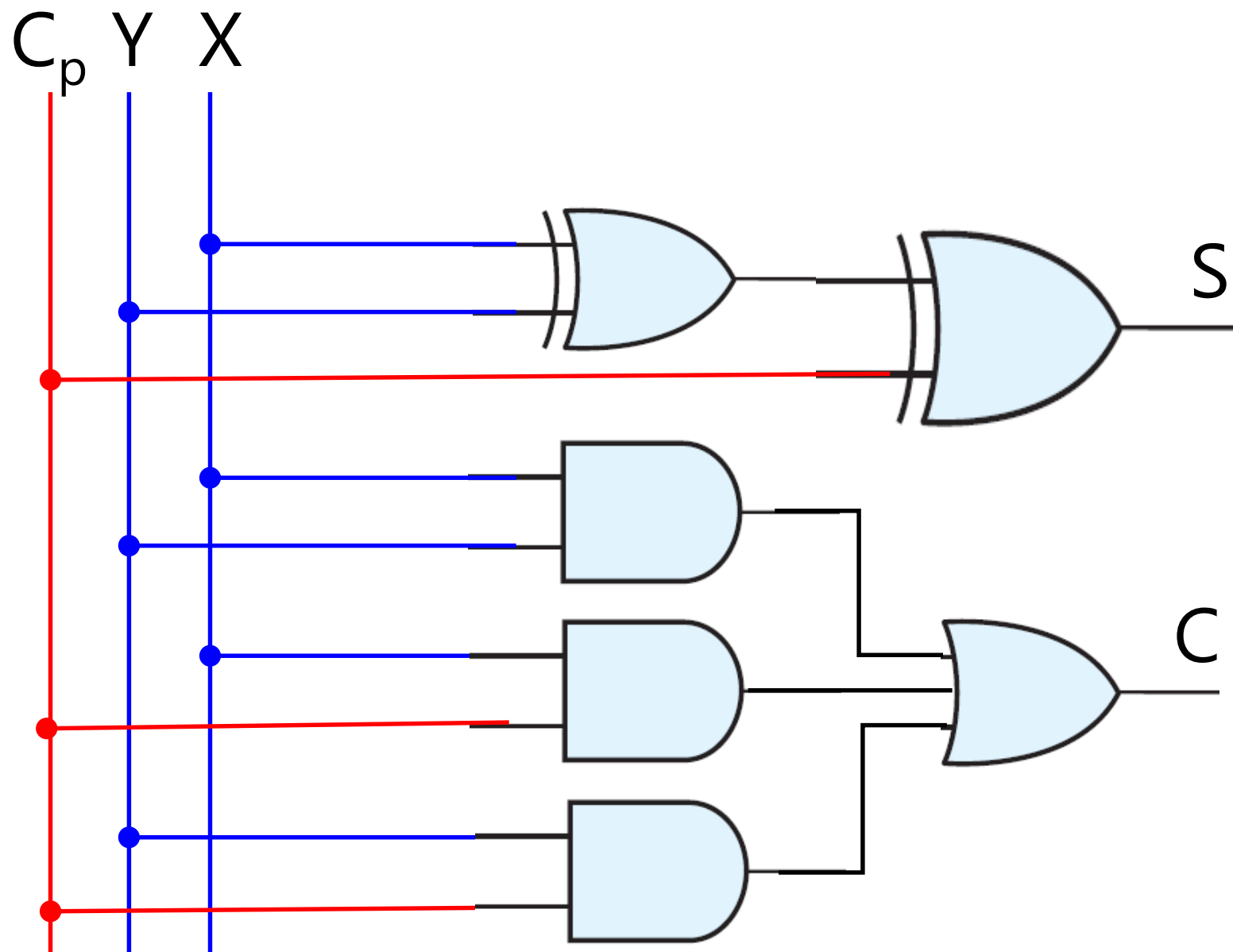


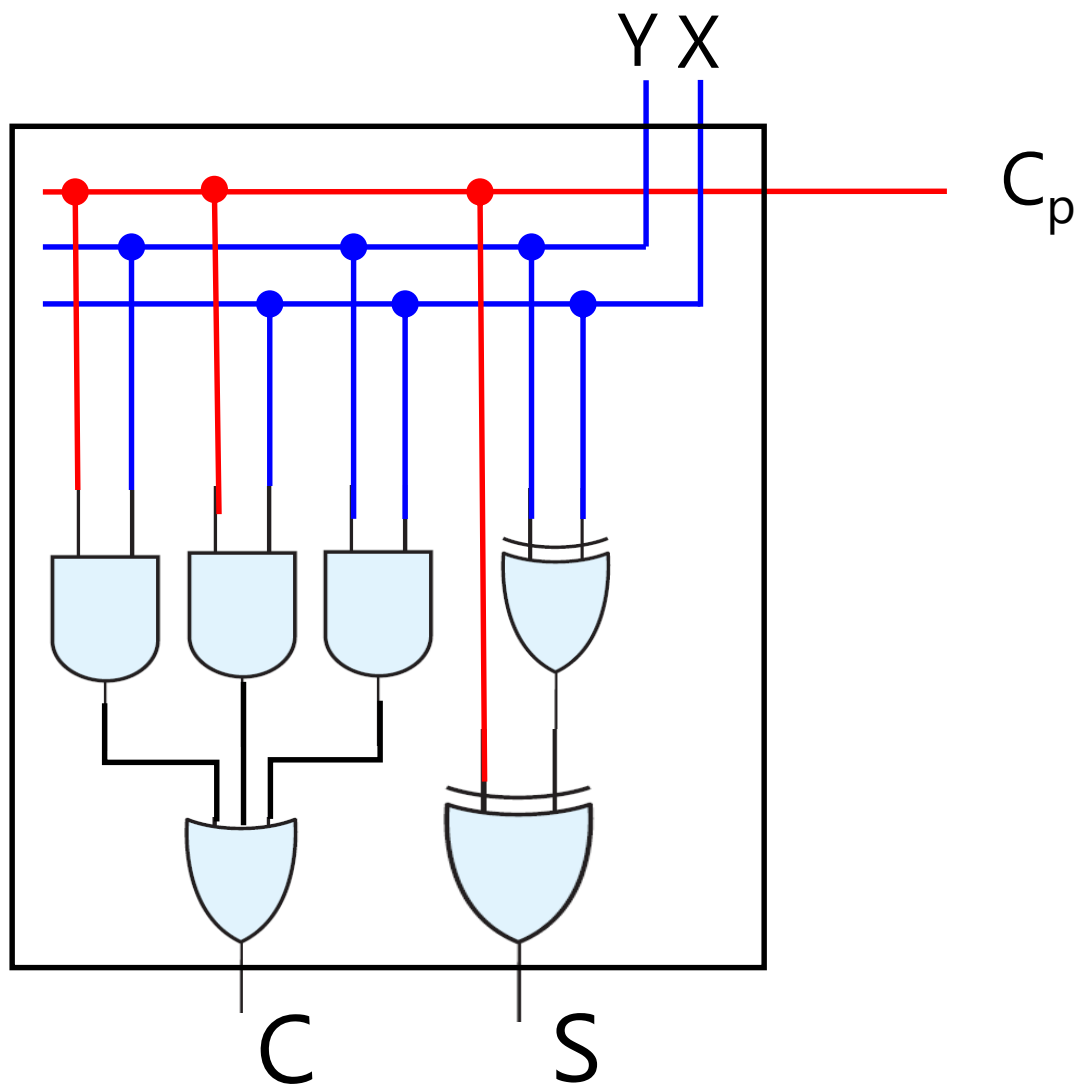

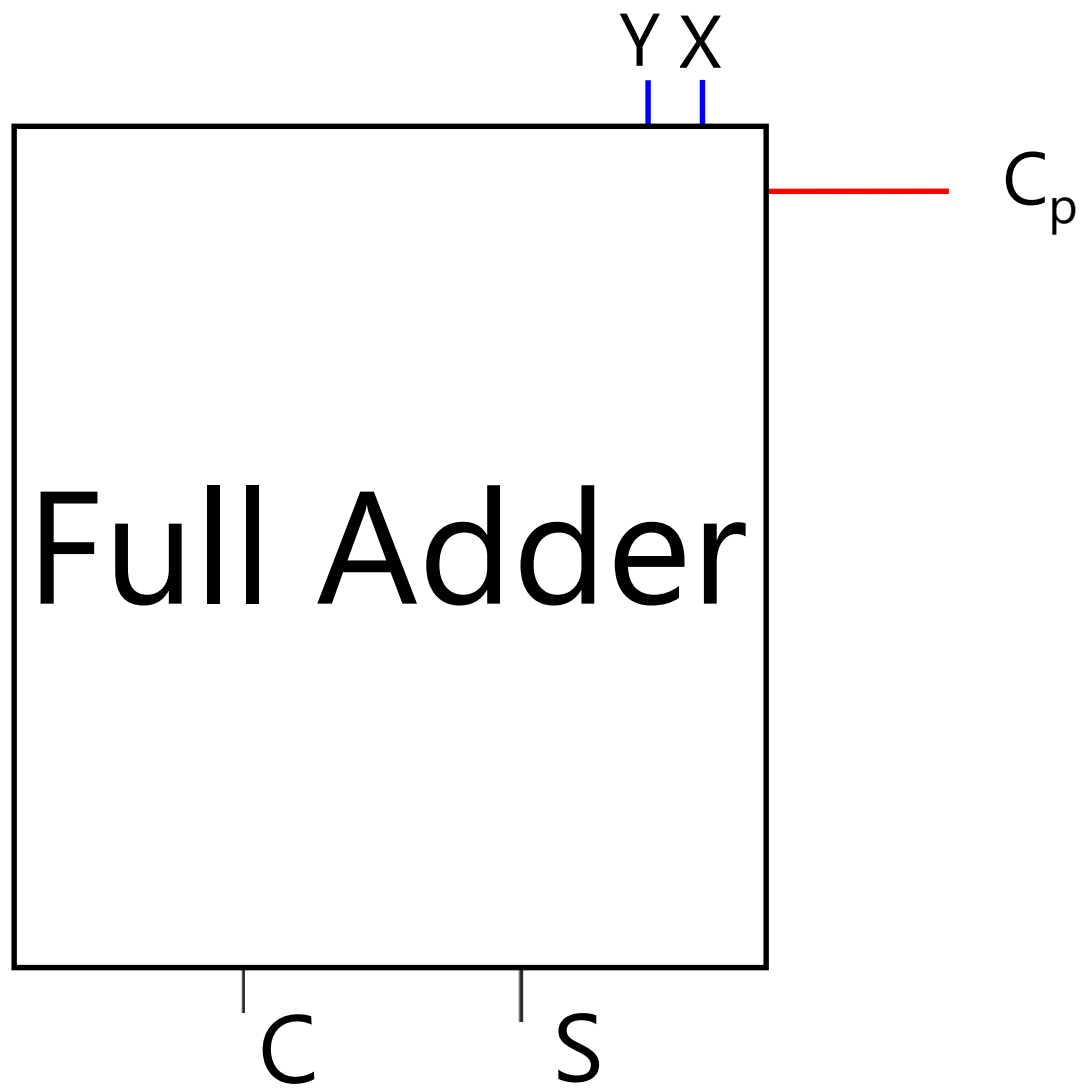


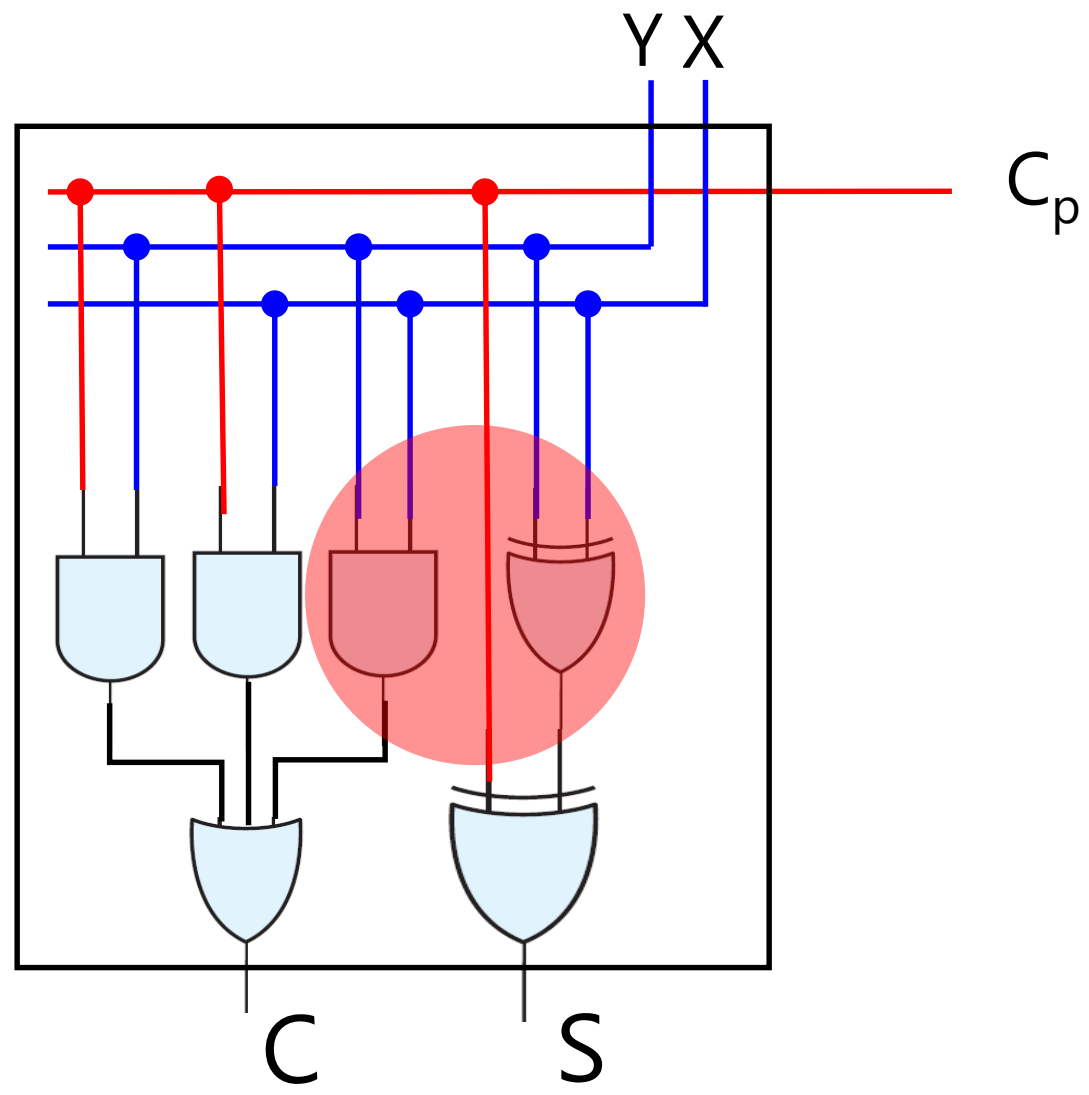

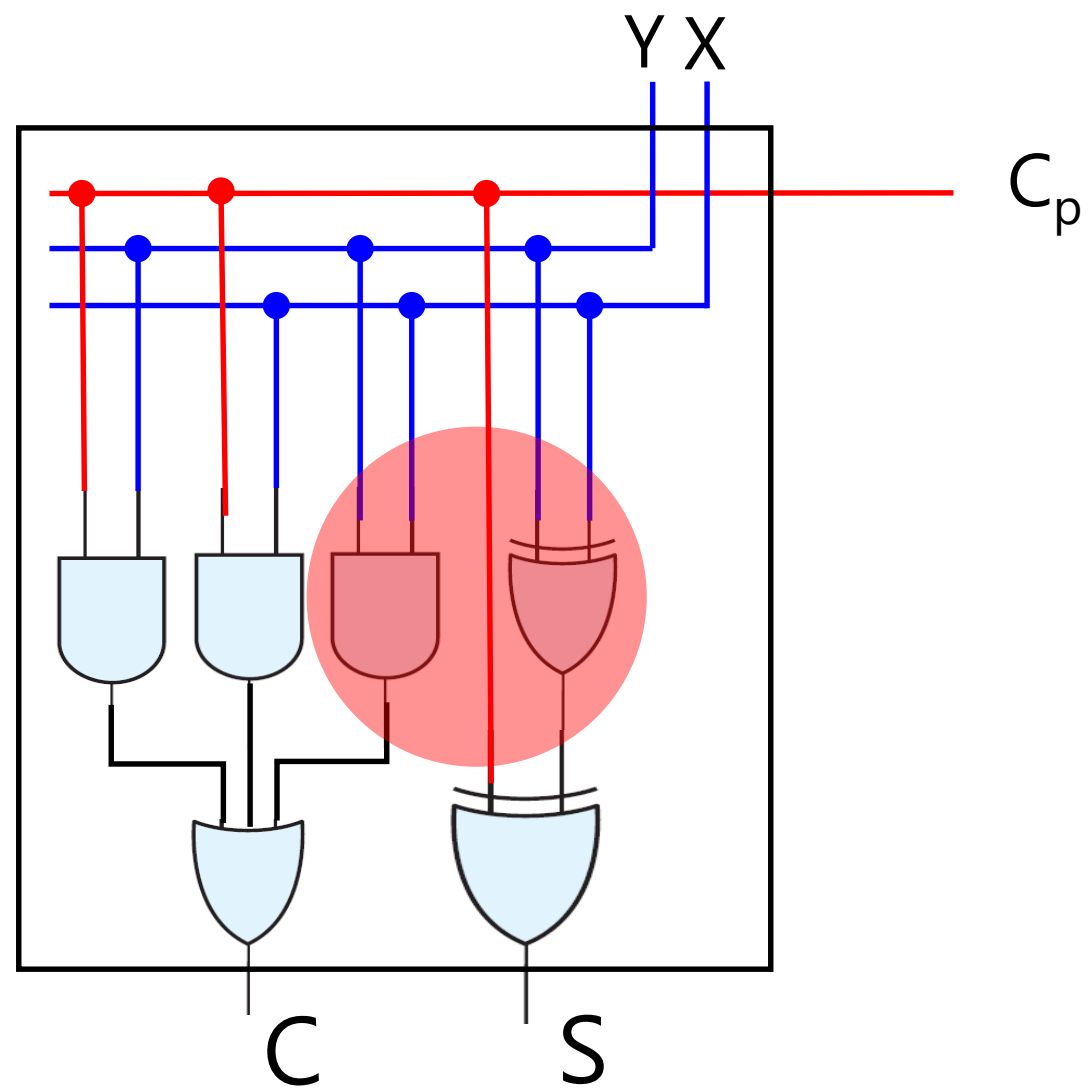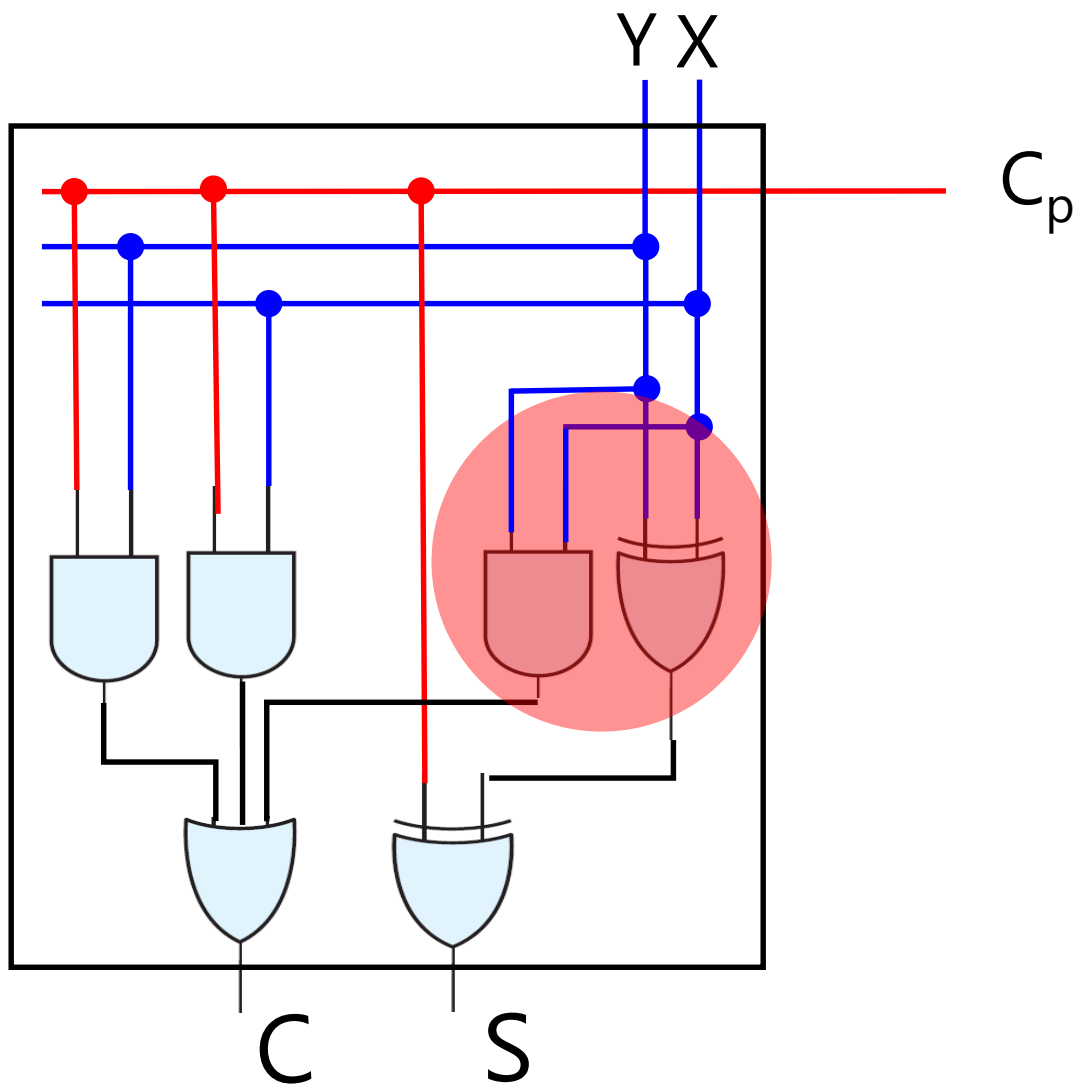


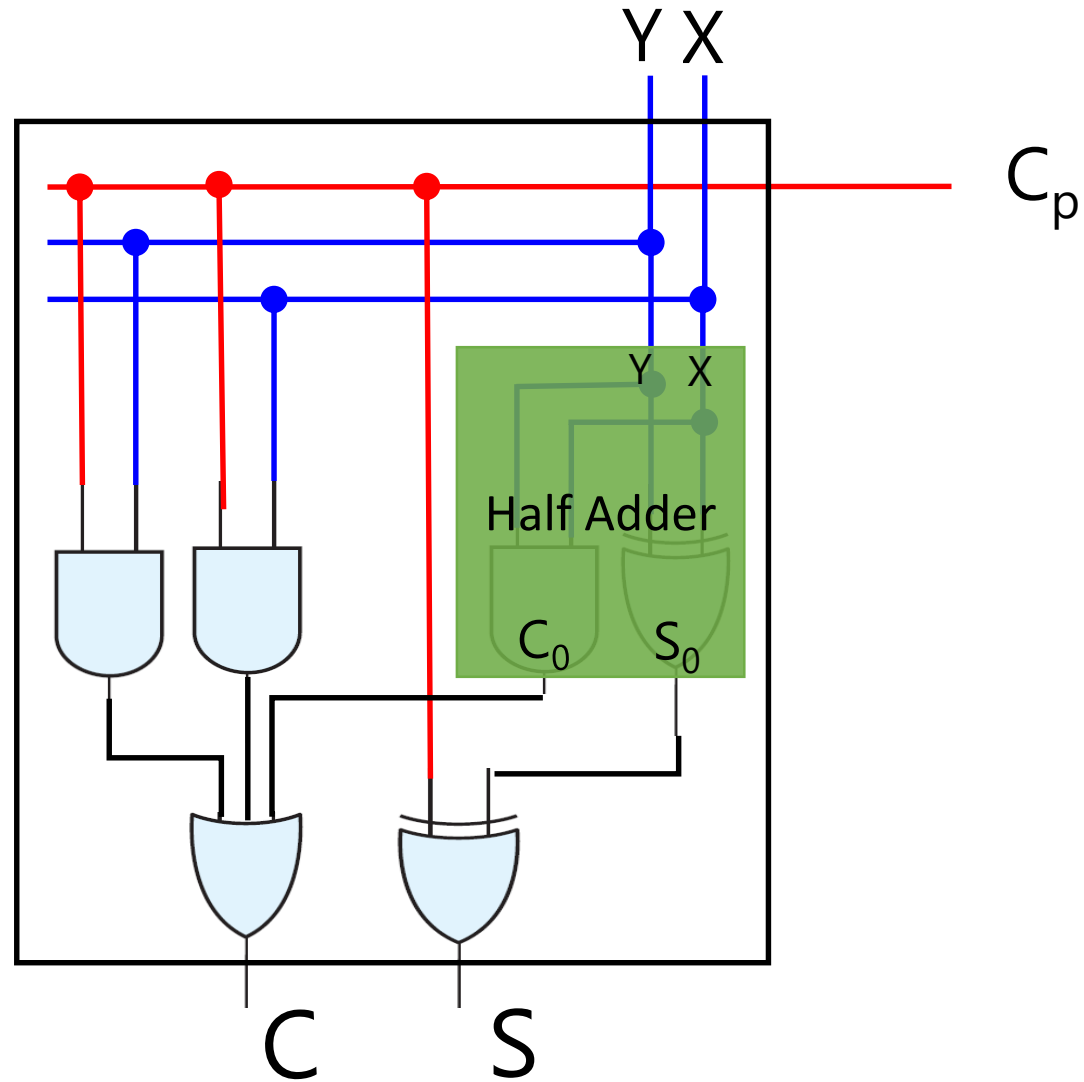




Full Adder = Half Adder + ...


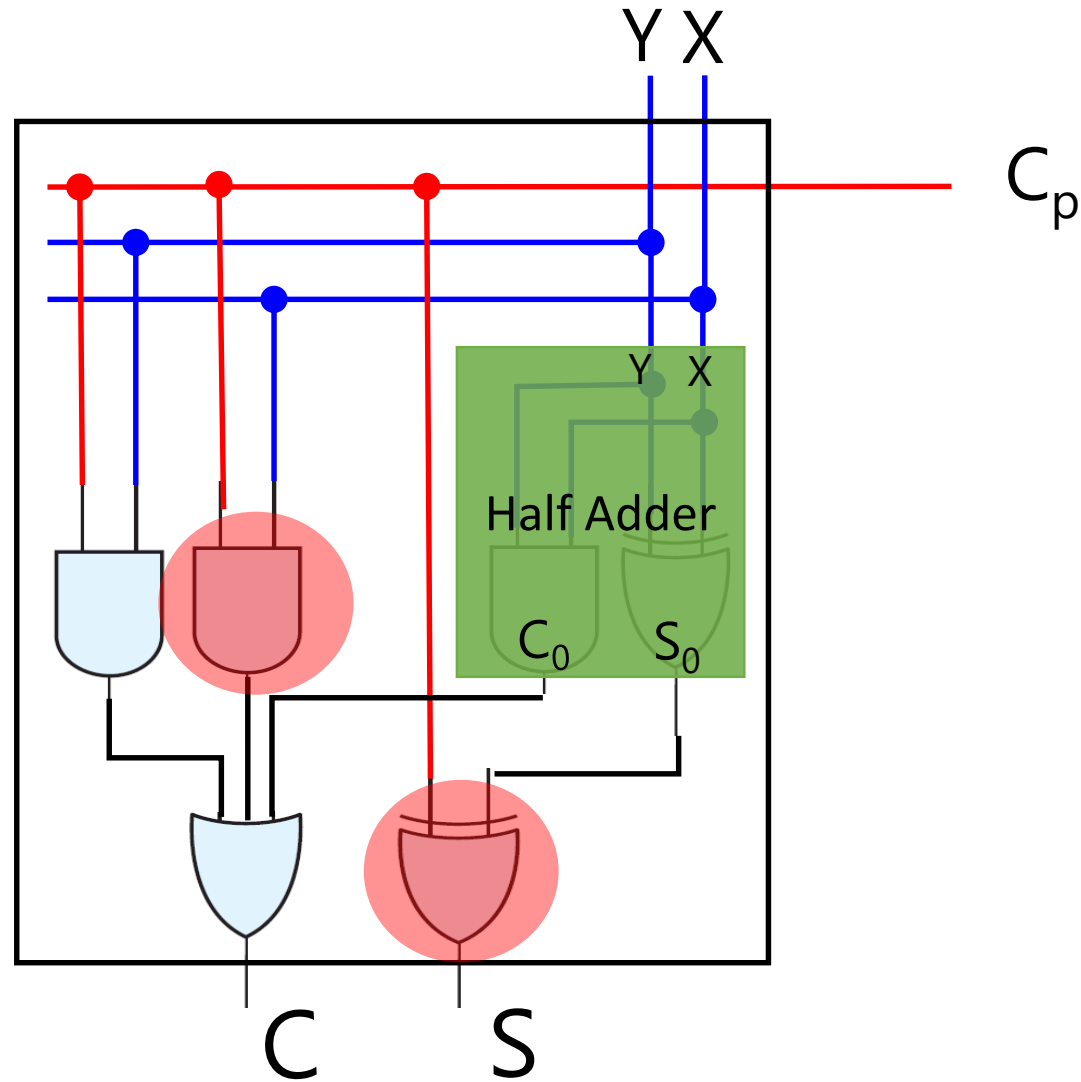




Full Adder = ? 2 Half Adder + ...

Full Adder \propto 2 Half Adder

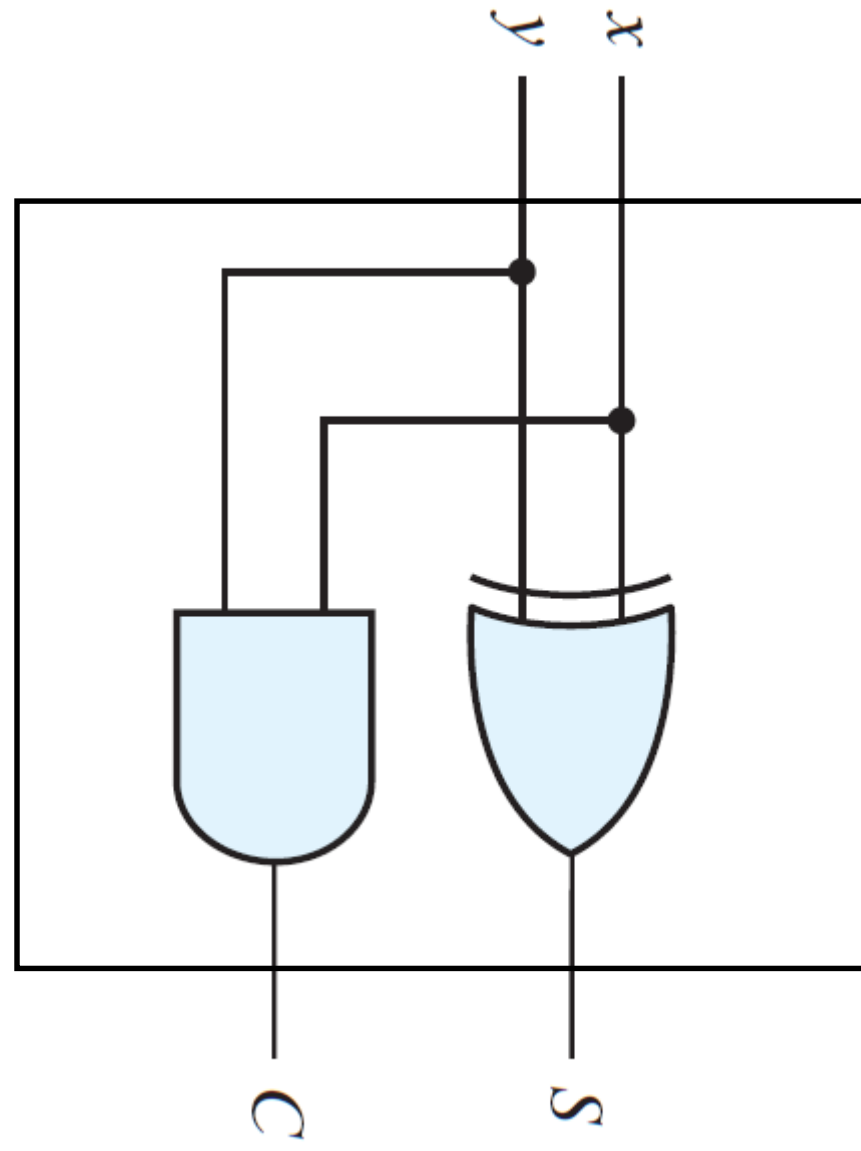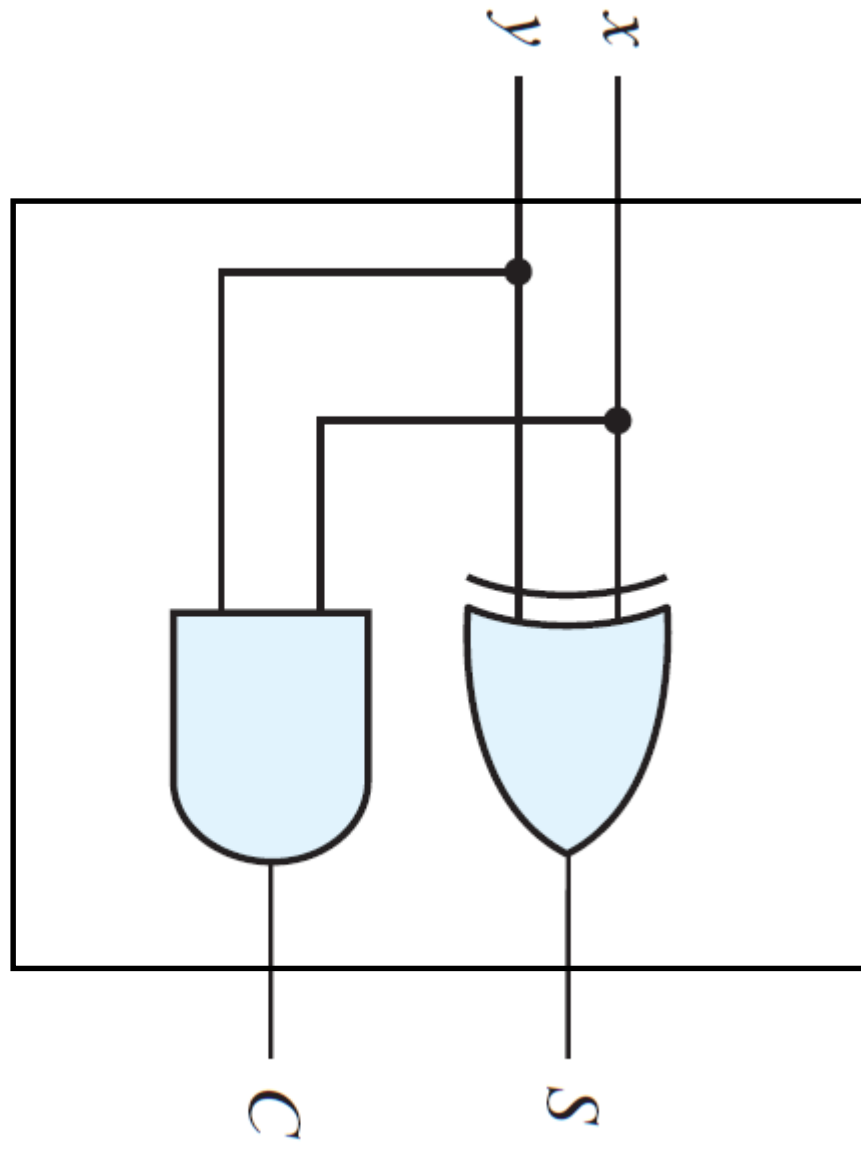

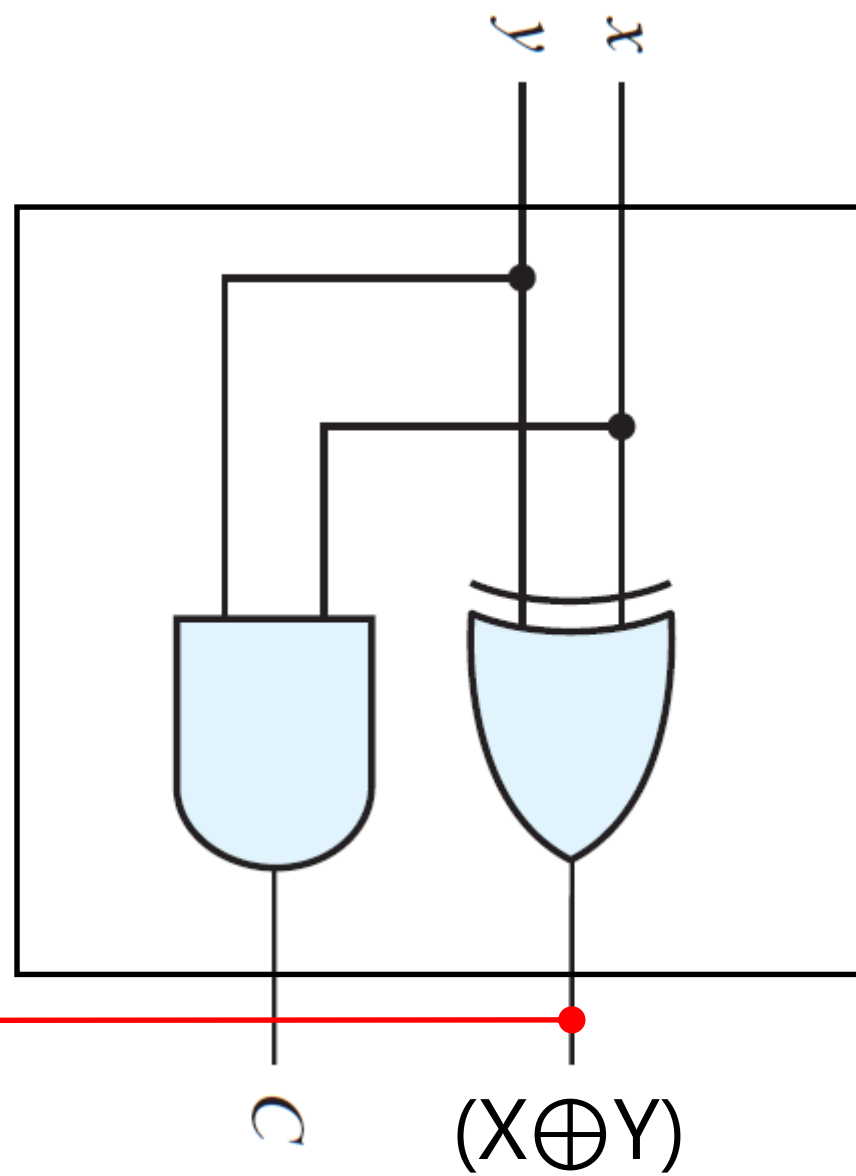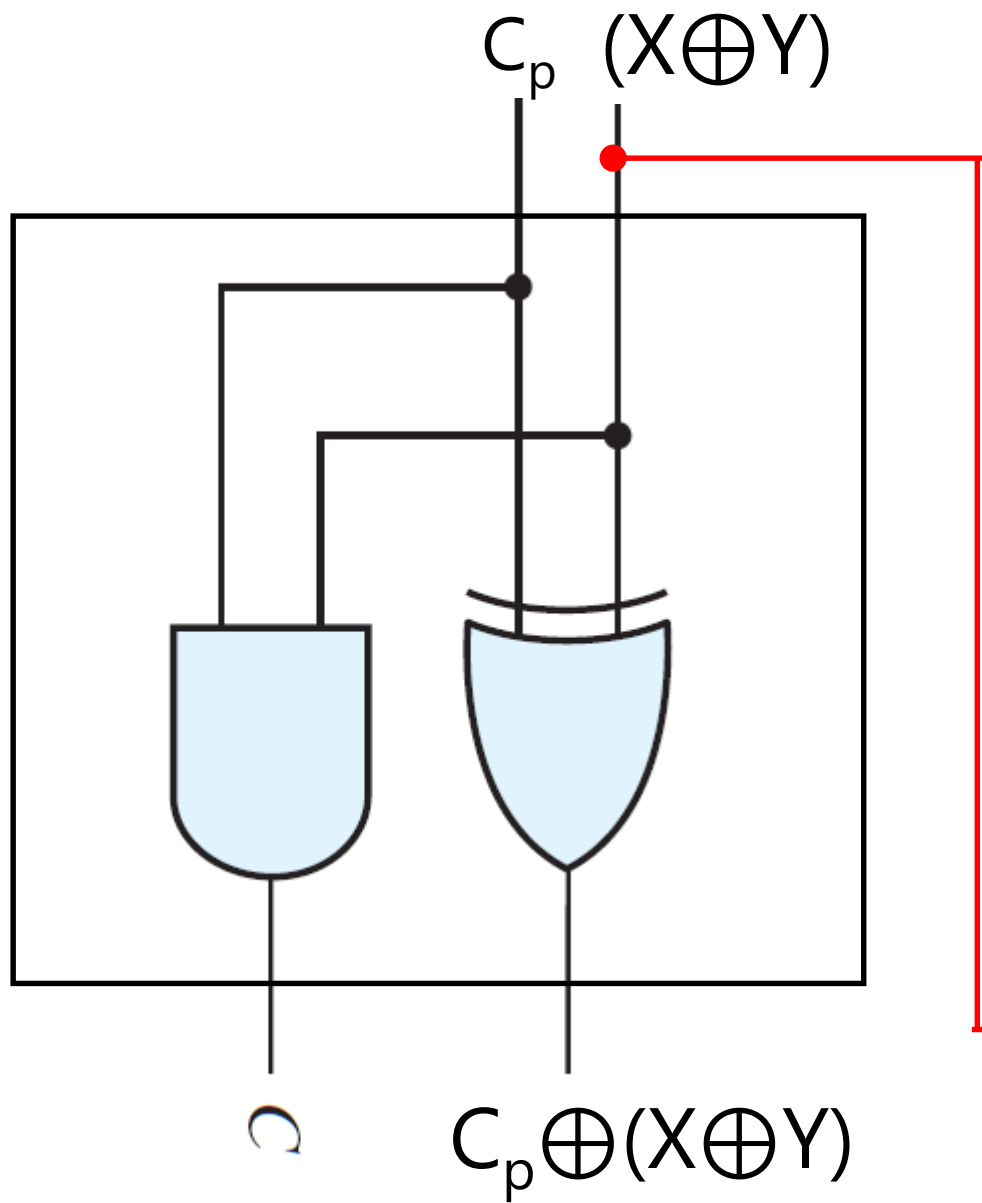


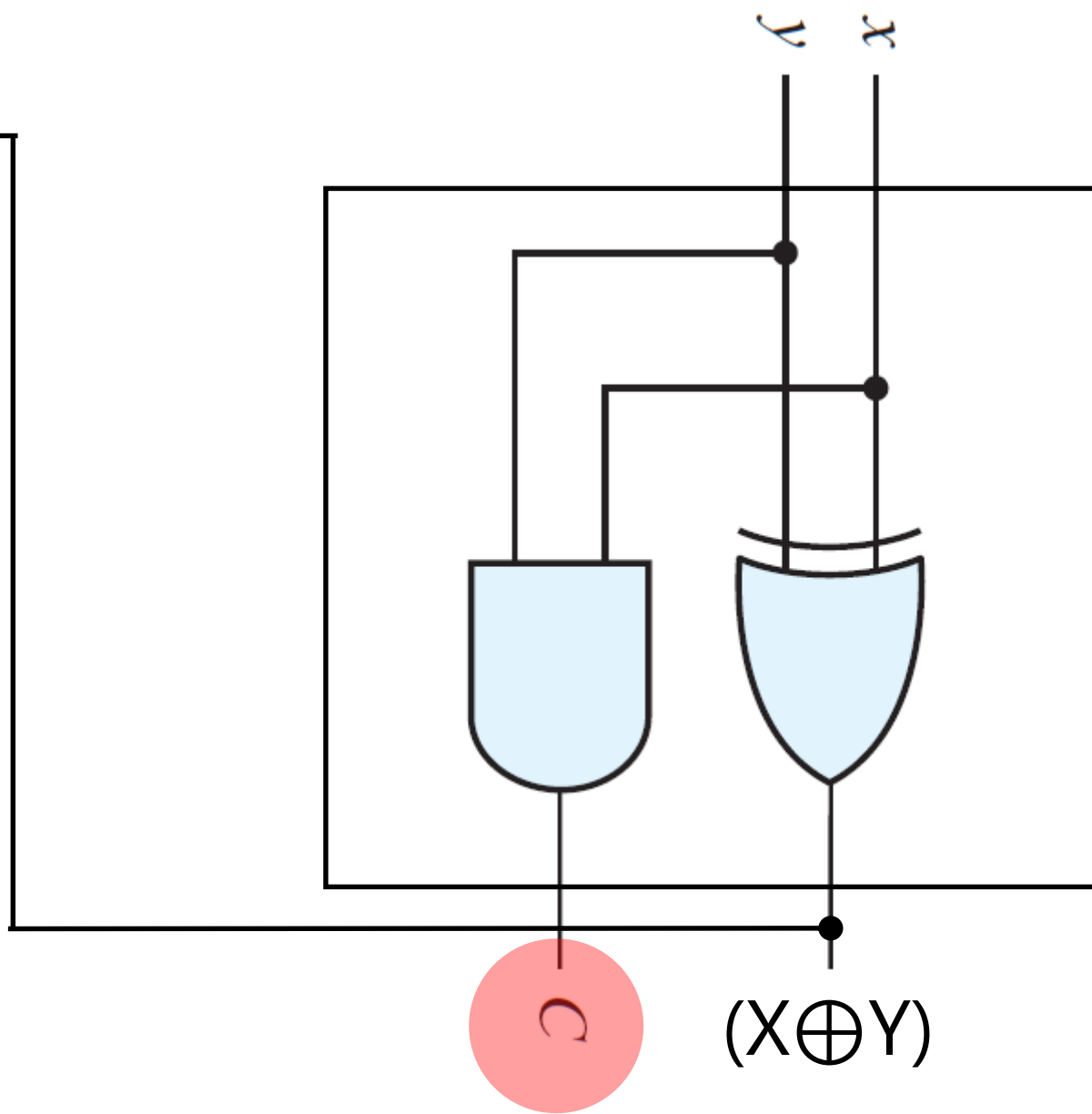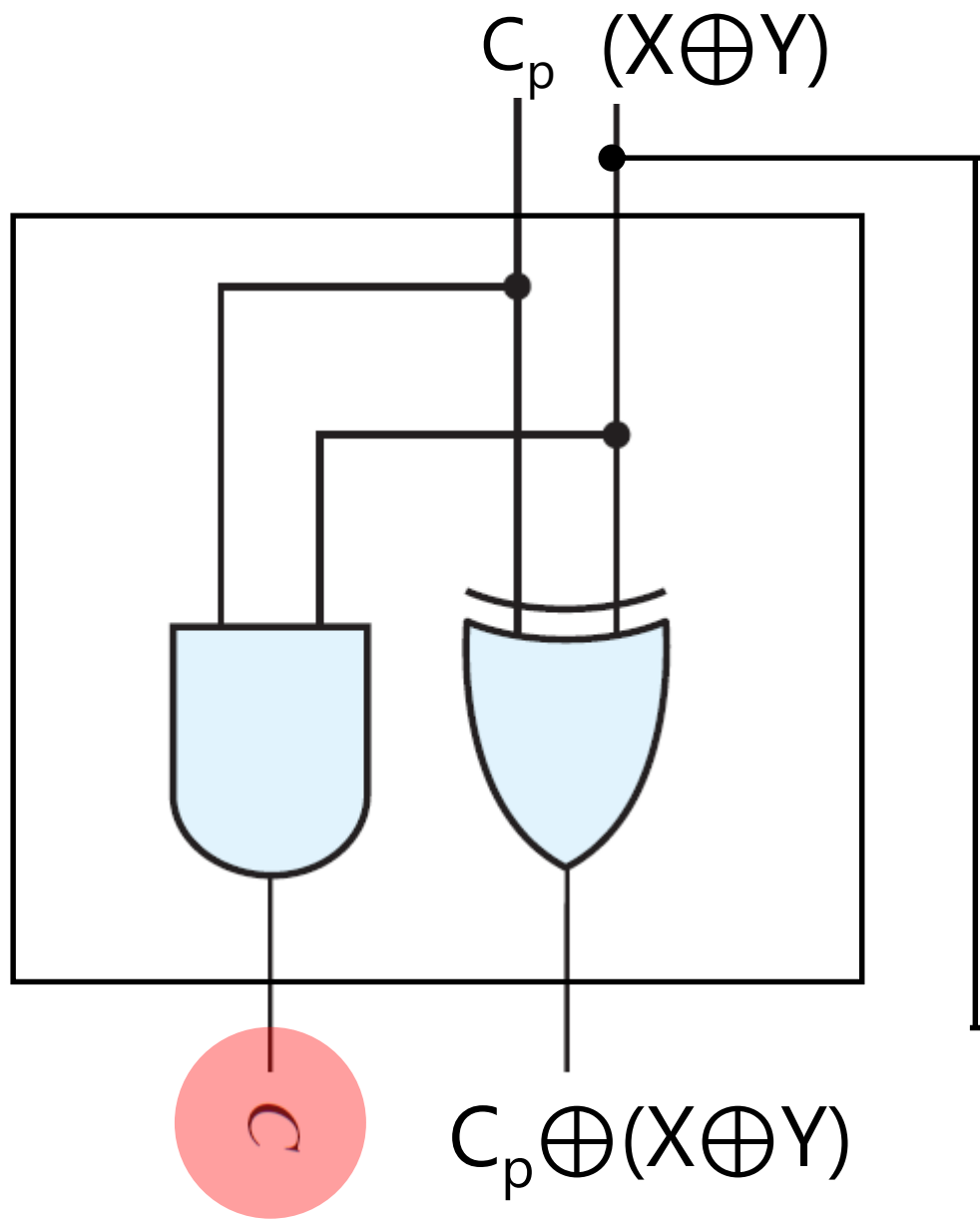

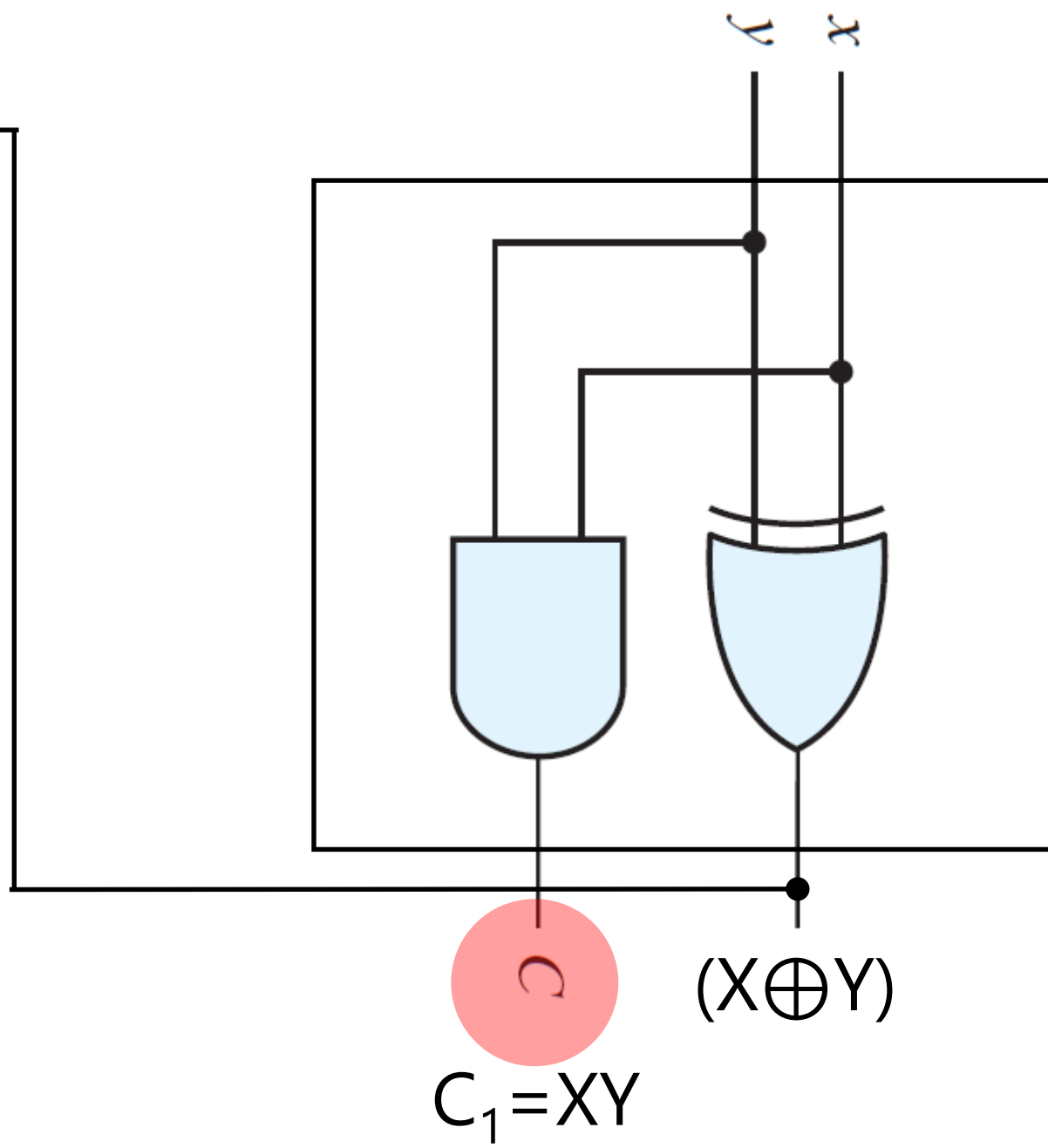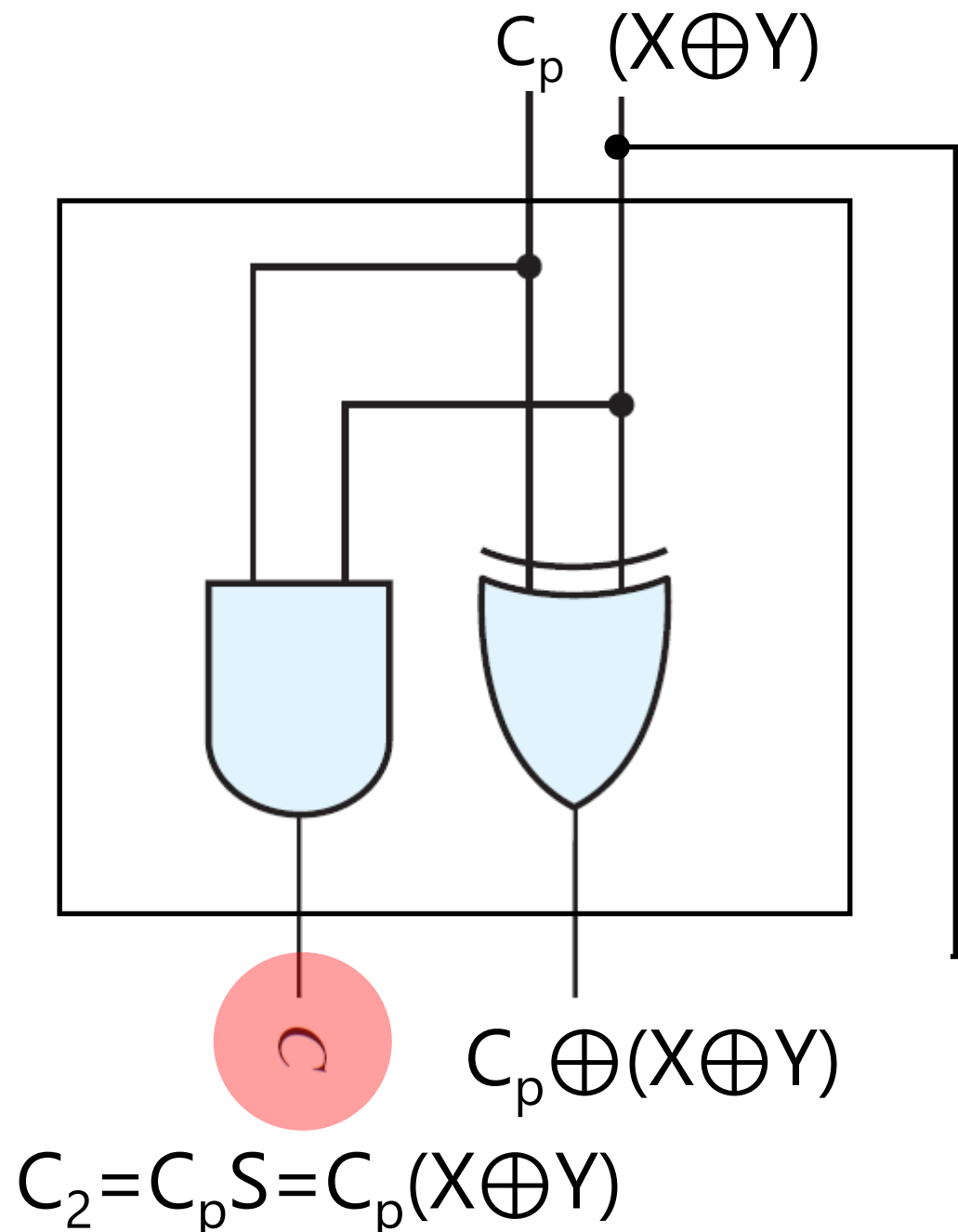

$$C_1 = XY$$

$$C_2 = C_p S = C_p (X \oplus Y)$$

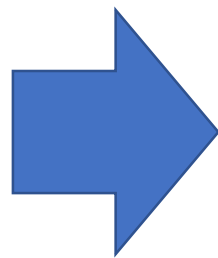

$$C = XY + C_p X + C_p Y$$

$$C = \sum m(3, 5, 6, 7)$$

		YX			
		00	01	11	10
C_p	0	0 m_0	0 m_1	1 m_3	0 m_2
	1	0 m_4	1 m_5	1 m_7	1 m_6


$$C = YX + C_p Y'X + C_p YX'$$


$$C = YX + C_p Y'X + C_p YX'$$

$$C = YX + C_p (Y'X + YX')$$


$$C = YX + C_p (X \oplus Y)$$

$$C = C_1 + C_2$$

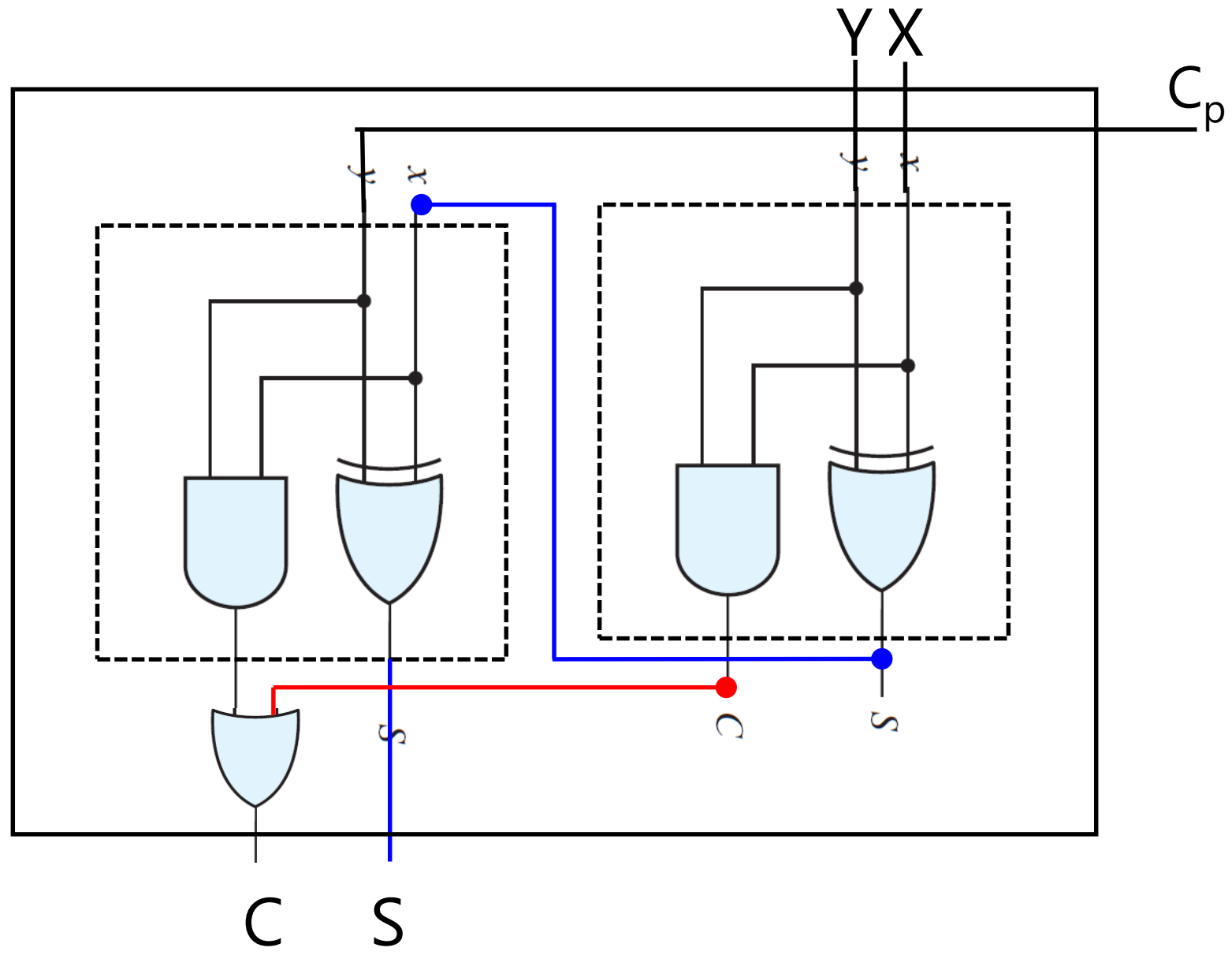

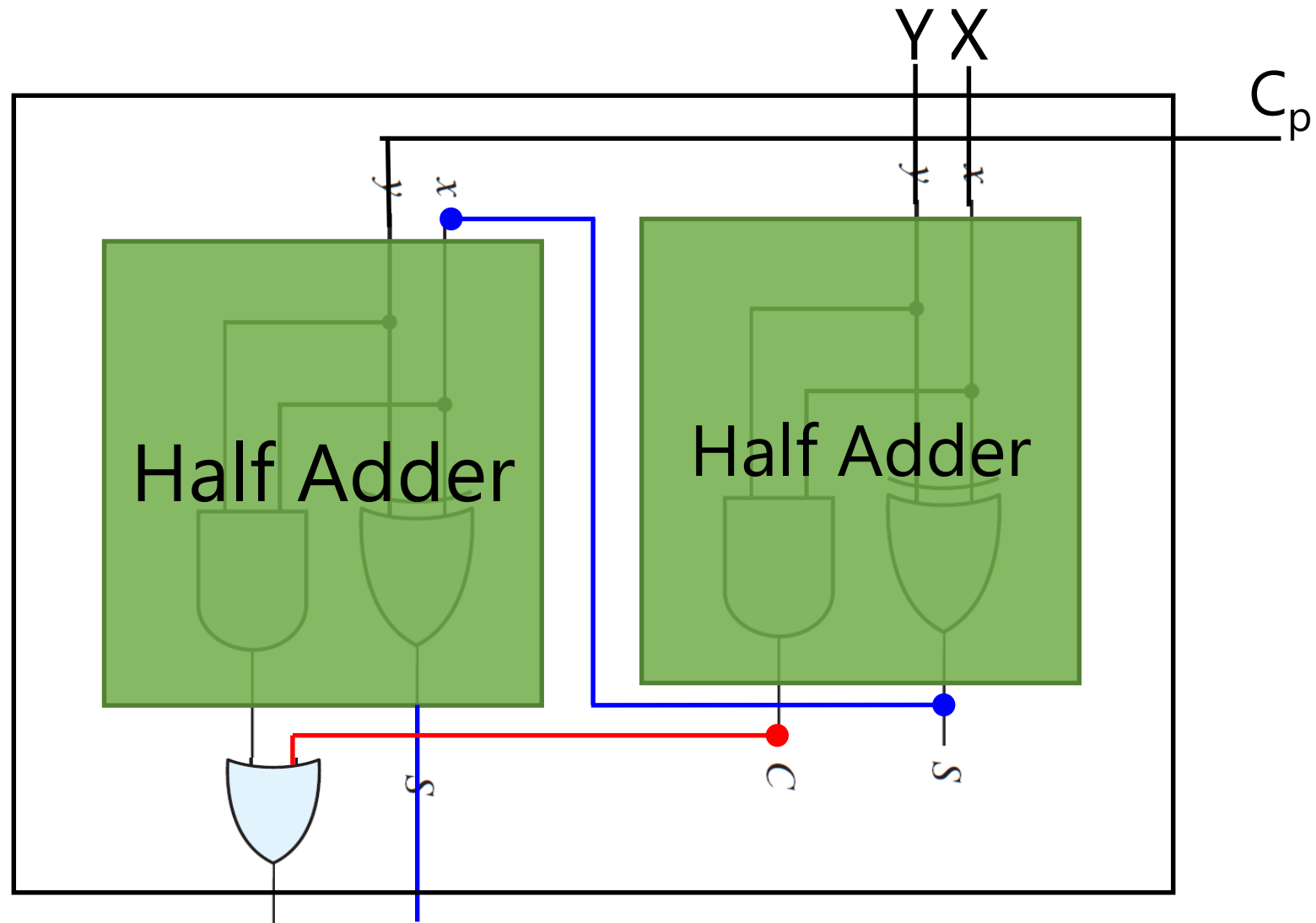


Full Adder^C = 2 Half Adder + OR

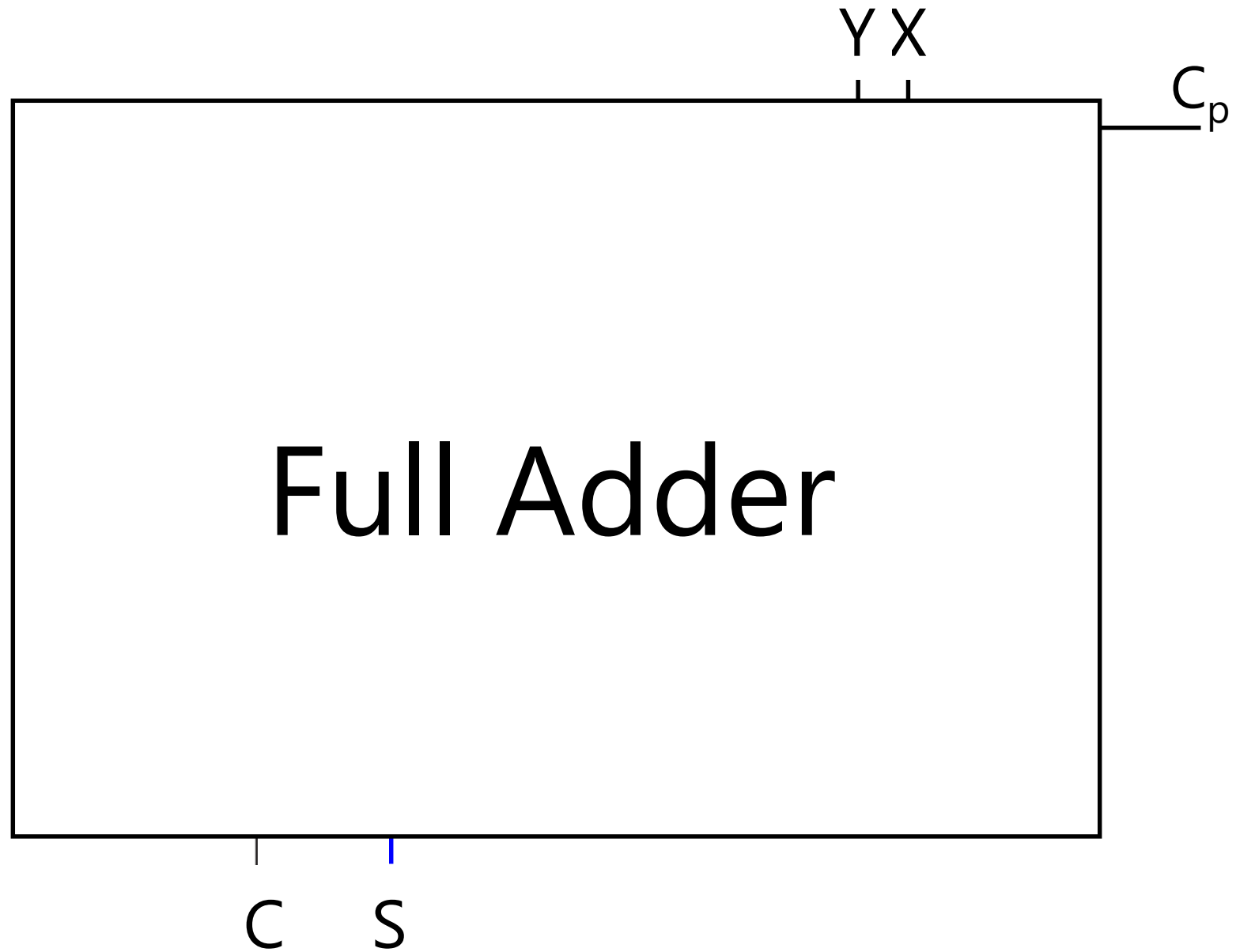



Design a logic circuit that
adds two binary numbers!

$$\begin{array}{r}
 C_3 C_2 C_1 C_0 \\
 X_4 X_3 X_2 X_1 \\
 + \quad Y_4 Y_3 Y_2 Y_1 \\
 \hline
 C_4 \quad S_4 S_3 S_2 S_1
 \end{array}$$


$C_0 = 0$

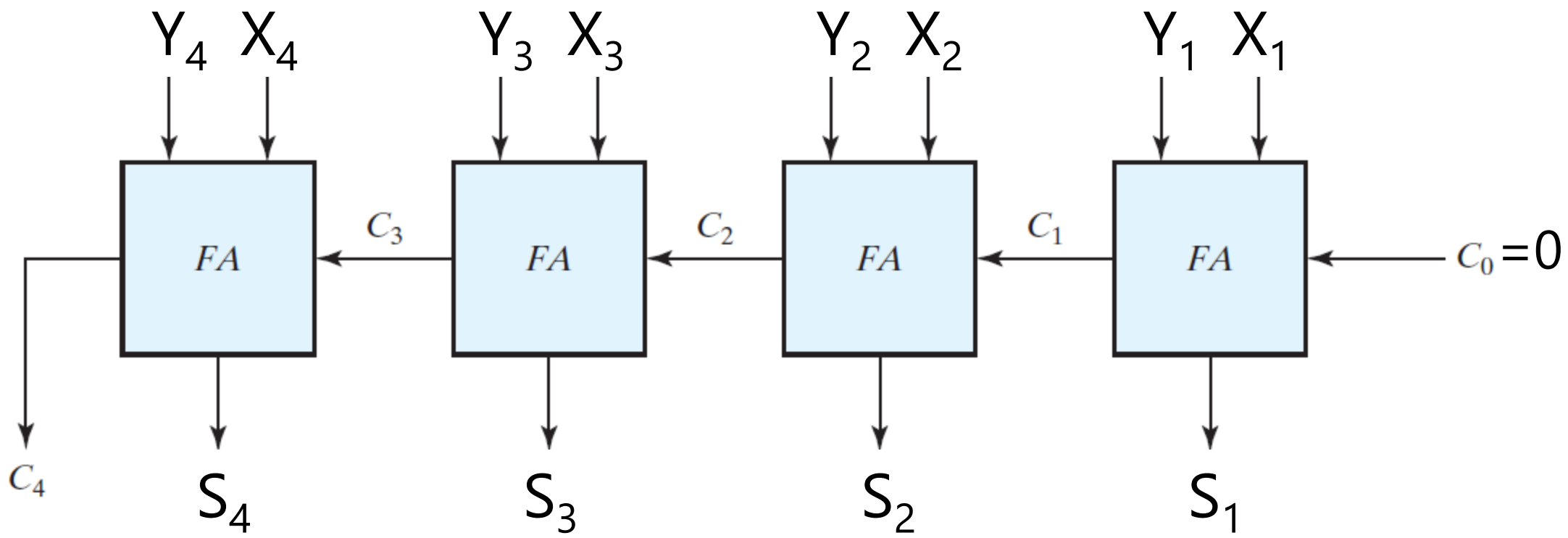

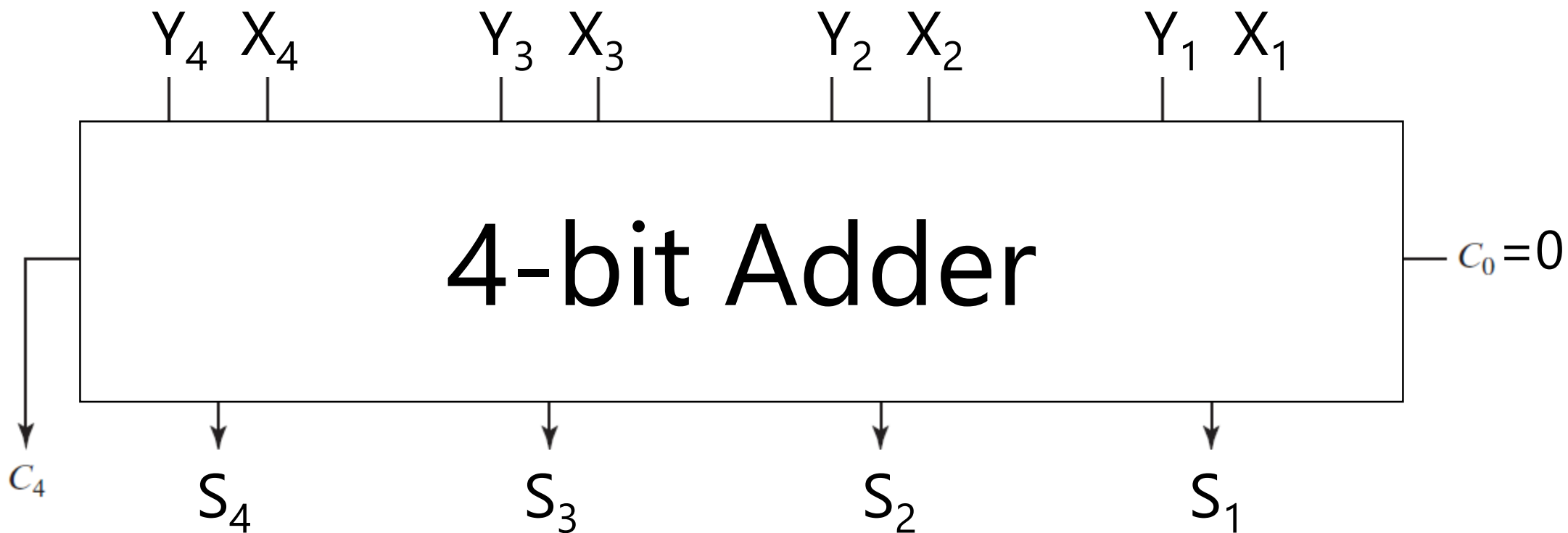

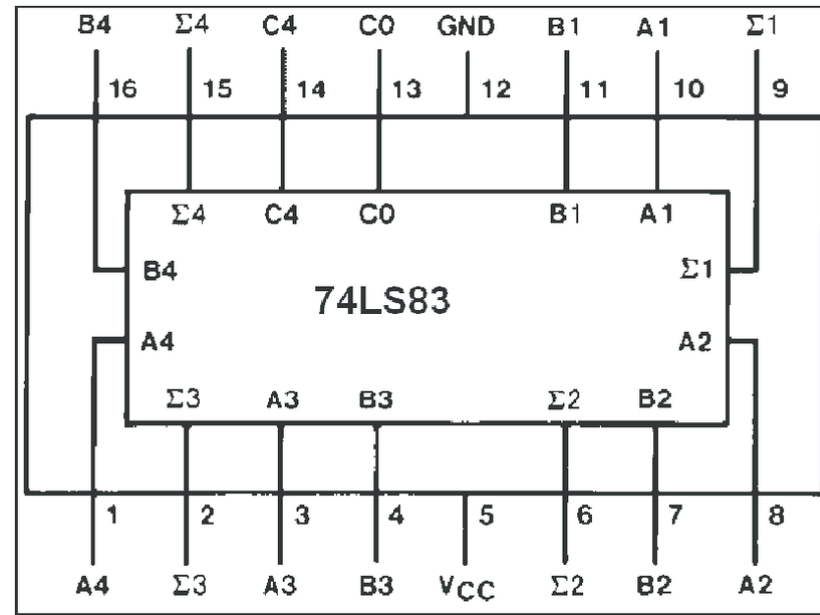

74LS83 pinout

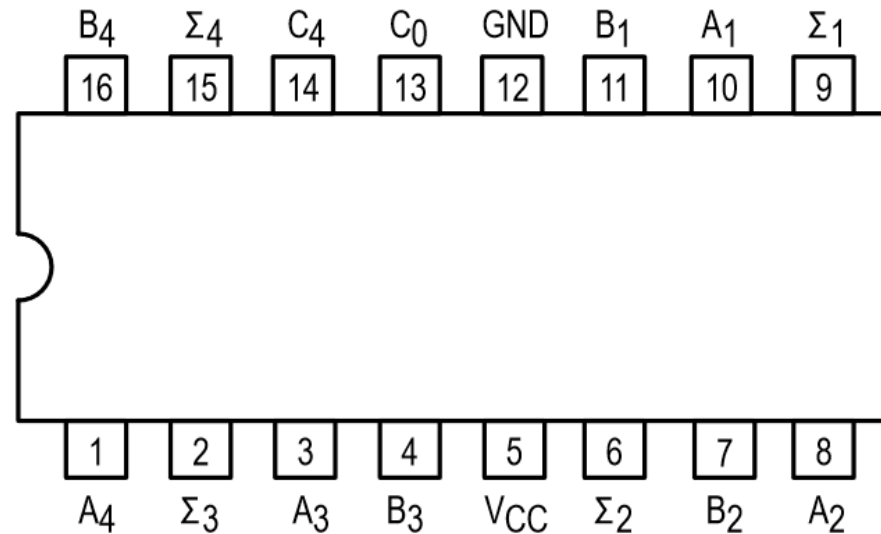

V_{CC}

A₁–A₄

B₁–B₄

C₀

Σ₁–Σ₄

C₄

5.5V max, 5V Typical

Operand A Inputs

Operand B Inputs

Carry Input


Sum Outputs (Note b)

Carry Output (Note b)

eBay > Business & Industrial > Electrical Equipment & Supplies > Other Electrical Equipment & Supplies

Share

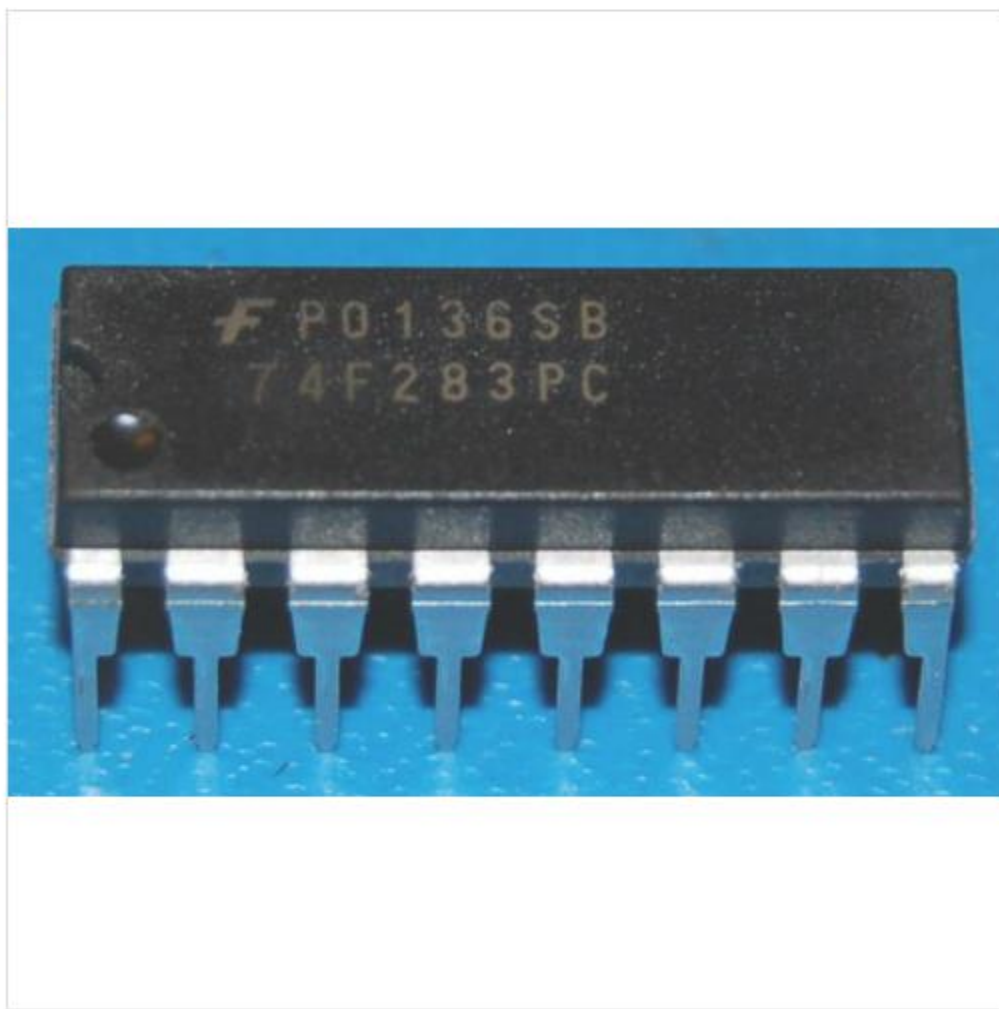74283 - 74F283N 4-Bit Binary Full Adder w/ Fast Carry, DIP-16



C \$6.55
+ C \$4.89 Shipping

Get it by **Tue, Nov 10 - Tue, Nov 17** from Havre-aux-Maisons, QC, Canada

- **New** condition
- 30 day returns - Buyer pays return shipping |

[Return policy](#)
[Read seller's description](#)
[See details](#)

MONEY BACK GUARANTEE

Qty: 1


Buy It Now

Add to cart

Watch

Sold by
[vedge23](#) (3476)
100.0% Positive feedback
[Contact seller](#)


Carry Propagation

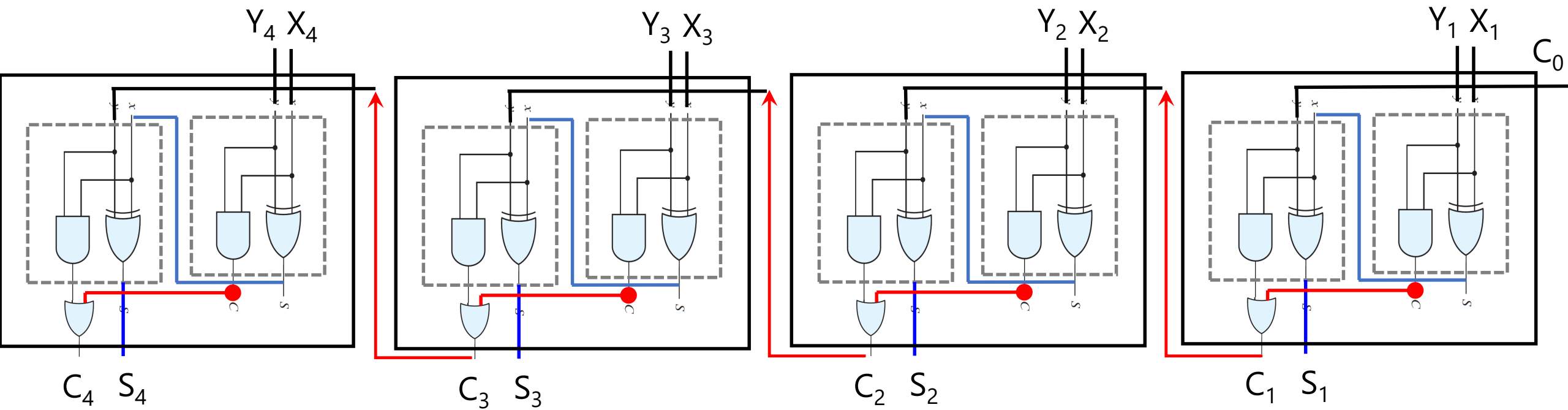

If gate delay is Δt , how long does it take to see the $S = S_4 S_3 S_2 S_1$?



$$S_4: 2 \times \Delta t + C_2$$

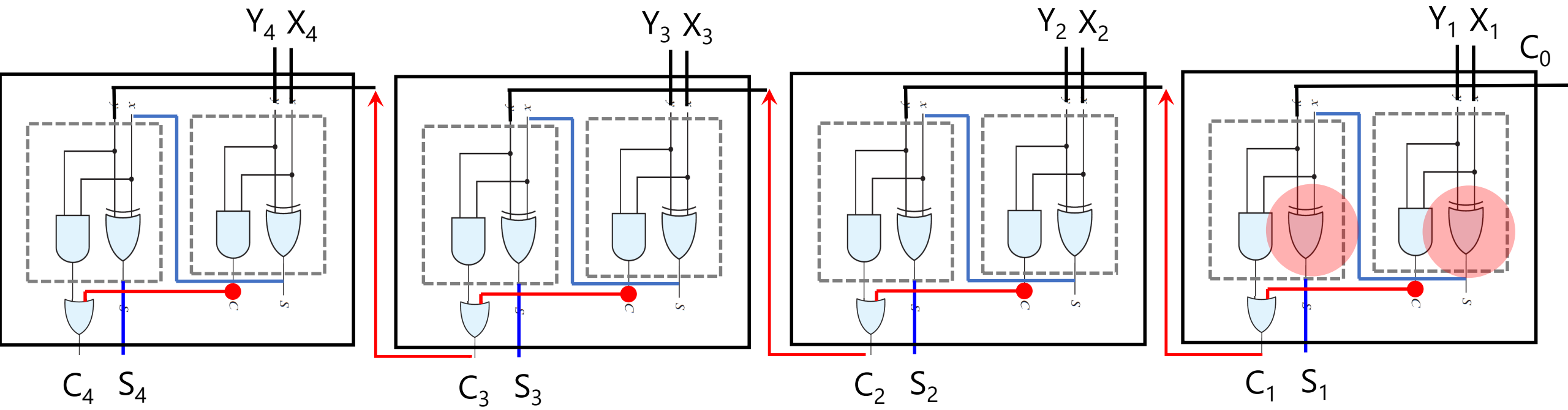

If gate delay is Δt , how long does it take to see the $S = S_4 S_3 S_2 S_1$?


$$S_1: 2 \times \Delta t$$

$$S_2: 2 \times \Delta t + C_1$$

$$S_3: 2 \times \Delta t + C_2$$

$$S_4: 2 \times \Delta t + C_3$$

In parallel

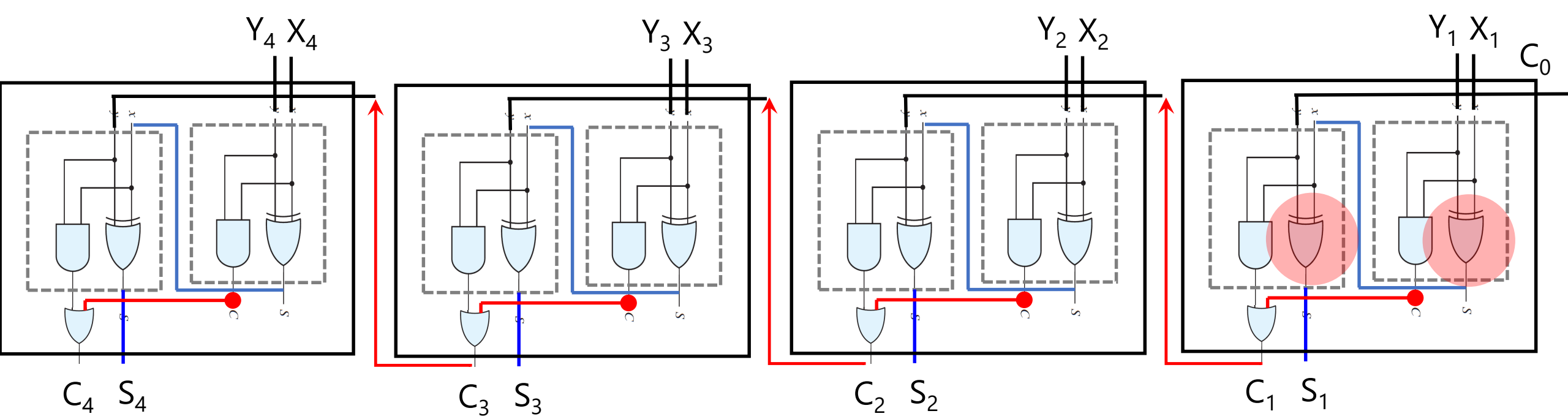

If gate delay is Δt , how long does it take to see the $S = S_4 S_3 S_2 S_1$?


$$S_1: 2 \times \Delta t$$

$$S_2: 2 \times \Delta t + C_1$$


$$S_3: 2 \times \Delta t + C_2$$

$$S_4: 2 \times \Delta t + C_3$$


In parallel

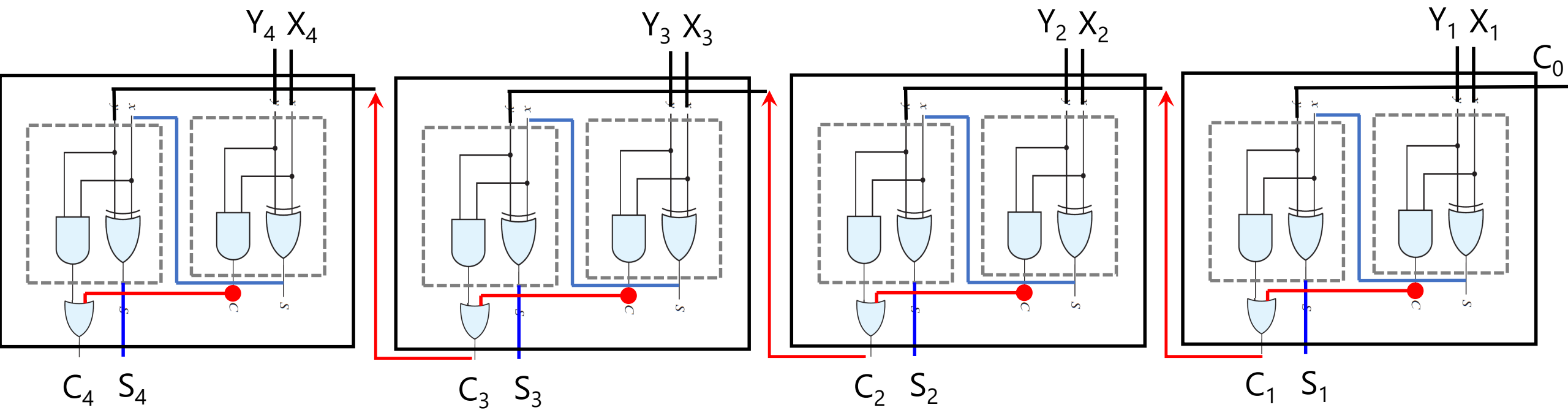

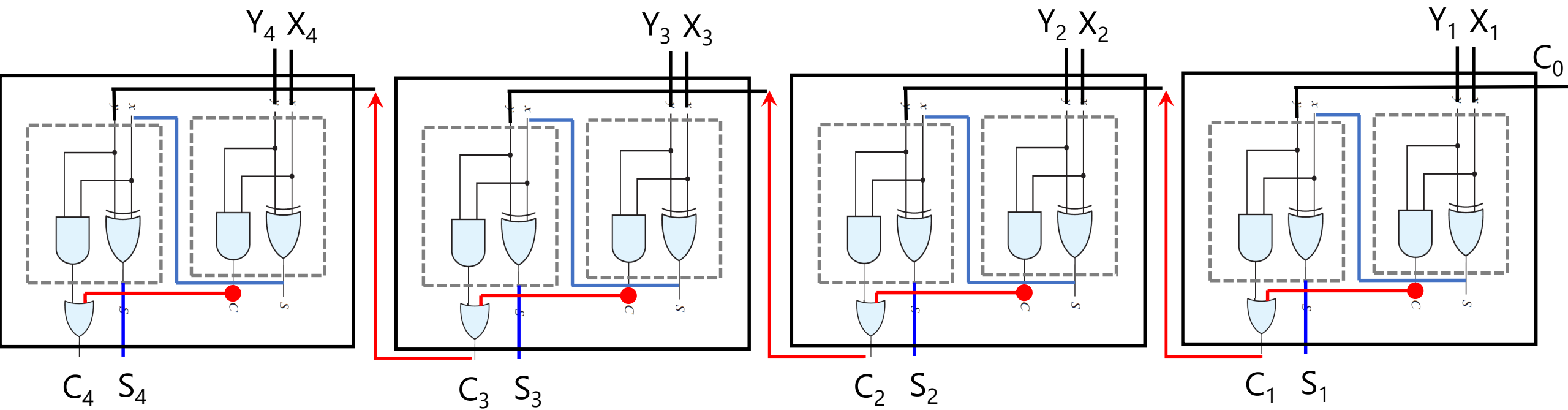If gate delay is Δt , how long does it take to see the $S = S_n \dots S_3 S_2 S_1$?



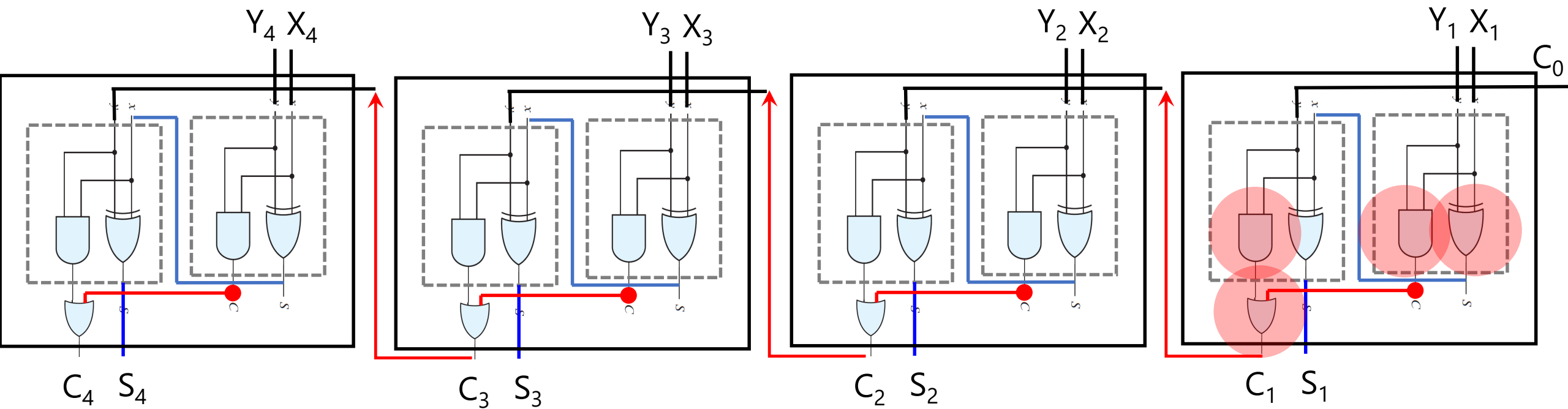
If gate delay is Δt , how long does it take to see the C_4 ?



If gate delay is Δt , how long does it take to see the C_4 ?

$$C_1 = Y_1 X_1 + C_0 (Y_1 \oplus X_1)$$


AND and XOR can be done in parallel.

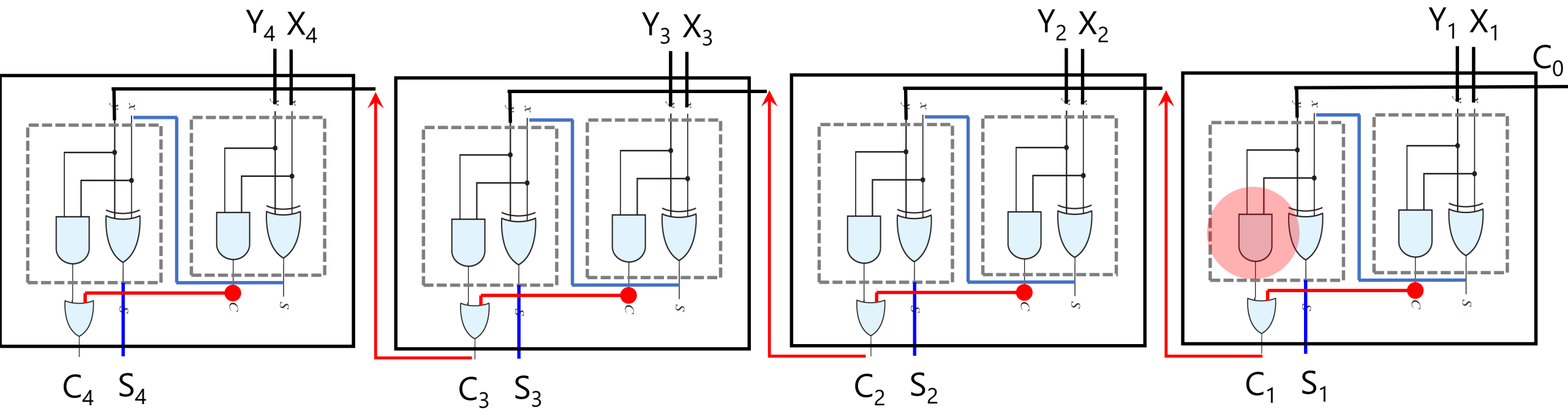

If gate delay is Δt , how long does it take to see the C_4 ?

$$C_1 = Y_1 X_1 + C_0 (Y_1 \oplus X_1) \rightarrow 1 \times \Delta t + 1 \times \Delta t$$


\uparrow
 C_0 AND

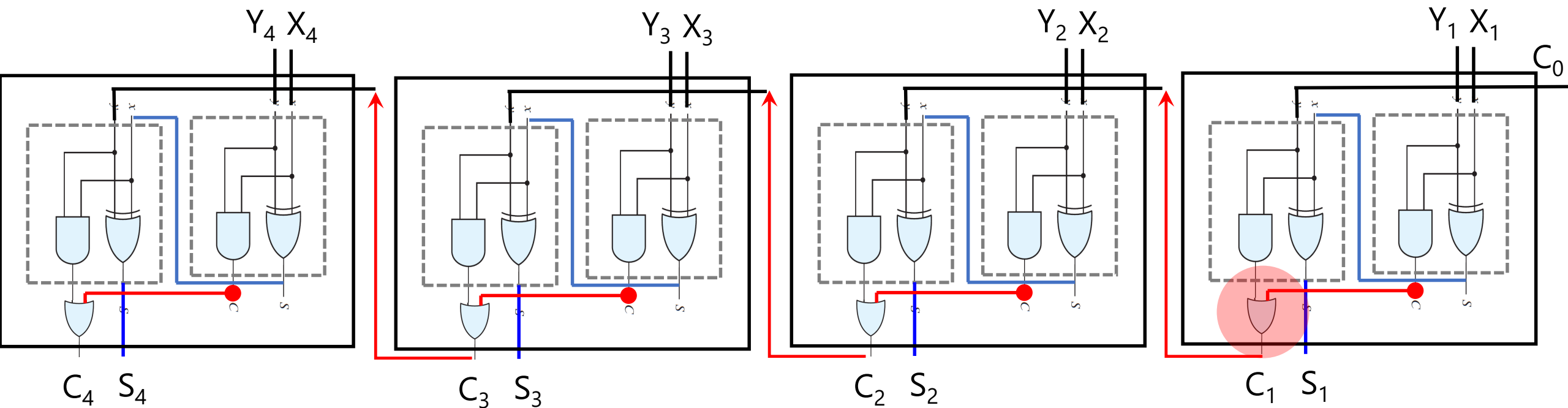

If gate delay is Δt , how long does it take to see the C_4 ?


$$C_1 = Y_1 X_1 + C_0 (Y_1 \oplus X_1) \rightarrow 1 \times \Delta t + 1 \times \Delta t + 1 \times \Delta t$$

↑
OR

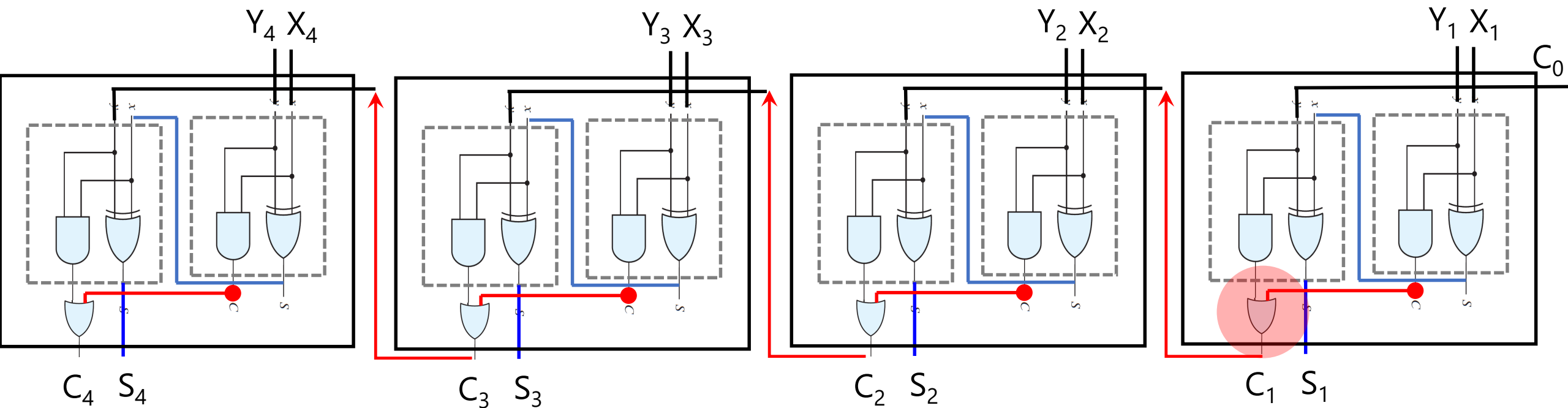

If gate delay is Δt , how long does it take to see the C_4 ?
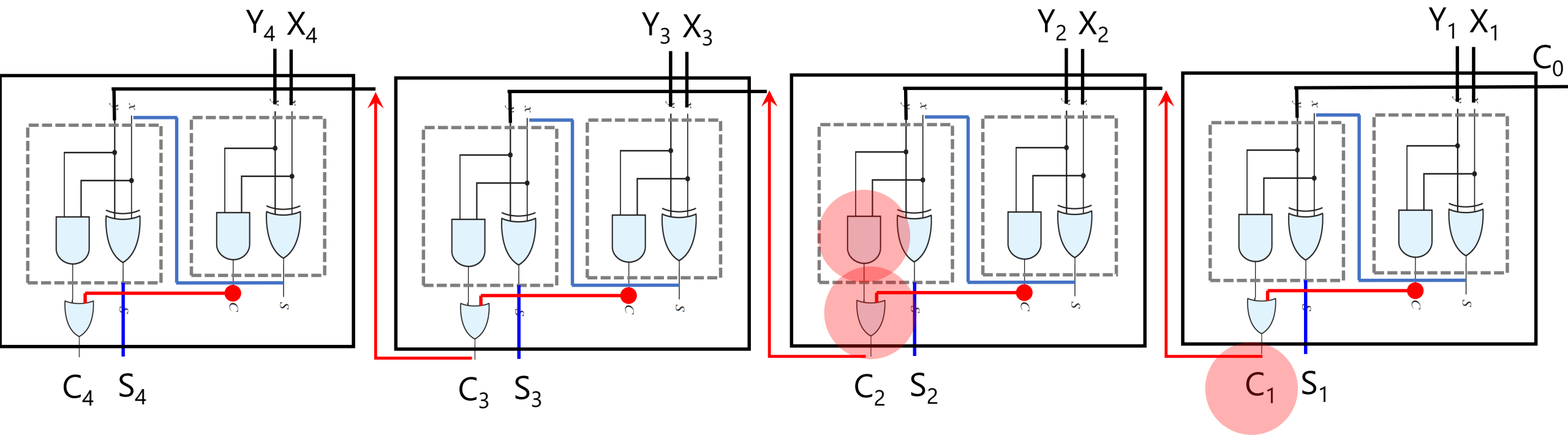
$$C_1 = Y_1 X_1 + C_0 (Y_1 \oplus X_1) \rightarrow 1 \times \Delta t + 1 \times \Delta t + 1 \times \Delta t = 3 \times \Delta t$$




If gate delay is Δt , how long does it take to see the C_4 ?

$$C_2 = Y_2 X_2 + C_1 (Y_2 \oplus X_2) \rightarrow C_1 + 2 \times \Delta t = 5 \times \Delta t$$

C_1 AND then OR

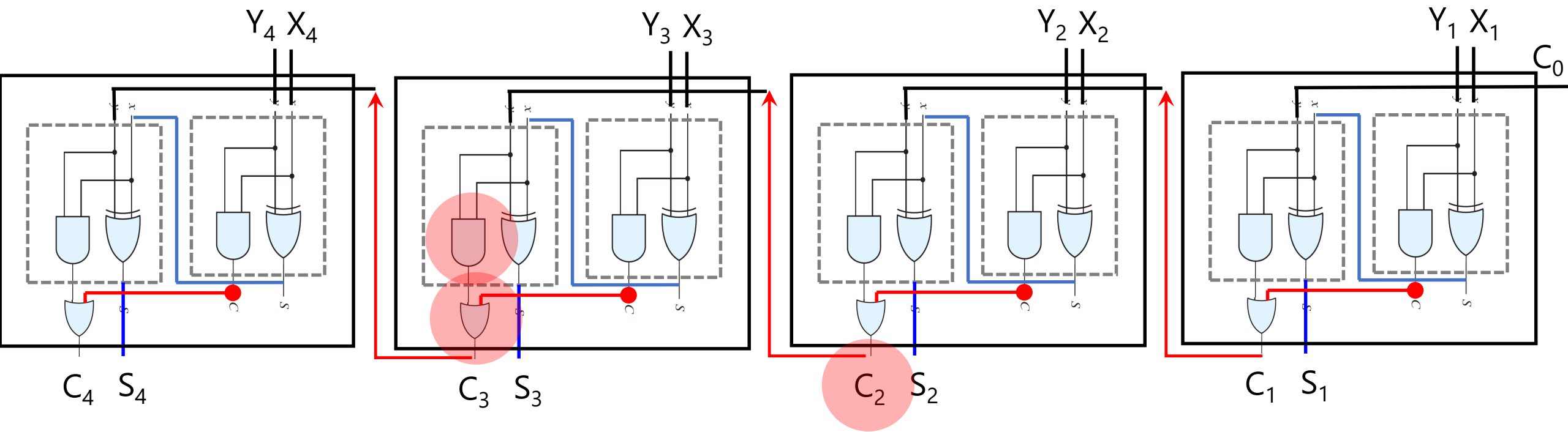
In the meantime, in parallel, we can do the $Y_2 X_2$ and $Y_2 \oplus X_2$



If gate delay is Δt , how long does it take to see the C_4 ?

$$C_3 = Y_3 X_3 + C_2 (Y_3 \oplus X_3) \rightarrow C_2 + 2 \times \Delta t = 7 \times \Delta t$$
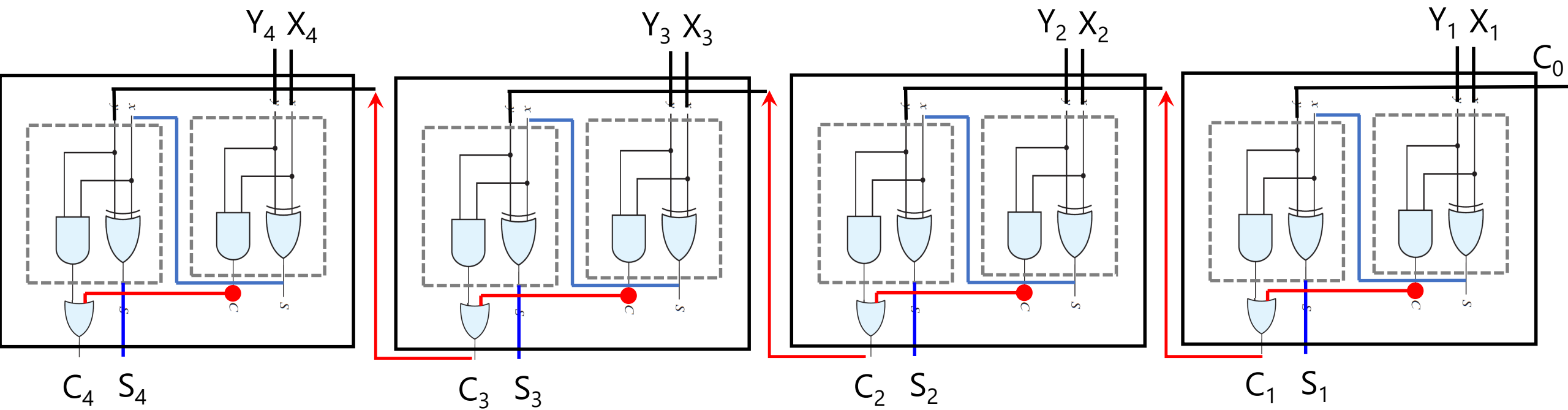
$$C_4 = Y_4 X_4 + C_3 (Y_4 \oplus X_4) \rightarrow C_3 + 2 \times \Delta t = 9 \times \Delta t$$



If gate delay is Δt , how long does it take to see the C_n ?

Carry Lookahead

$C_{1:n} \rightarrow$ Constant Delay
Book Page 138-141

Binary Adder

Does it matter we have **signed** or **unsigned** binary numbers?
Justify your answer.

Binary Subtractor

Signed-2's-Complement

$$X - Y$$

Subtraction in Signed-2's-Complement

$$X_n X_{n-1} \dots X_2 X_1 - Y_n Y_{n-1} \dots Y_2 Y_1$$

Subtraction in Signed-2's-Complement

$$X + 2's\text{-comp}(Y)$$

Subtraction in Signed-2's-Complement

$$X + 1's\text{-comp}(Y) + 1$$

Subtraction in Signed-2's-Complement


bitwise




$$X + Y' + 1$$


Subtraction in Signed-2's-Complement


bitwise

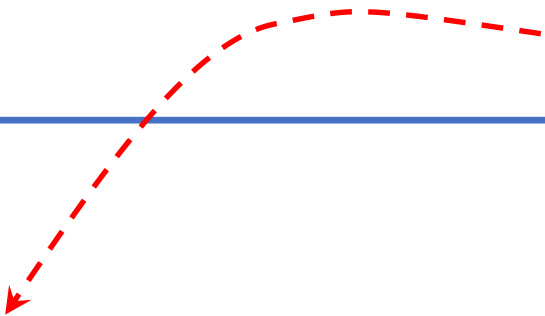

$$X + Y' + (C_0 = 1)$$

Subtraction in Signed-2's-Complement

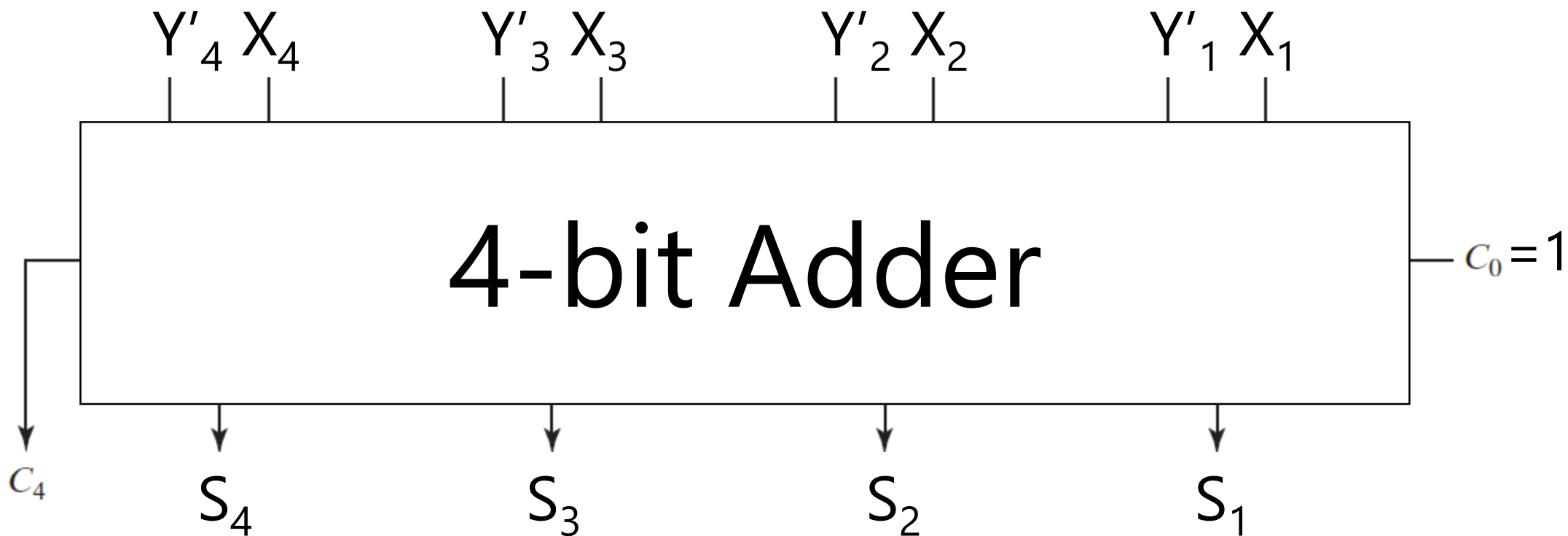

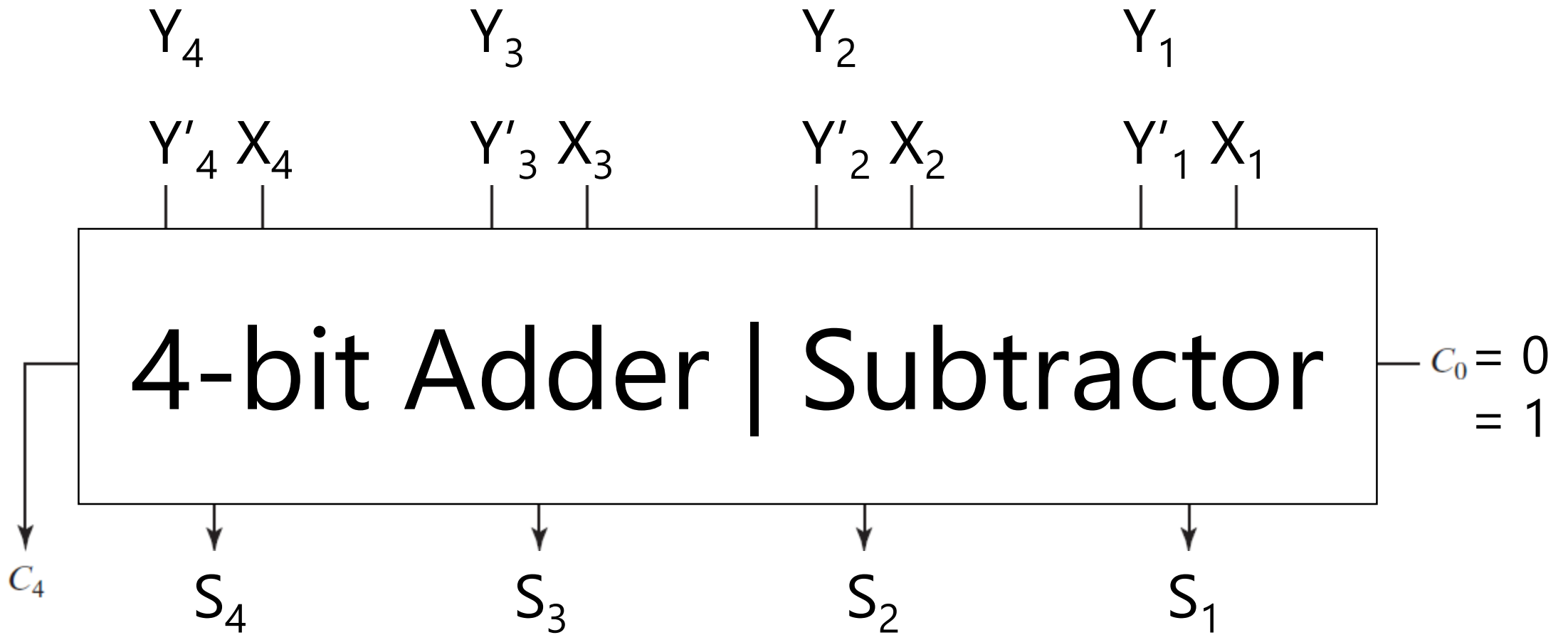

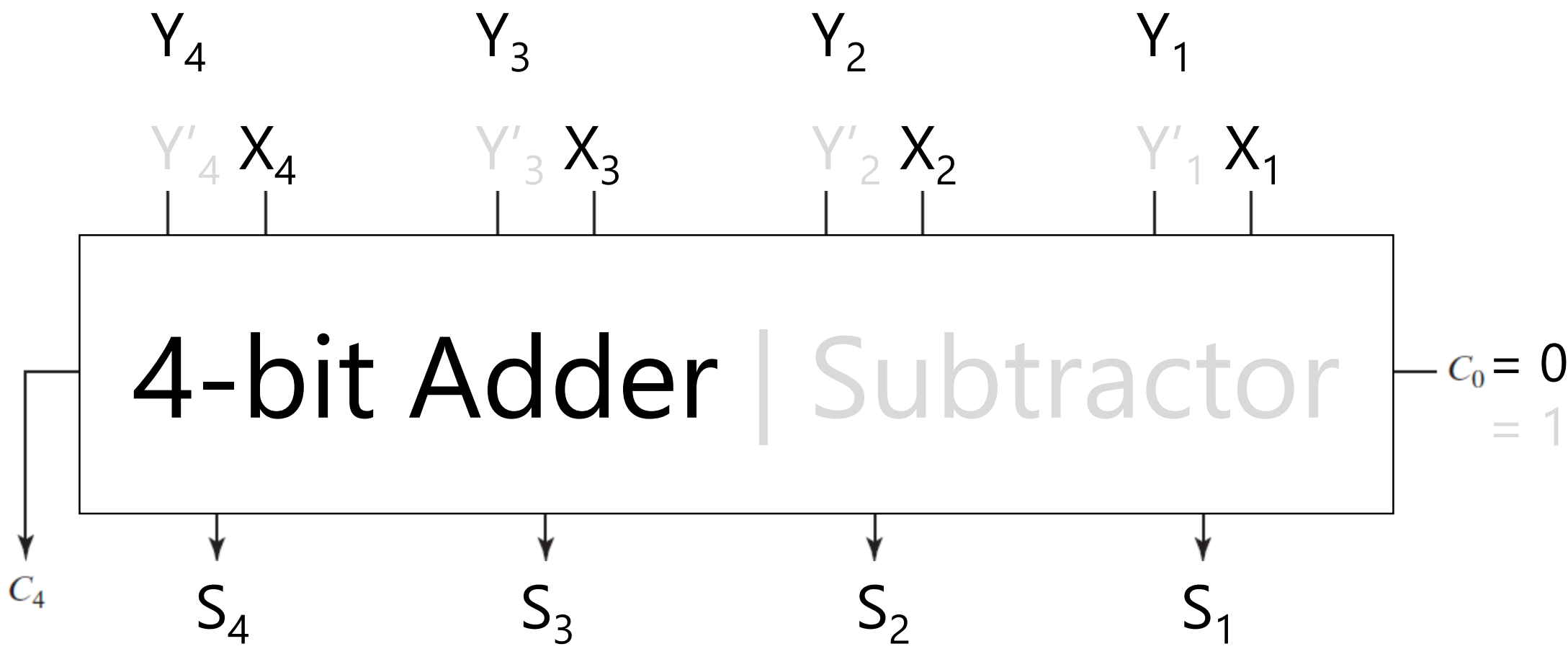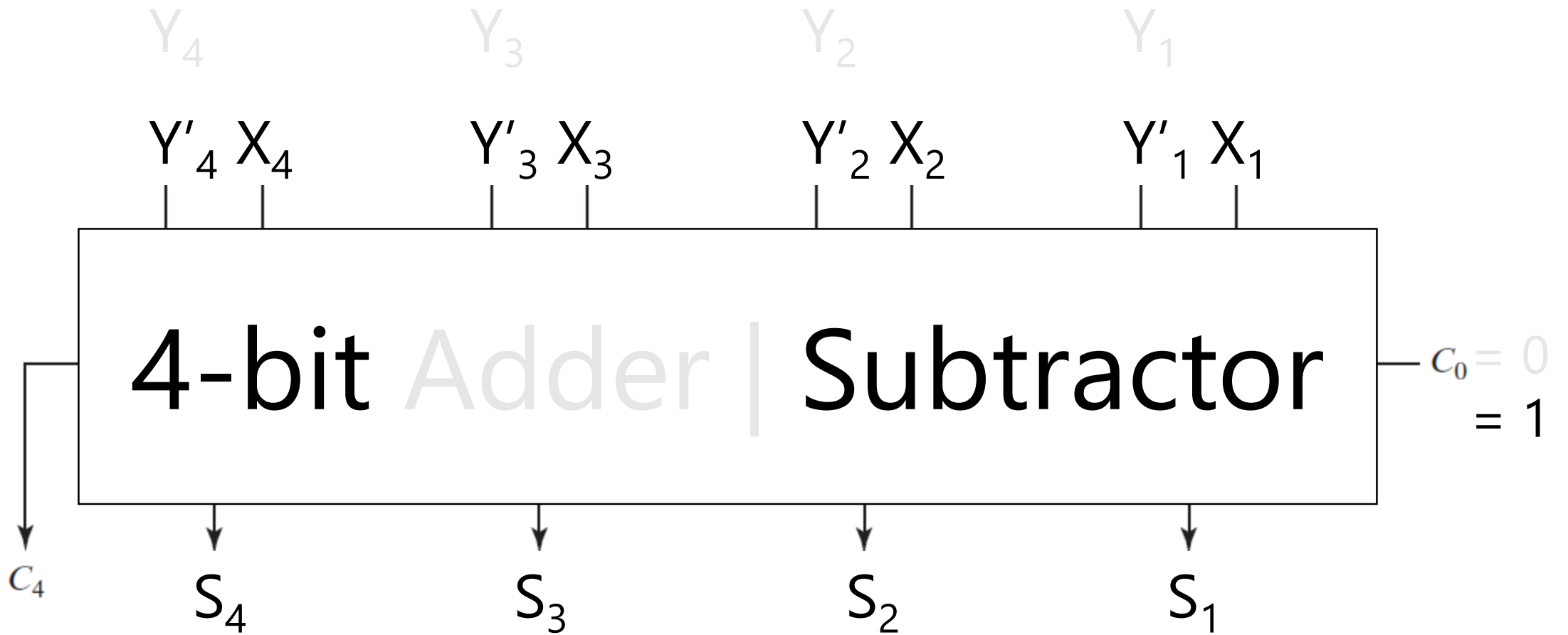




$$A ? 0 = A$$

$$A ? 1 = A'$$


$$A \oplus 0 = A$$

$$A \oplus 1 = A'$$

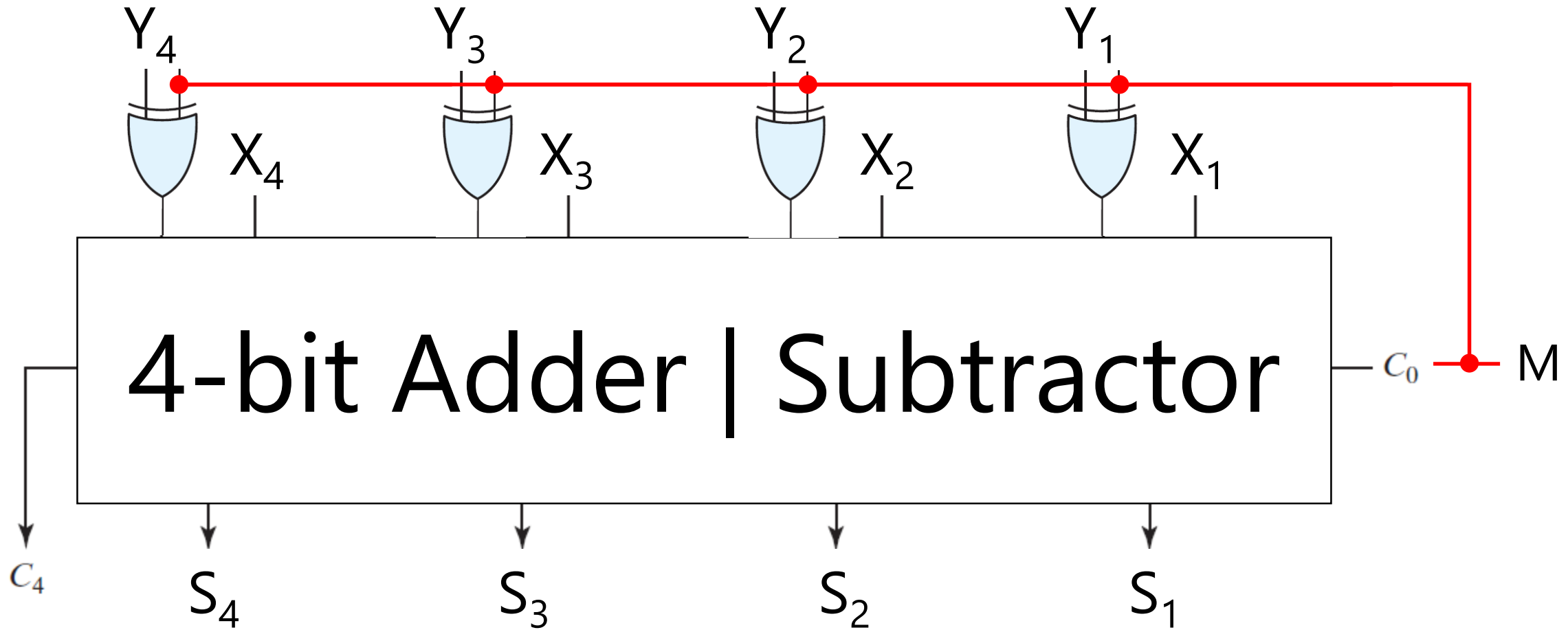

$M=0 \rightarrow$ Adder

$M=1 \rightarrow$ Subtractor

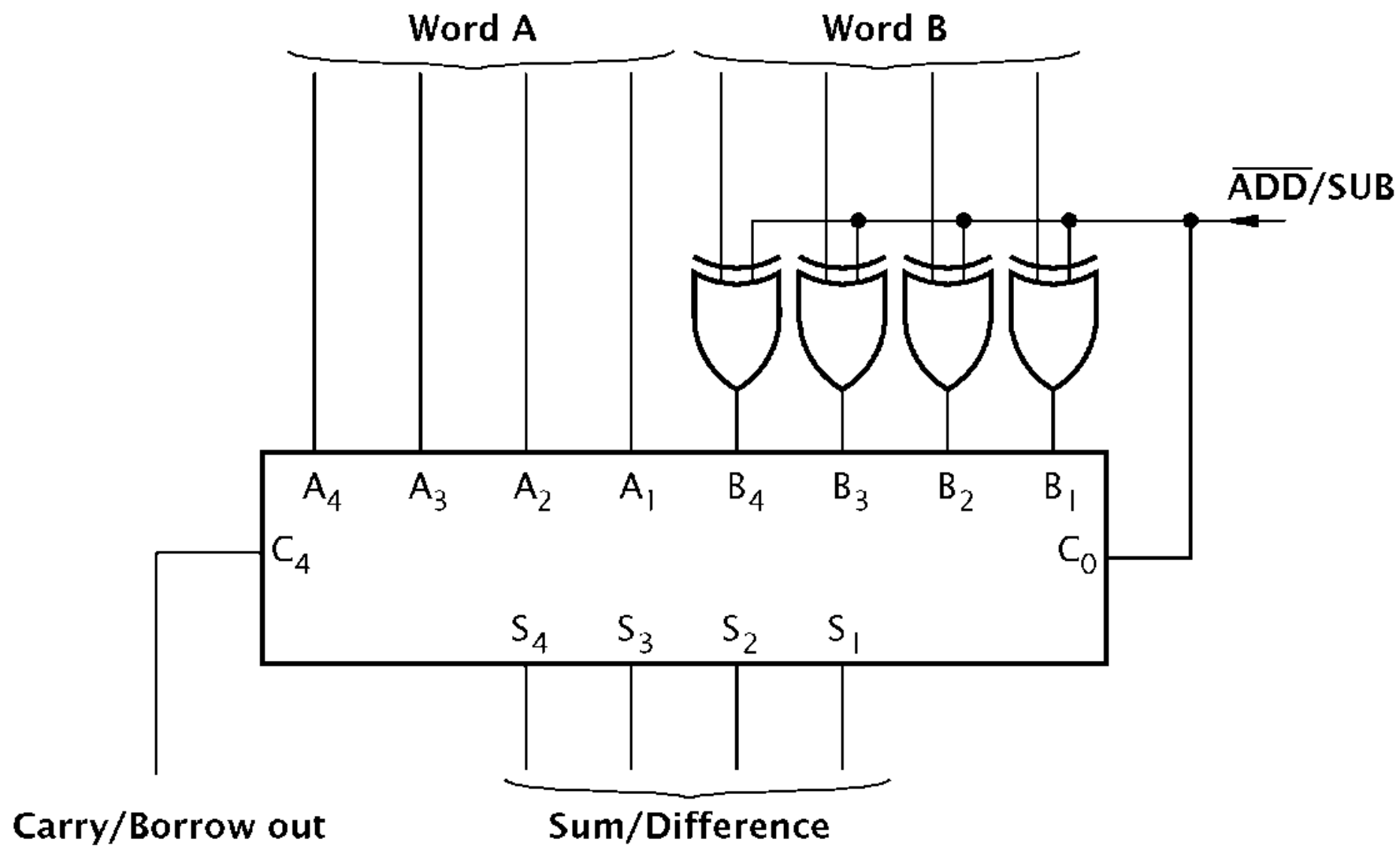

Binary Subtractor

Unsigned?

Overflow

Signed-2's-Complement
