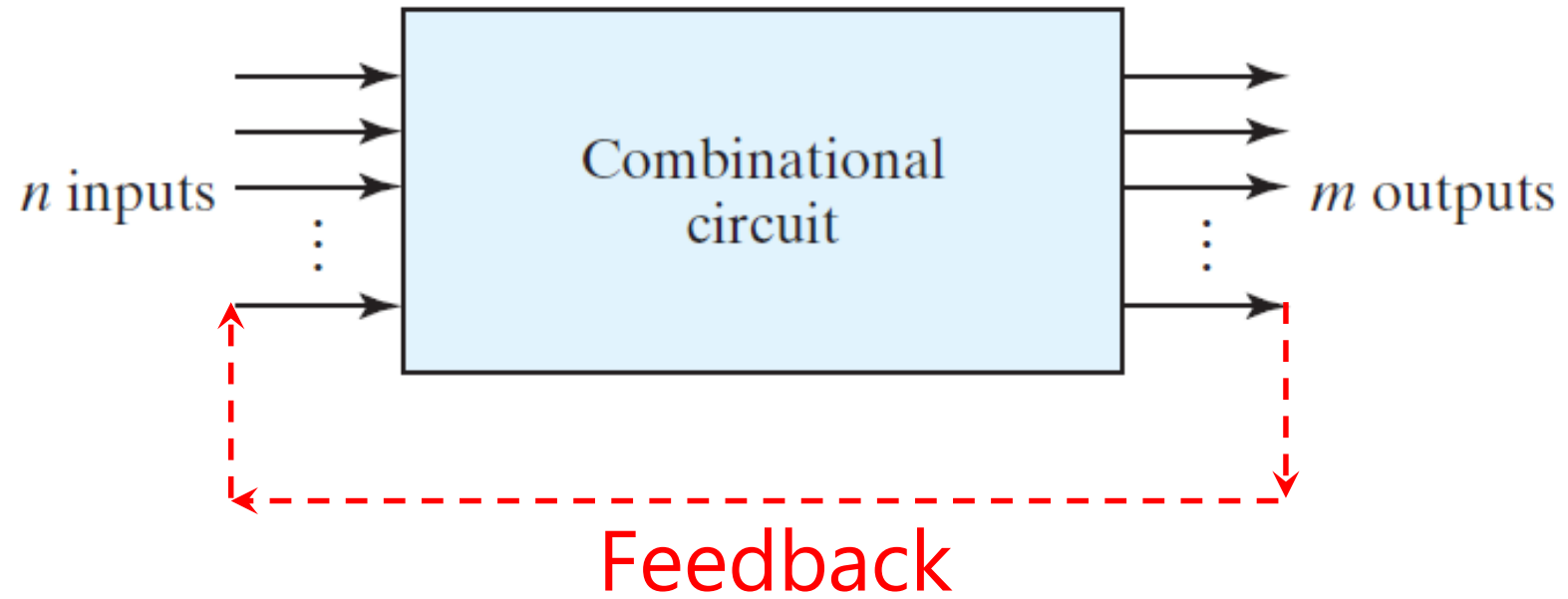




Sequential Logic



Sequential Logic





Voltage

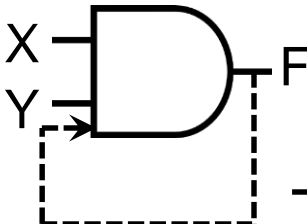
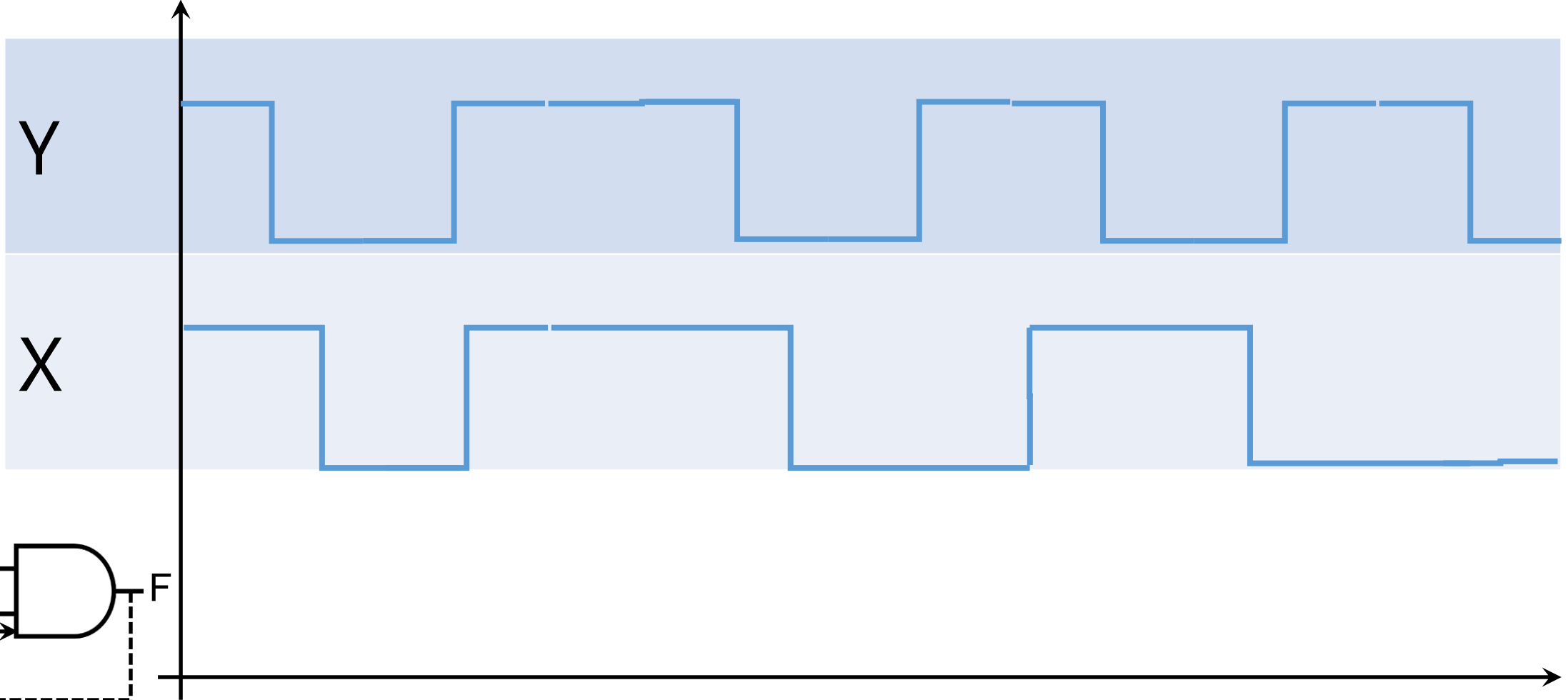


Time

Voltage

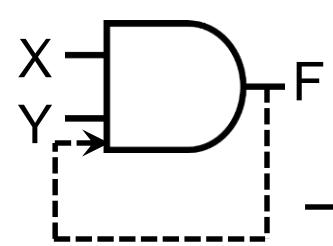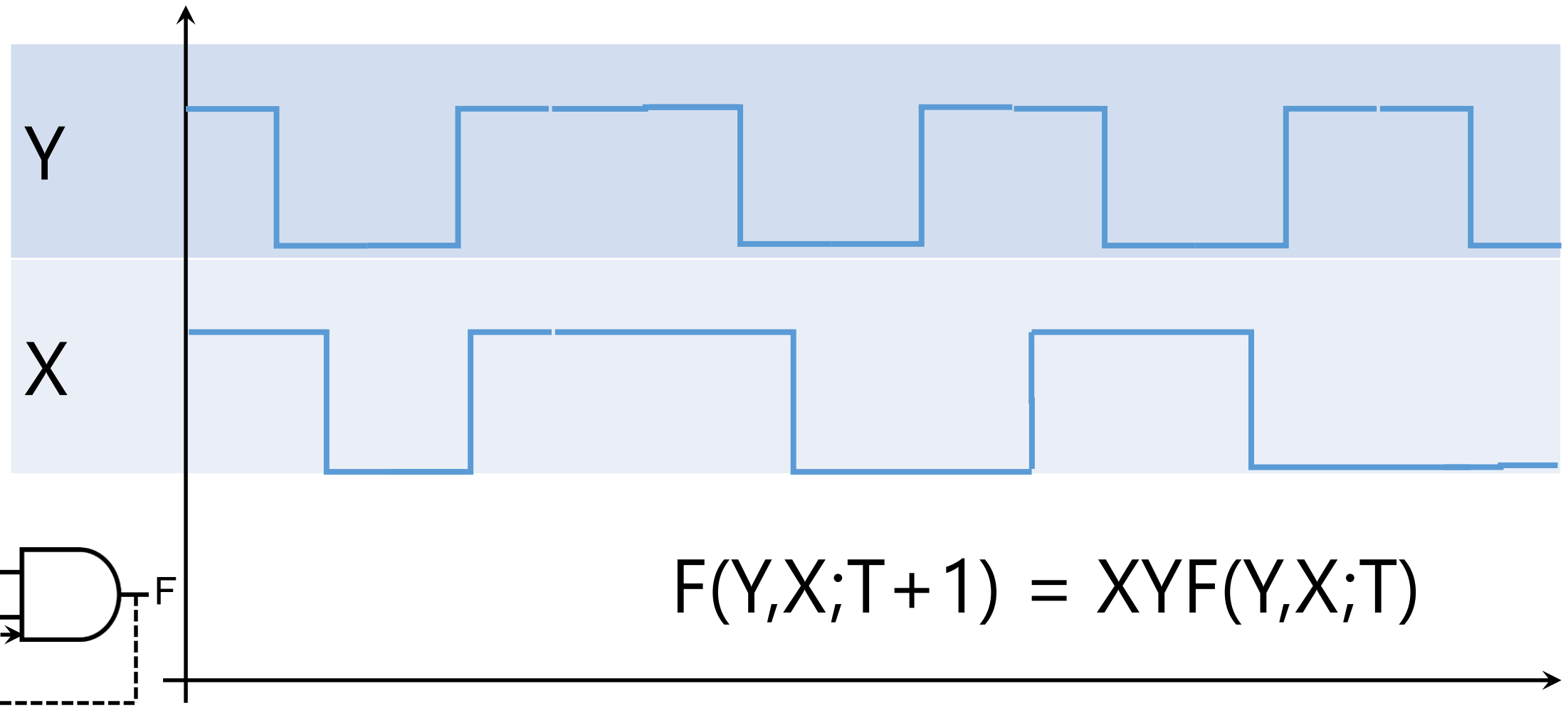

Voltage

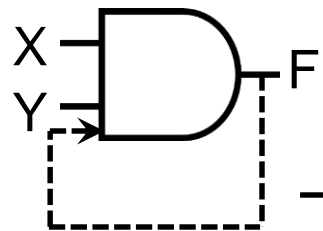
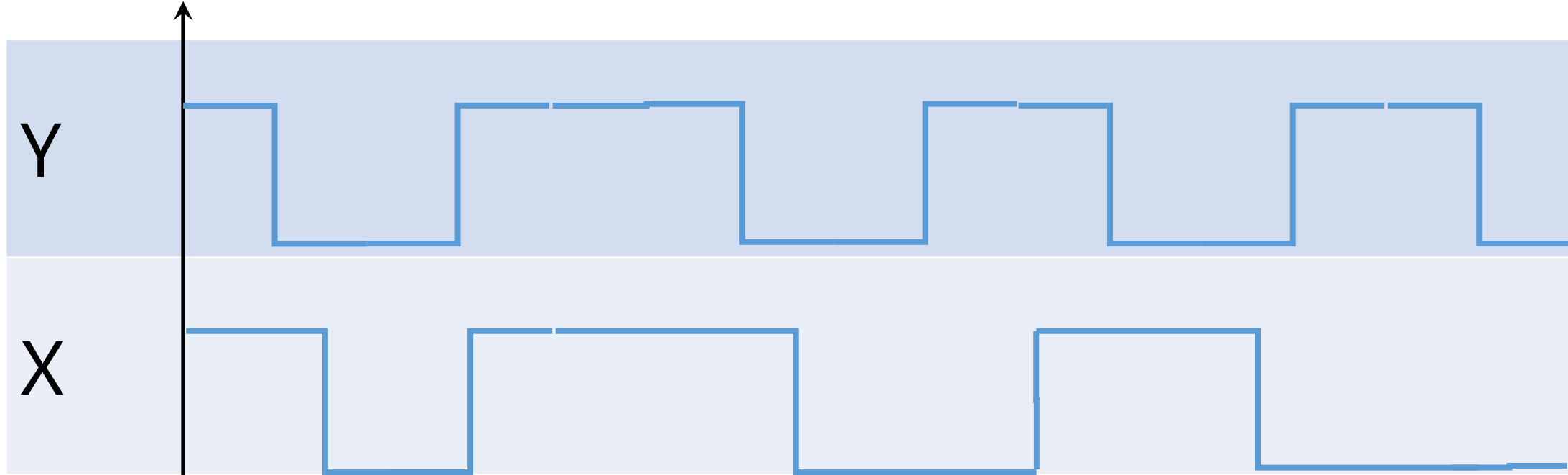


$$F(Y,X;T+1) = XYF(Y,X;T) ; F(Y,X;0) = 0$$

by default in positive logic

Time



Voltage

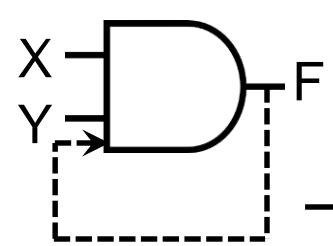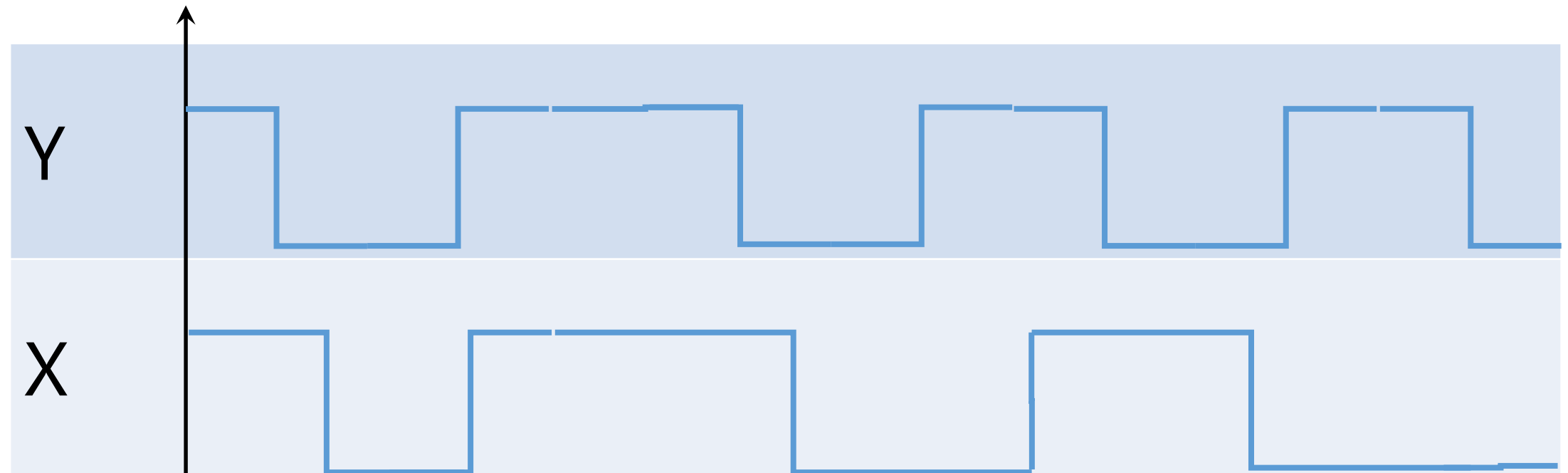

$$F(Y,X;T+1) = XYF(Y,X;T) ; F(Y,X;0) = 0$$




Voltage

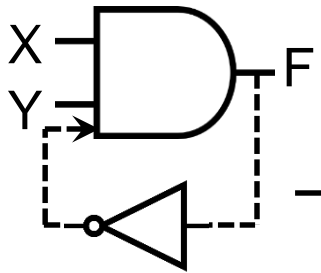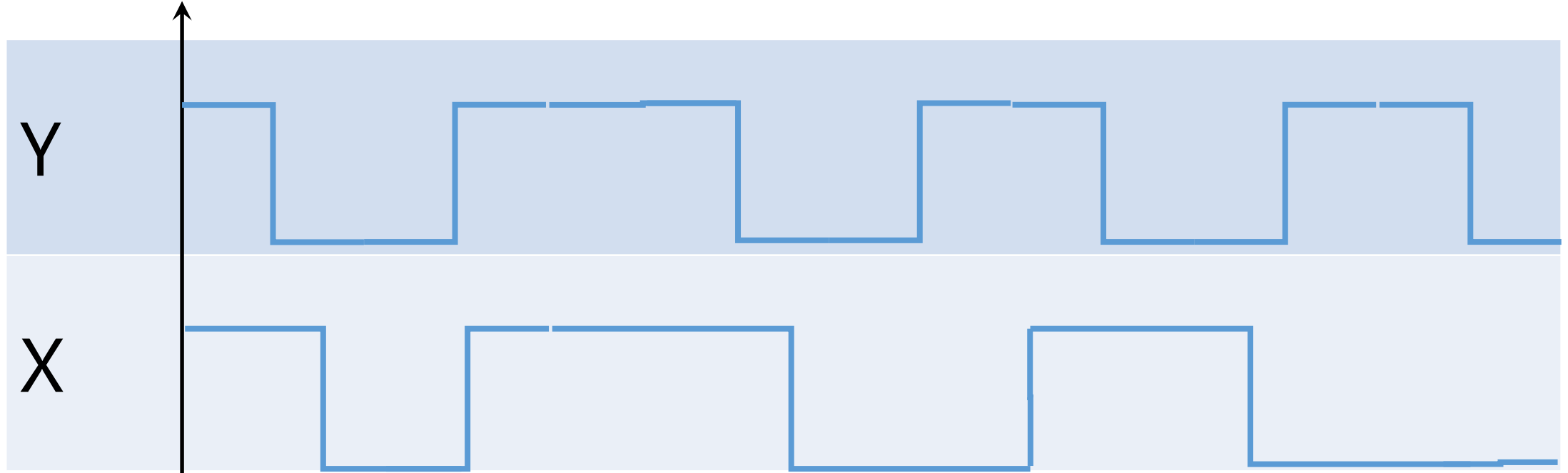


Time

$$F(Y,X;T+1) = XYF'(Y,X;T) ; F(Y,X;0) = 0$$

Voltage

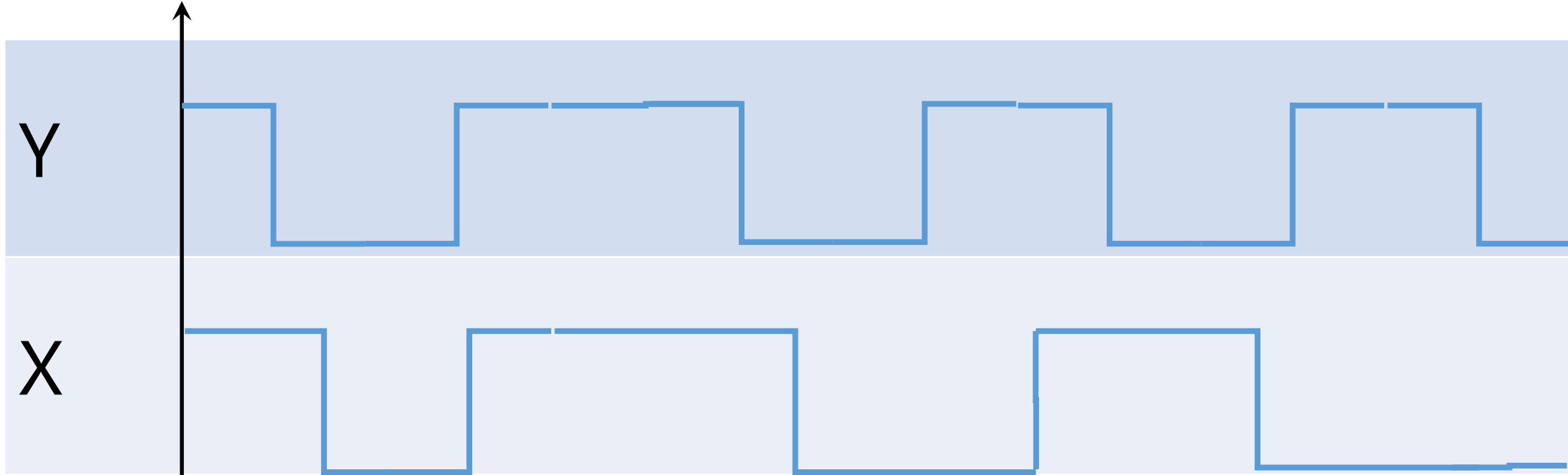


$\Delta t: XYF'(0)=110'=111=1$

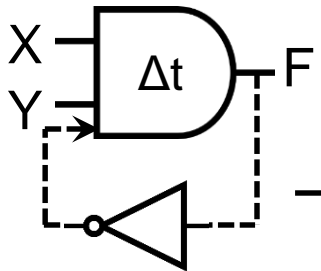


Time

$$F(Y,X;T+1) = XYF'(Y,X;T) ; F(Y,X;0) = 0$$

Voltage

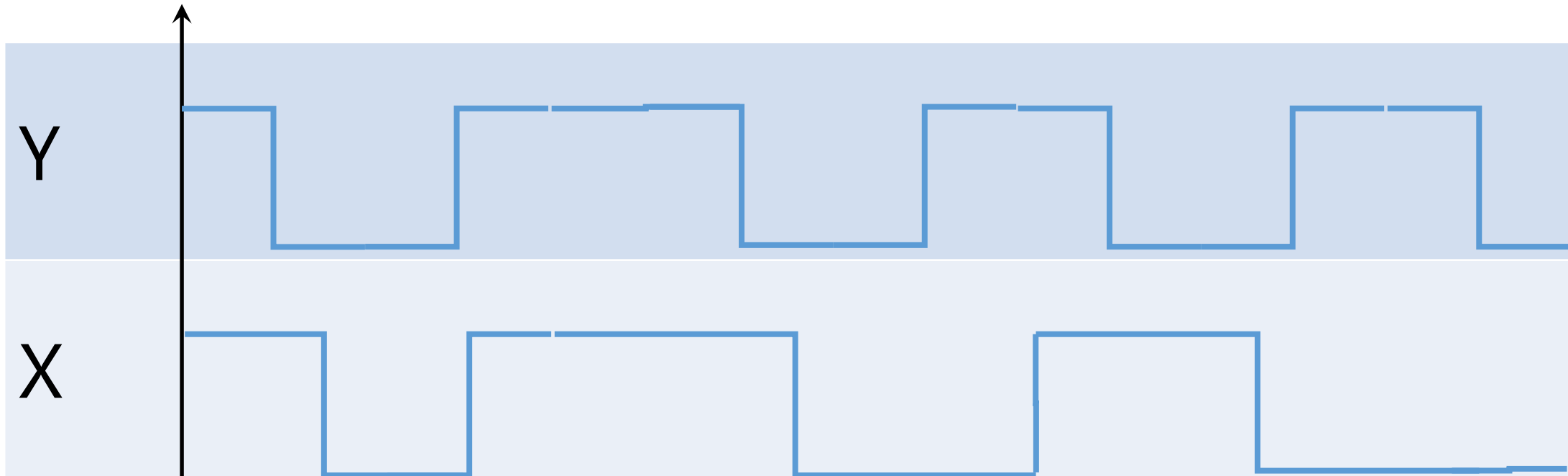

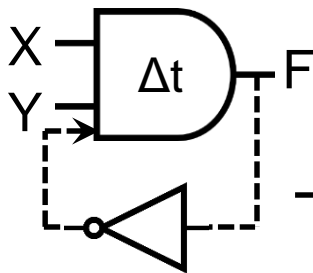
$2 \times \Delta t$: $XYF'_1 = 111' = 110 = 0$




Time

$$F(Y, X; T+1) = XYF'(Y, X; T) ; F(Y, X; 0) = 0$$

Voltage

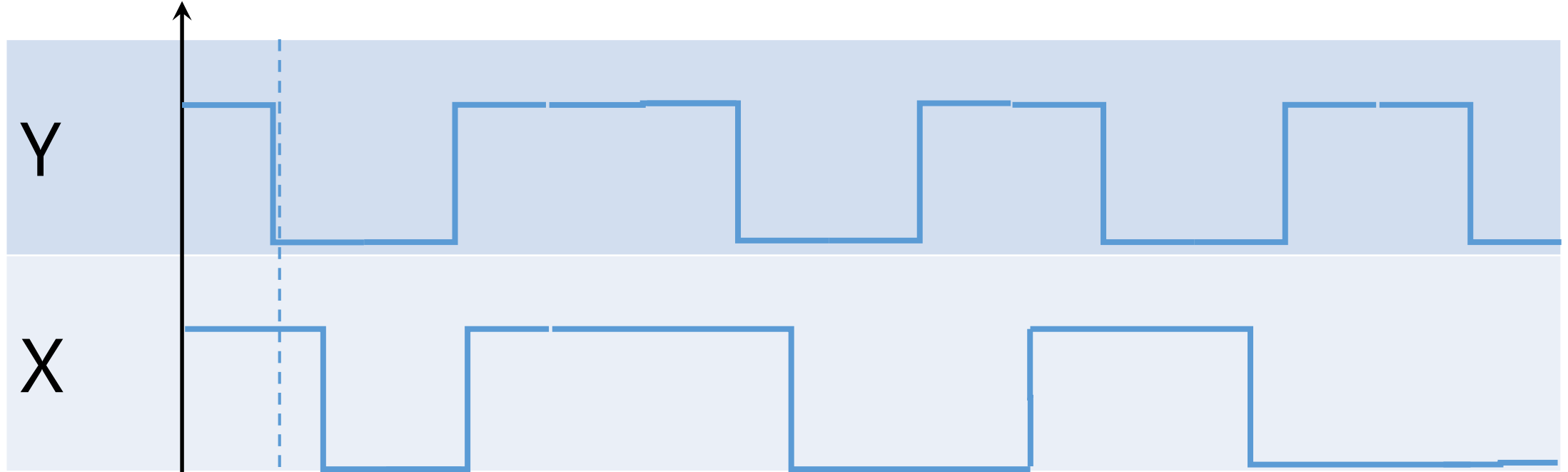

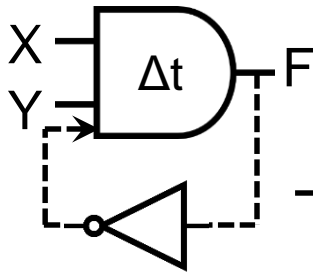
$3 \times \Delta t: XYF'_2 = 100' = 101 = 0$




Time

$$F(Y, X; T+1) = XYF'(Y, X; T) ; F(Y, X; 0) = 0$$

Voltage

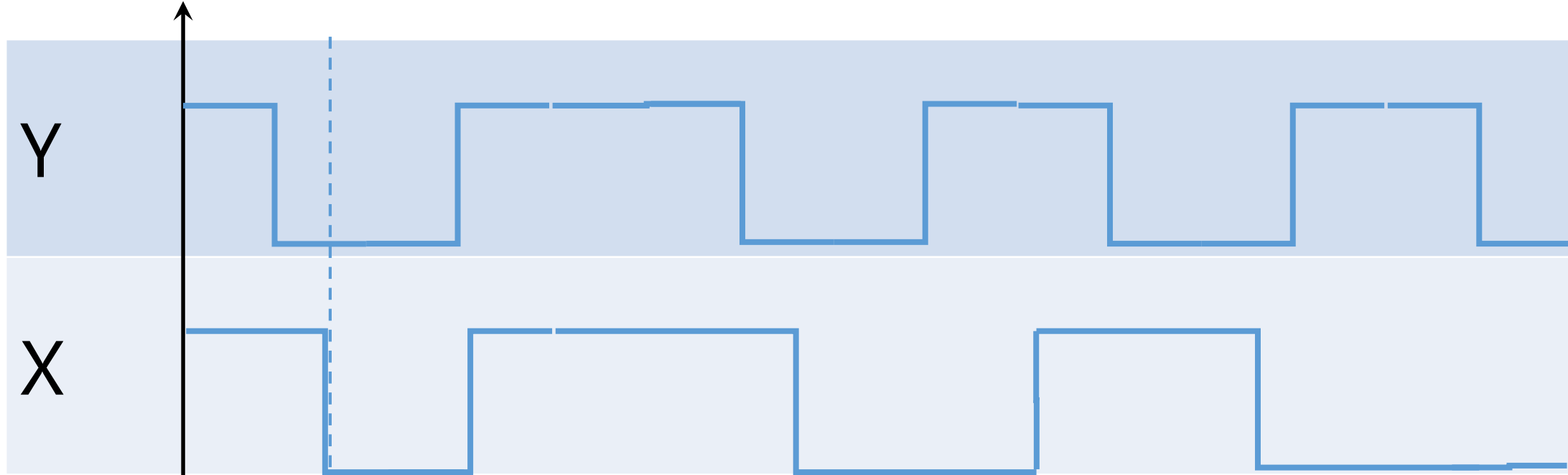

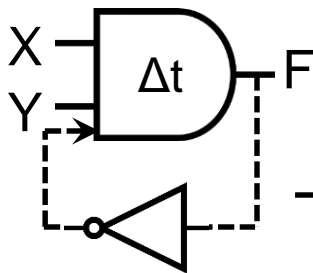
$4 \times \Delta t: XYF'_3 = 000' = 001 = 0$



$$F(Y,X;T+1) = XYF'(Y,X;T) ; F(Y,X;0) = 0$$




Time

Voltage

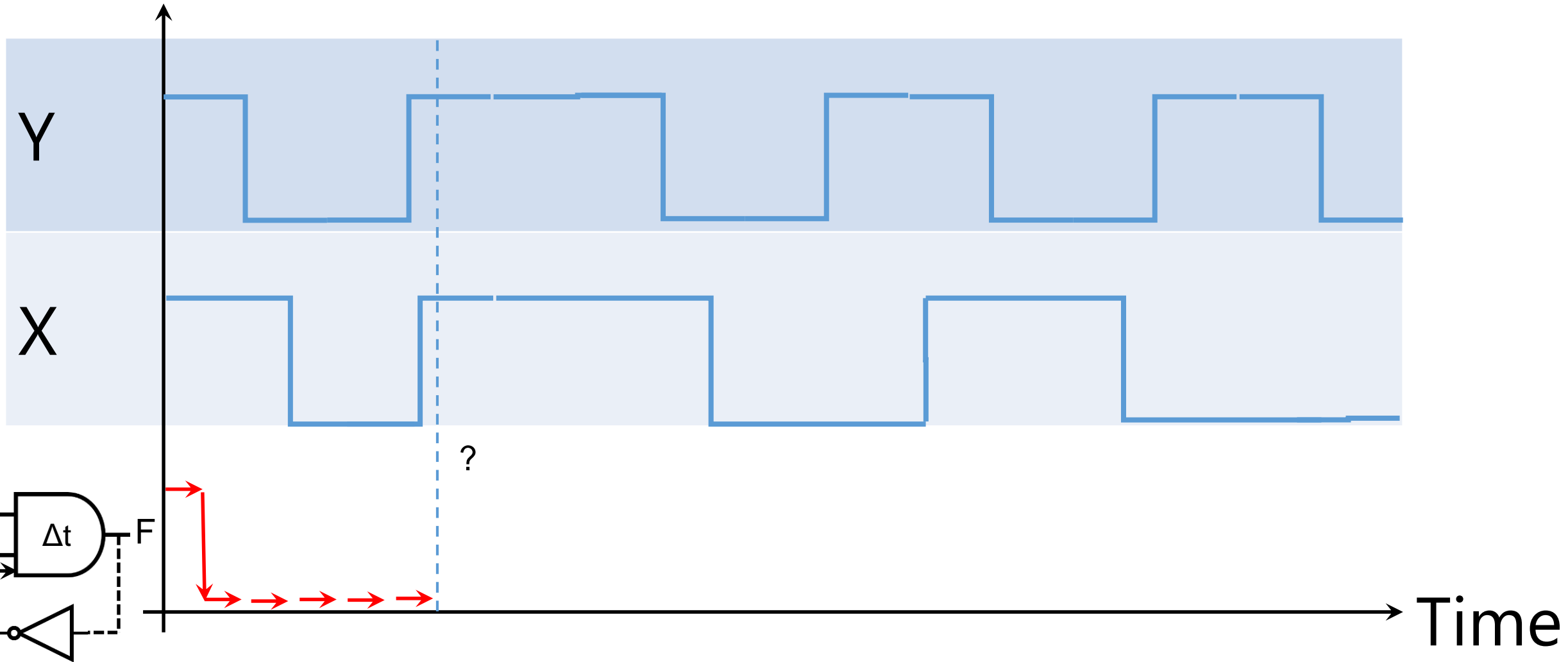


$$F(Y,X;T+1) = XYF'(Y,X;T) ; F(Y,X;0) = 0$$

Voltage

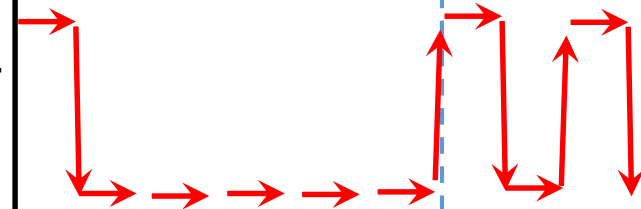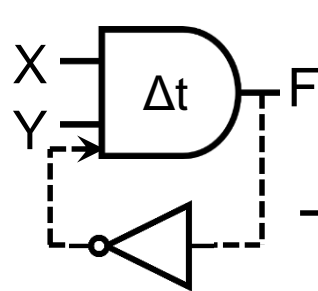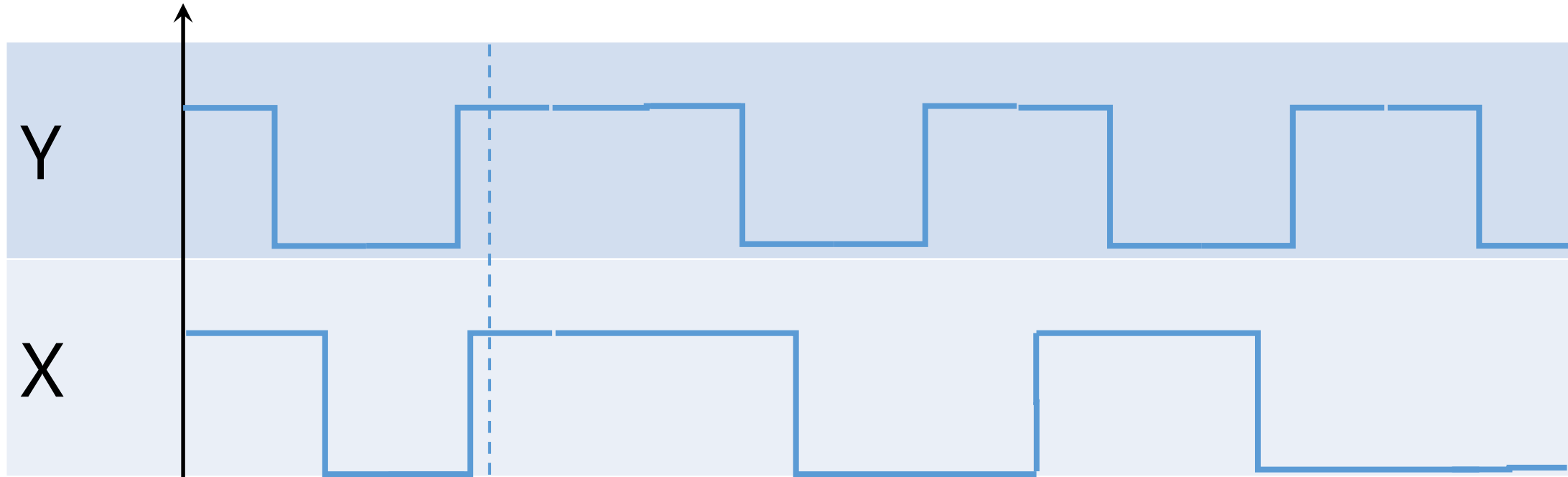


$$F(Y,X;T+1) = XYF'(Y,X;T) ; F(Y,X;0) = 0$$


Time

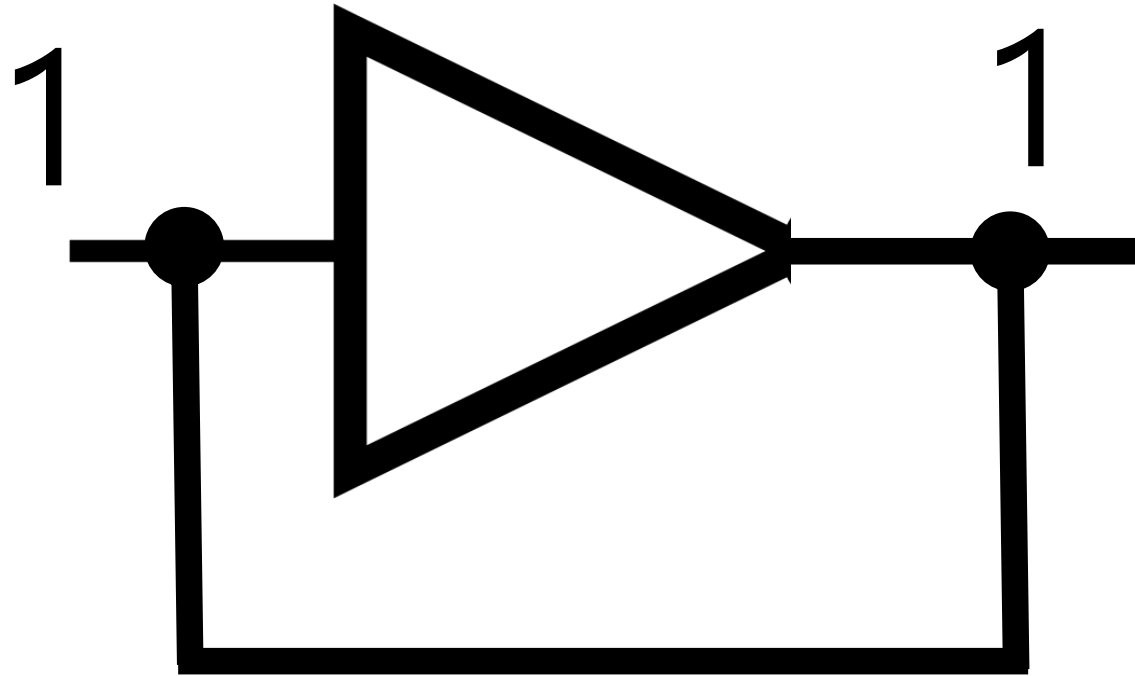


By feedback we can memorize 1

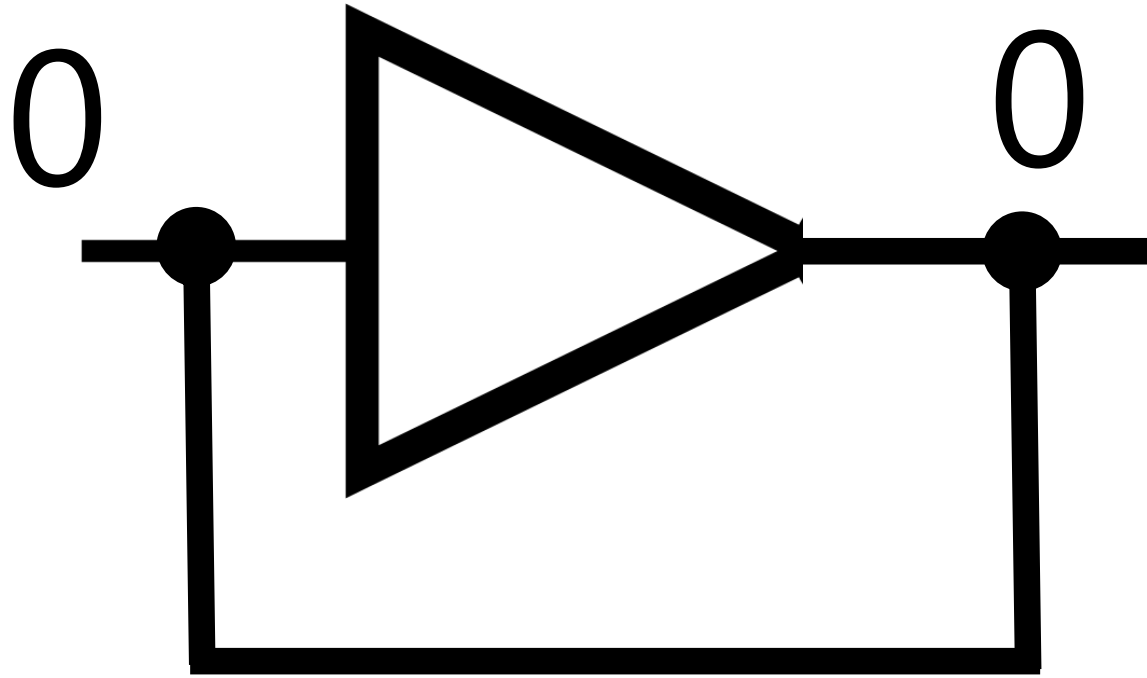

By feedback we can memorize 0

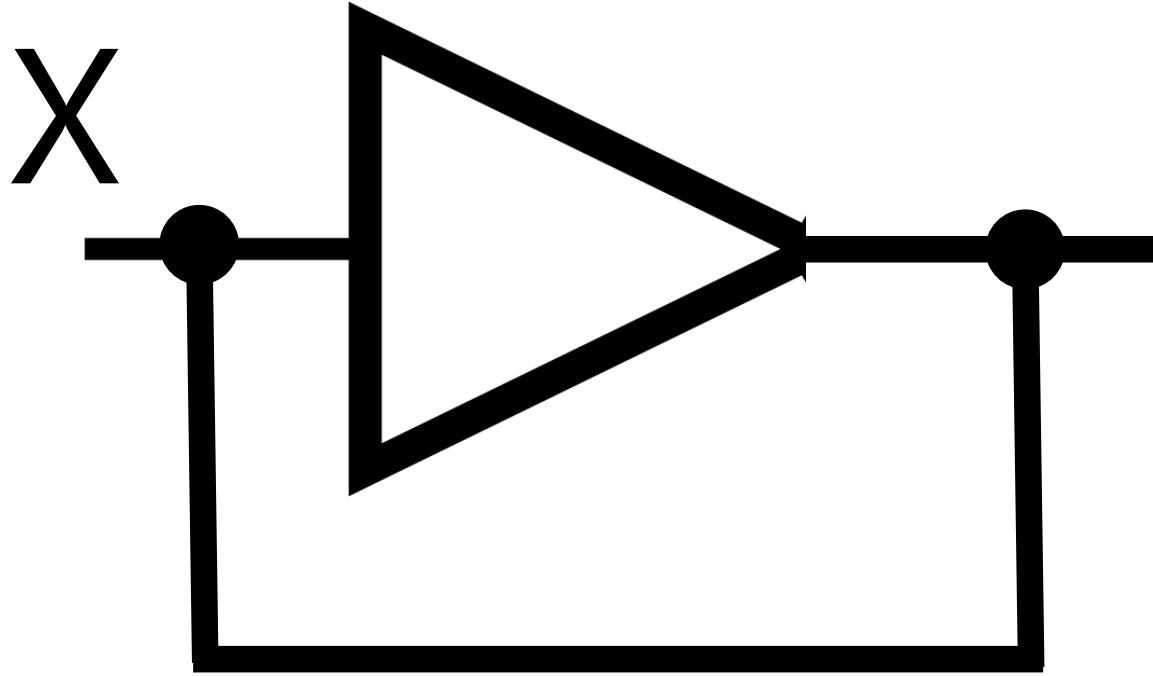

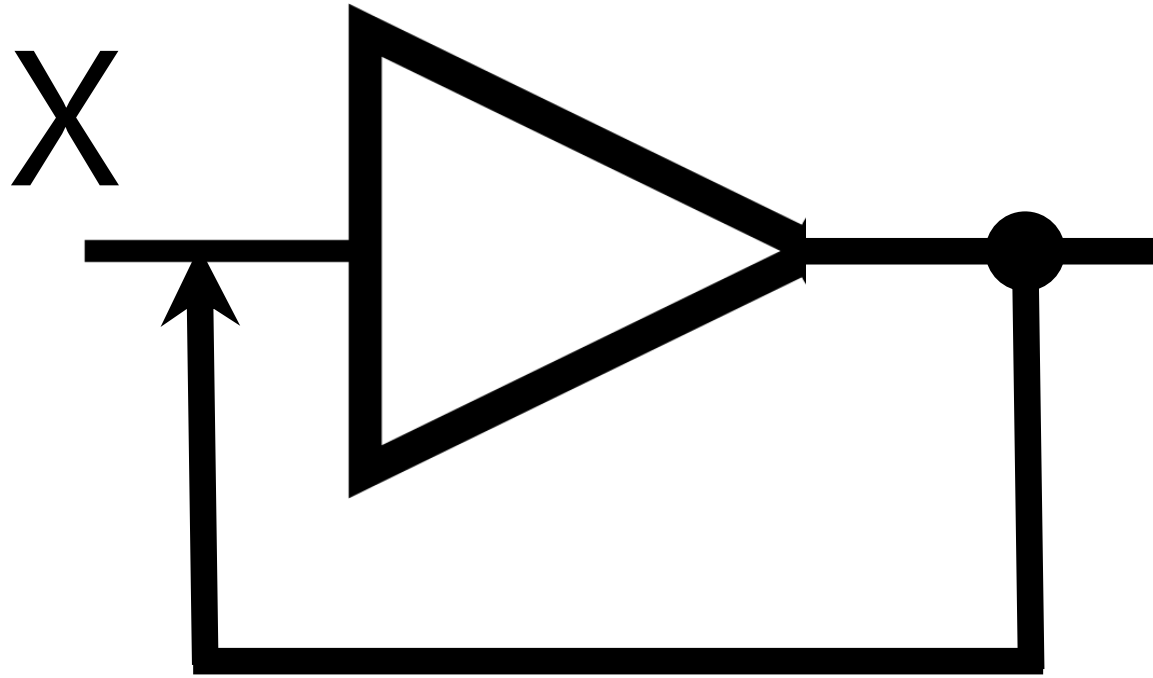
This design is logically **incorrect**! Why?




This design is logically **incorrect**! Why?

Buffer gate accepts one input.


We have two inputs: X and X_{T-1}

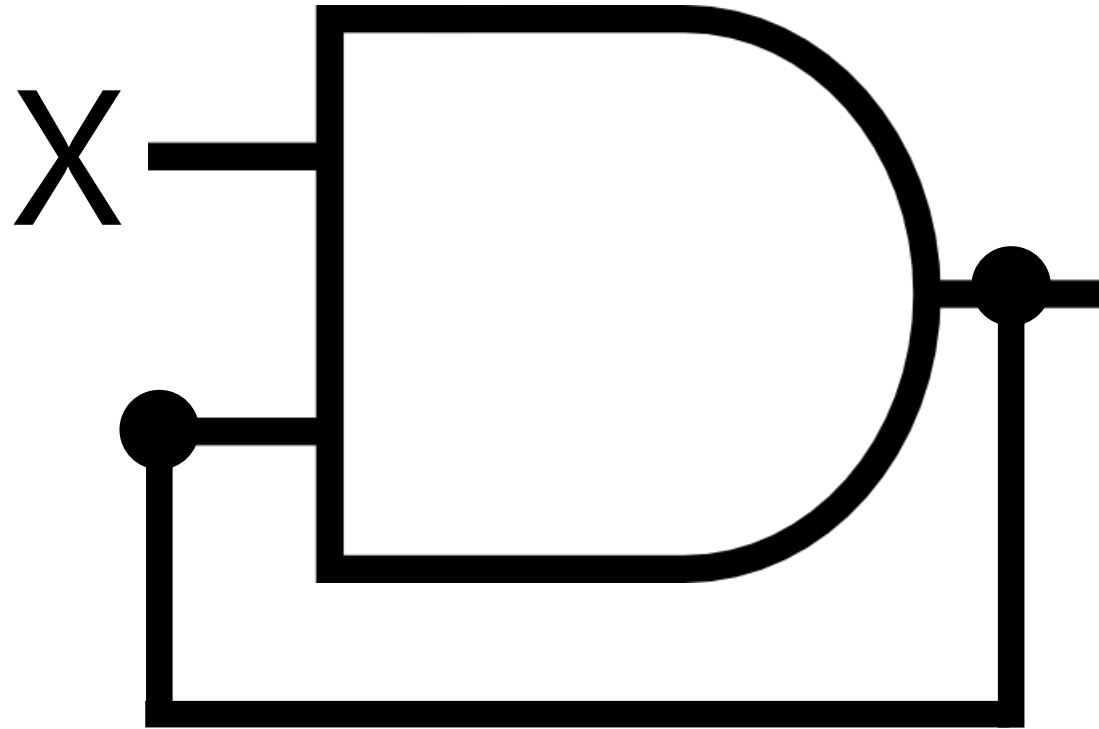


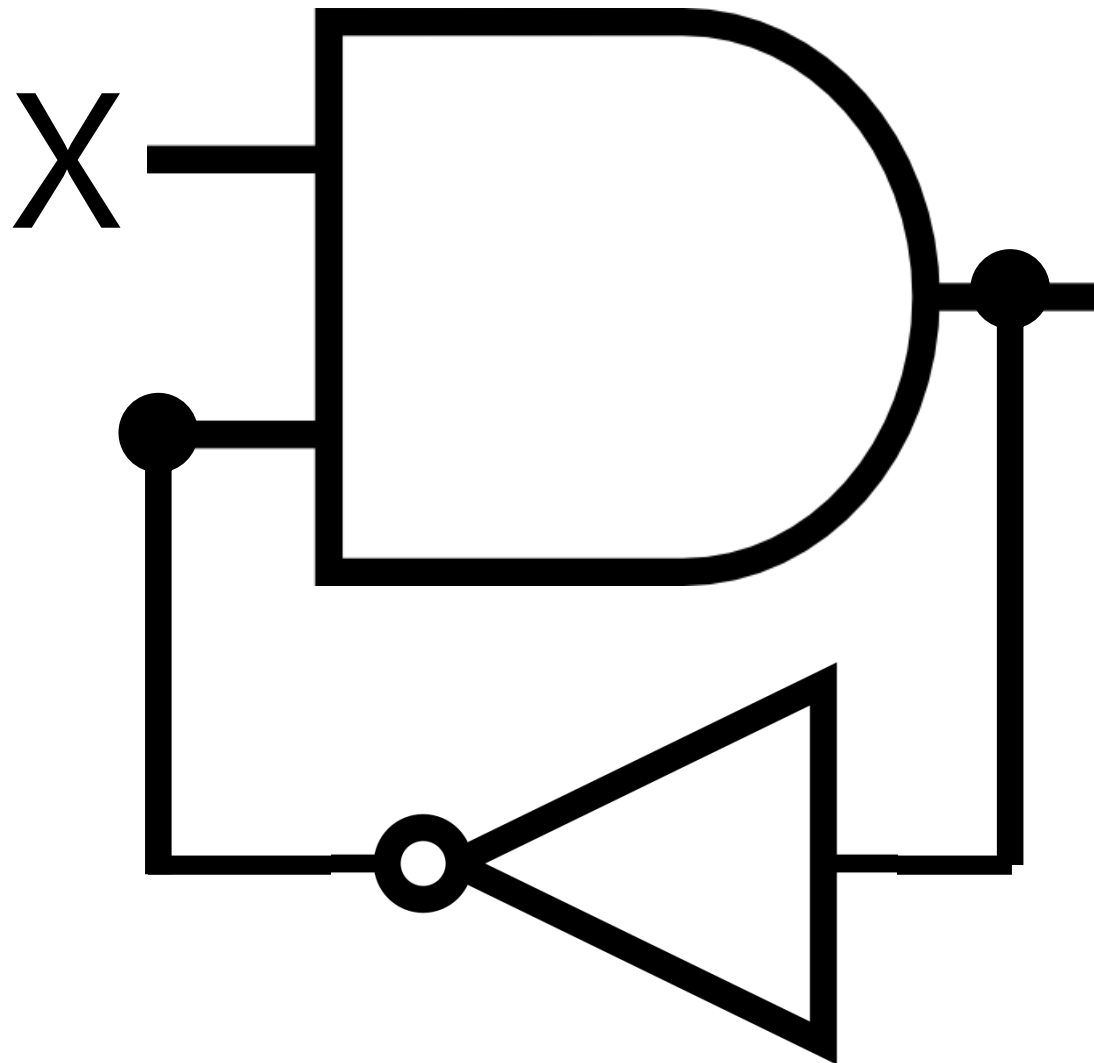This design is logically correct!
But what's the problem?




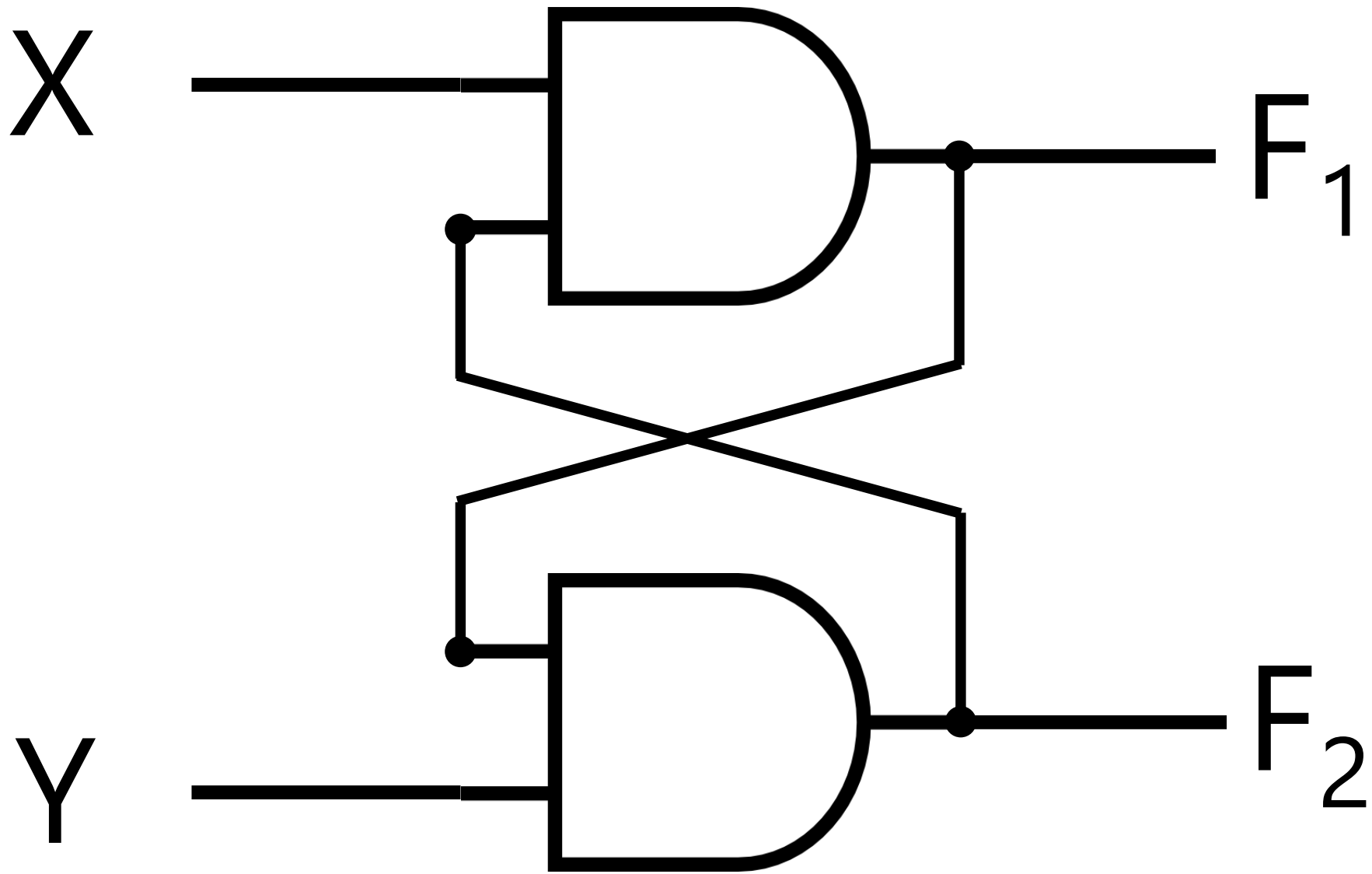This design is also logically correct!
But what's the problem?




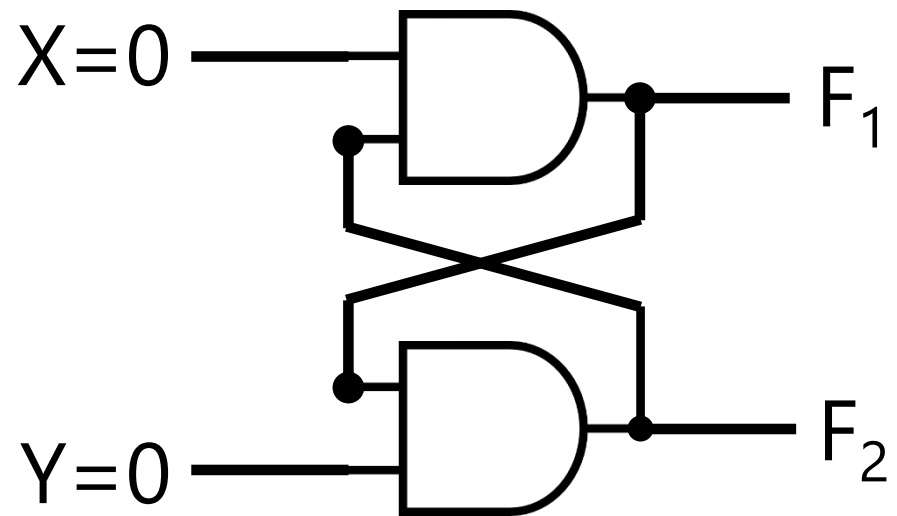


Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0		

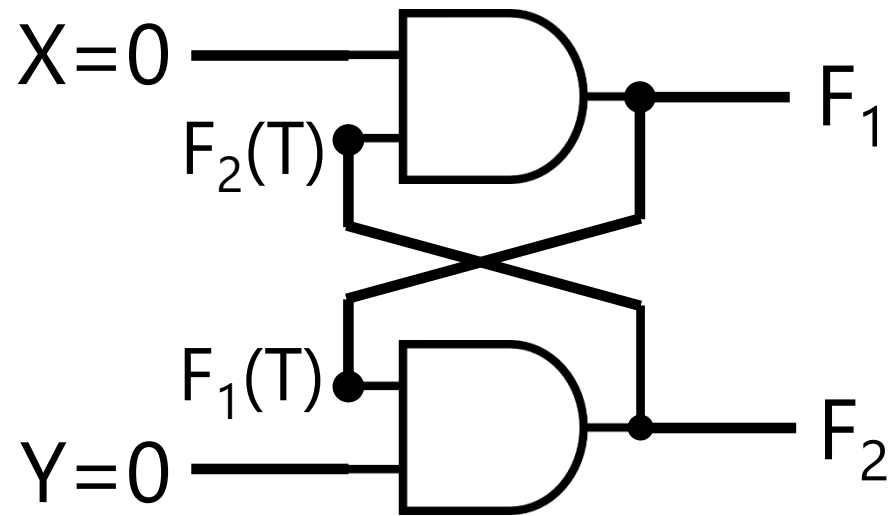


Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0		

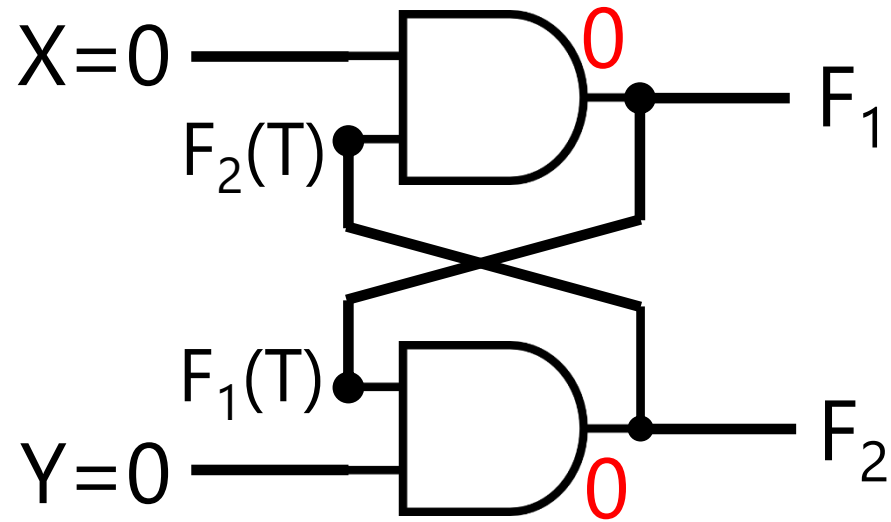


Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0

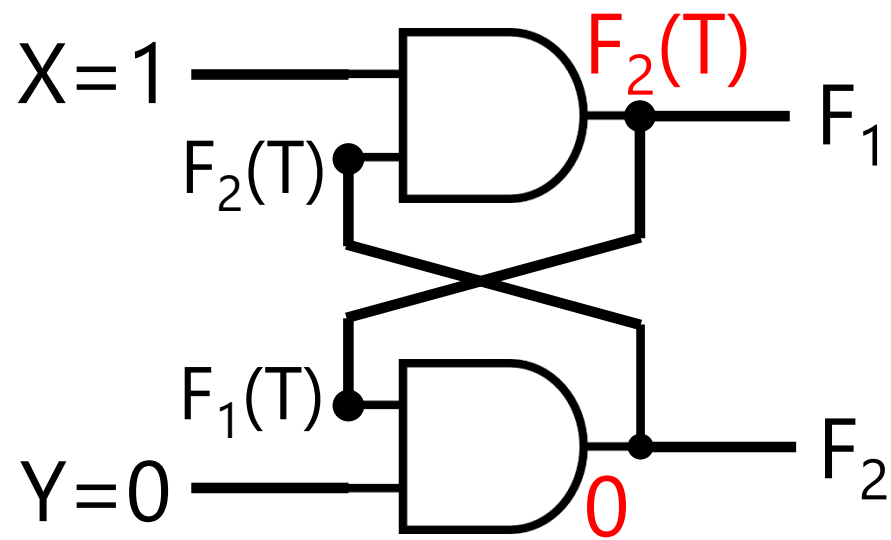


Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0
0	1	$F_2(T)$	0

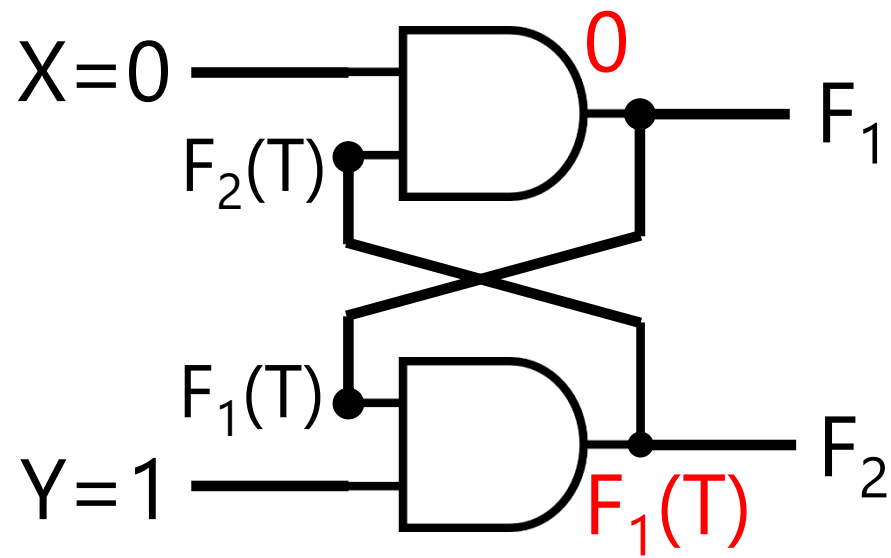

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0
0	1	$F_2(T)$	0
1	0	0	$F_1(T)$

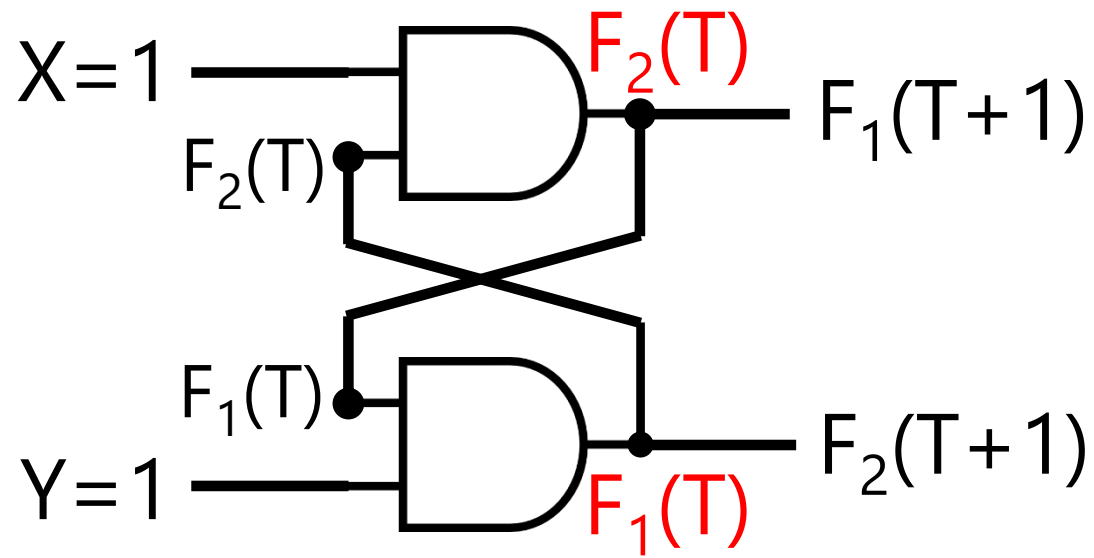


Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0
0	1	$F_2(T)$	0
1	0	0	$F_1(T)$
1	1	$F_2(T)$	$F_1(T)$

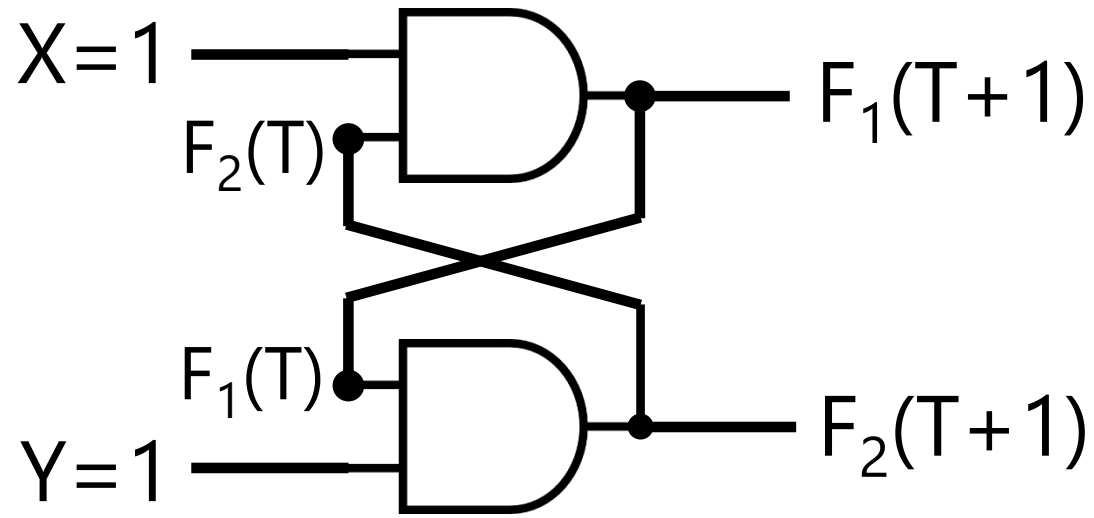


When it goes to 00 state, never recover to 1!

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0
0	1	$F_2(T)$	0
1	0	0	$F_1(T)$
1	1	$F_2(T)$	$F_1(T)$

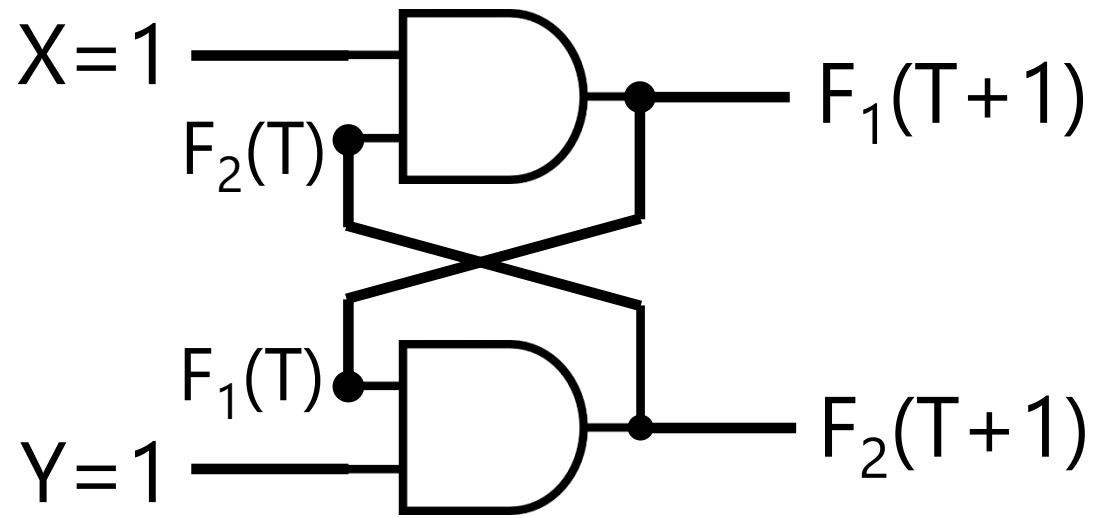


When it goes to 00 state, never recover to 1!

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	0

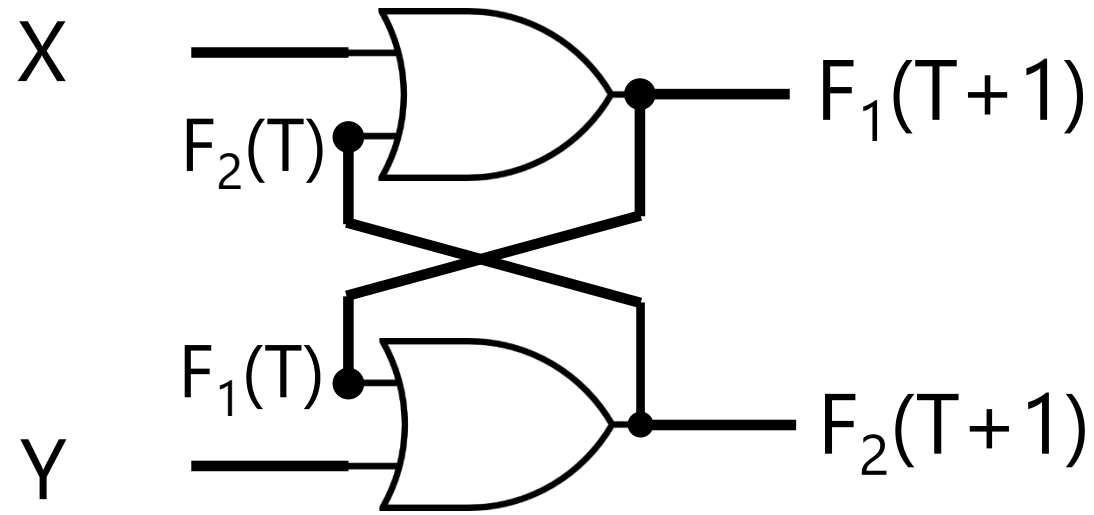


How about OR gates? Do they solve the problem?

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0		
0	1		
1	0		
1	1		

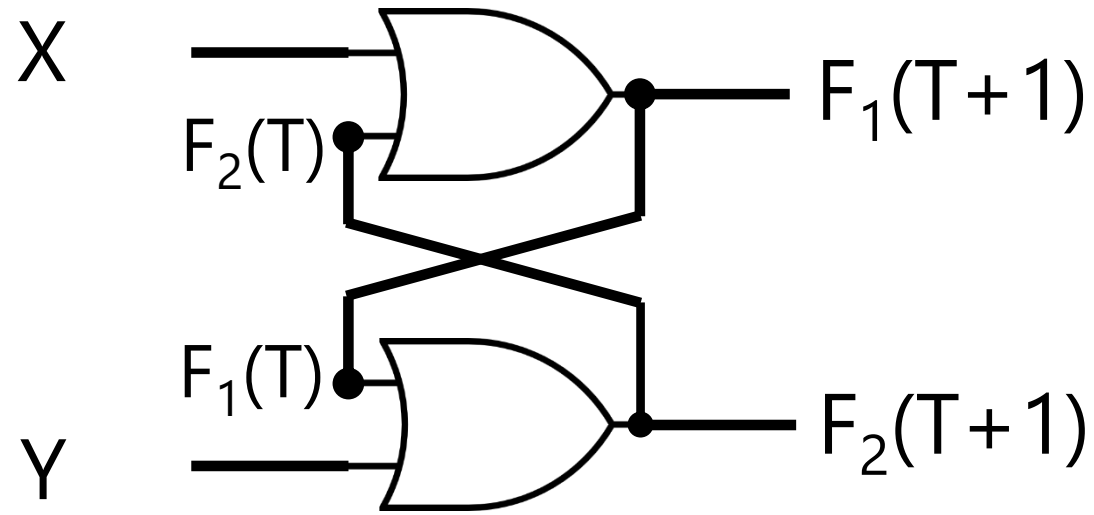


How about OR gates? Do they solve the problem? **No! Why?**

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0		
0	1		
1	0		
1	1		

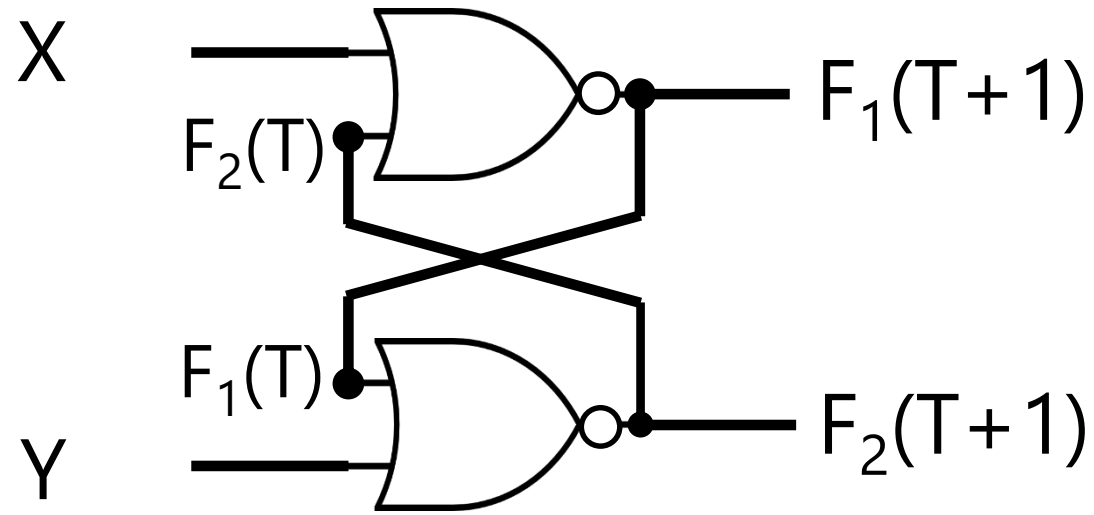


How about NOR gates? Do they solve the problem?

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0		
0	1		
1	0		
1	1		

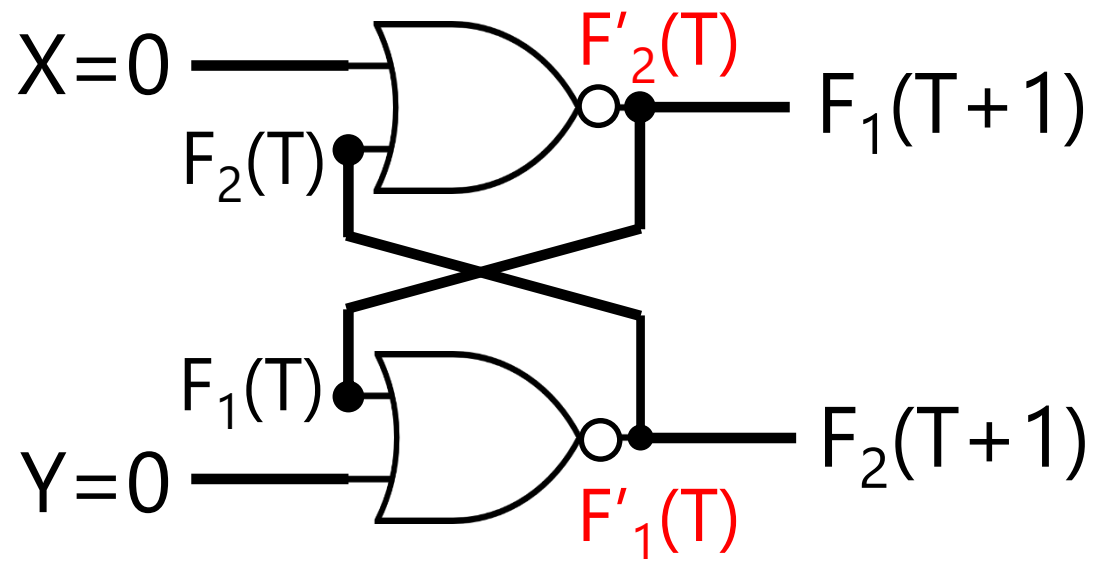


How about NOR gates? Do they solve the problem?

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	$F'_2(T)$	$F'_1(T)$
0	1		
1	0		
1	1		

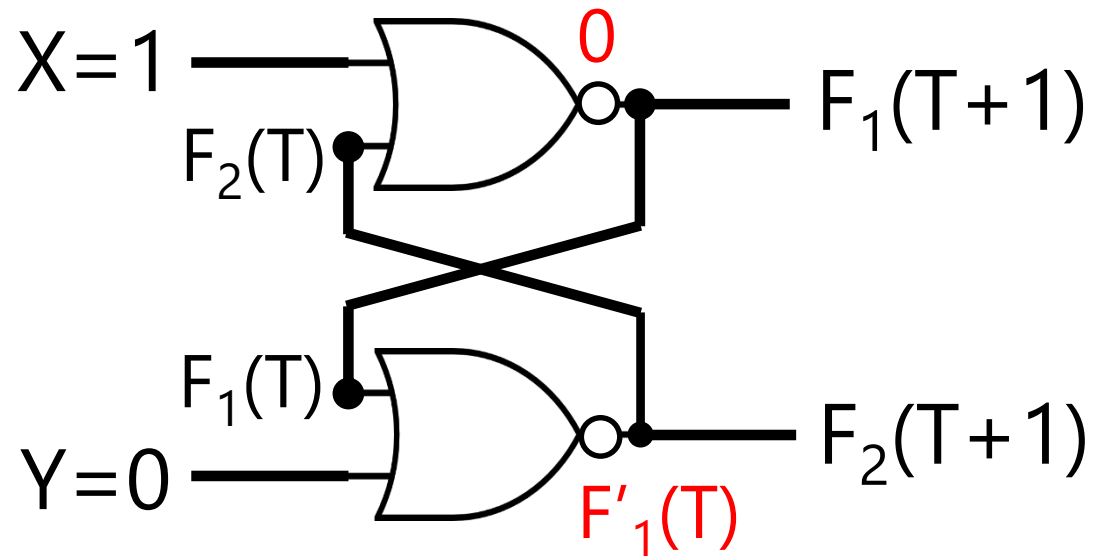


How about NOR gates? Do they solve the problem?

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	$F'_2(T)$	$F'_1(T)$
0	1	0	$F'_1(T)$
1	0		
1	1		

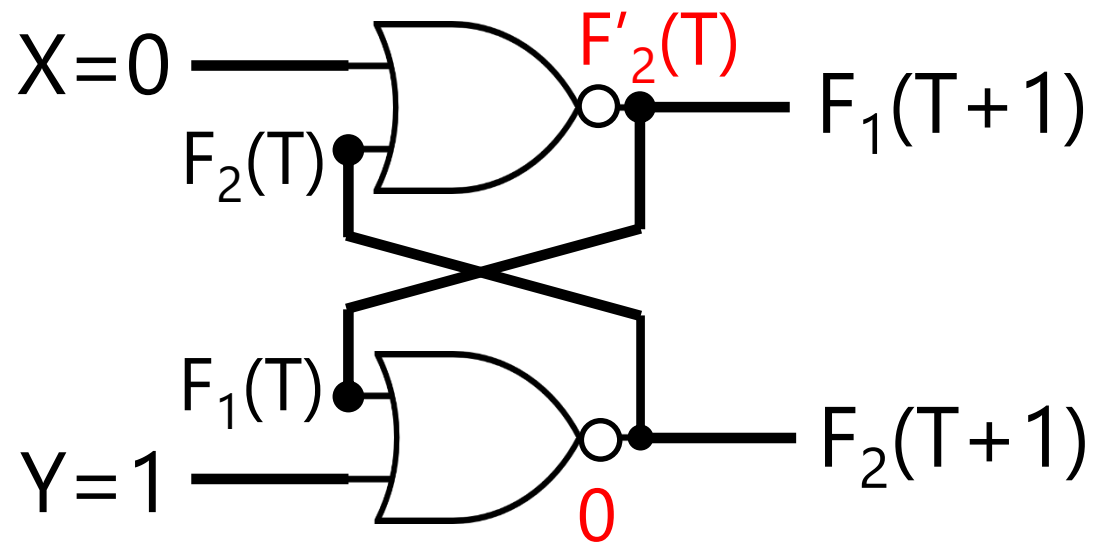


How about NOR gates? Do they solve the problem?

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	$F'_2(T)$	$F'_1(T)$
0	1	0	$F'_1(T)$
1	0	$F'_2(T)$	0
1	1		

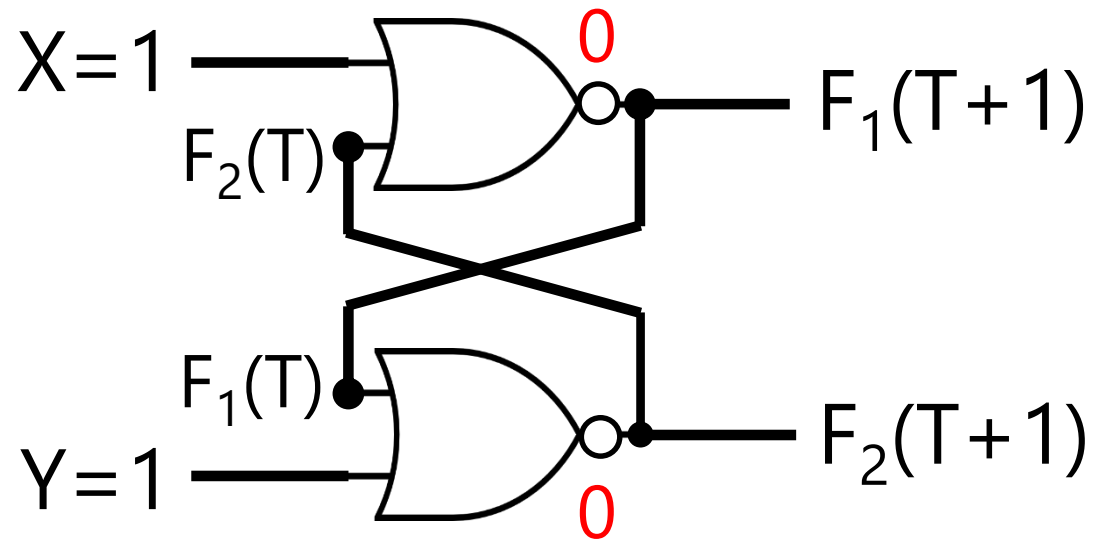


How about NOR gates? Do they solve the problem?

Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	$F'_2(T)$	$F'_1(T)$
0	1	0	$F'_1(T)$
1	0	$F'_2(T)$	0
1	1	0	0

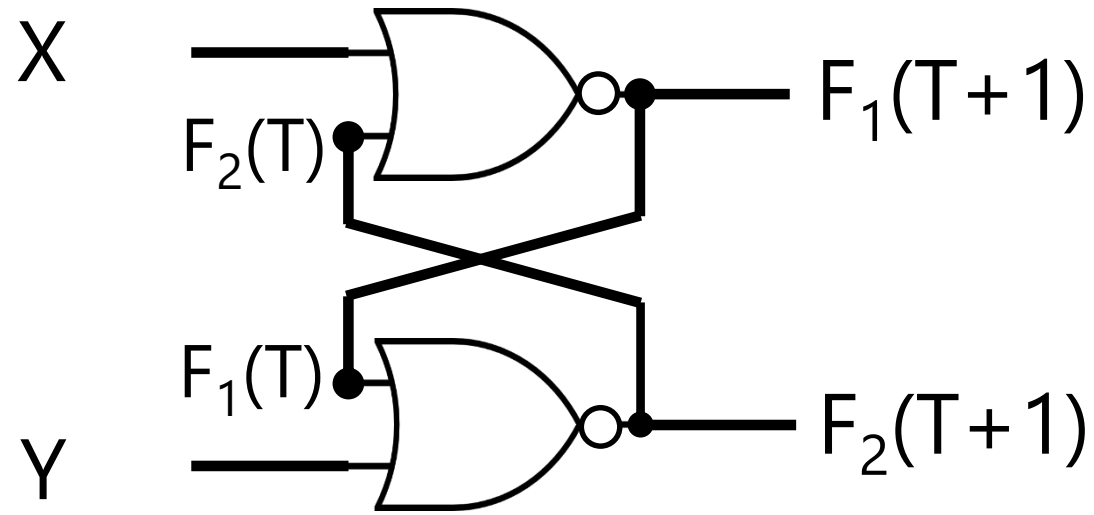


Seems working. But we have to check all possible current states?


Y	X	$F_1(T+1)$	$F_2(T+1)$
0	0	$F'_2(T)$	$F'_1(T)$
0	1	0	$F'_1(T)$
1	0	$F'_2(T)$	0
1	1	0	0

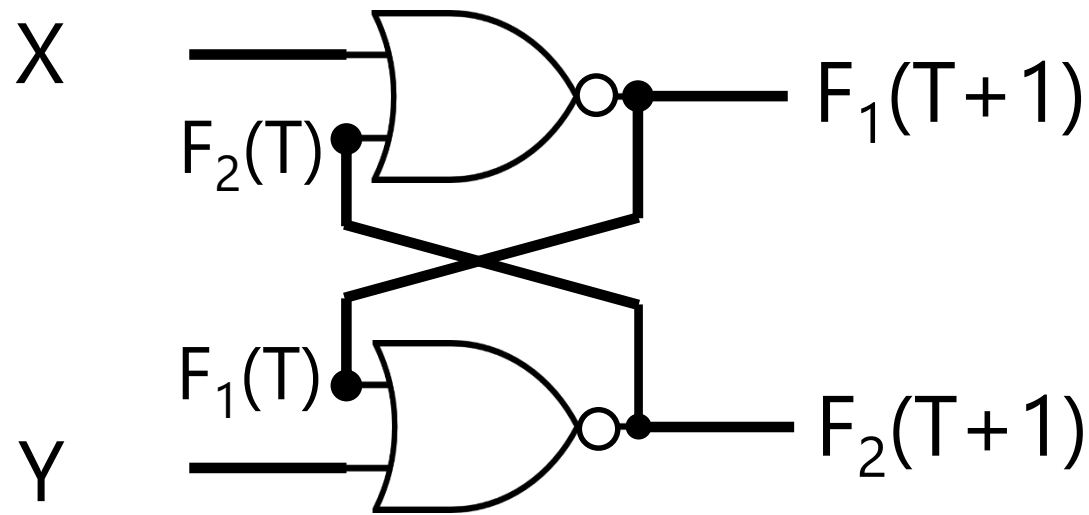

		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0	$F'_2(T)$	$F'_1(T)$
0	1			0	$F'_1(T)$
1	0			$F'_2(T)$	0
1	1			0	0

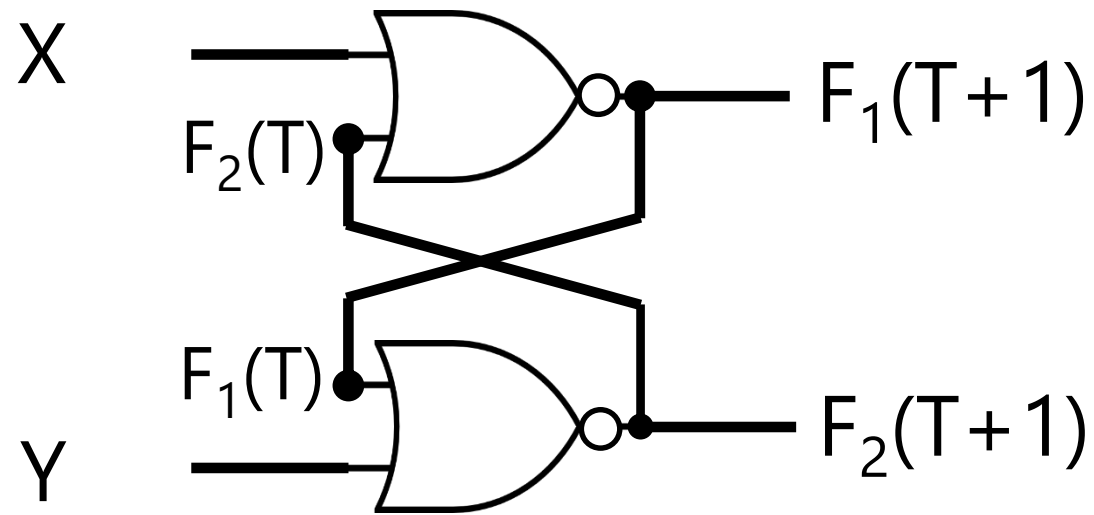


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0	1	1
0	1			0	1
1	0			1	0
1	1			0	0

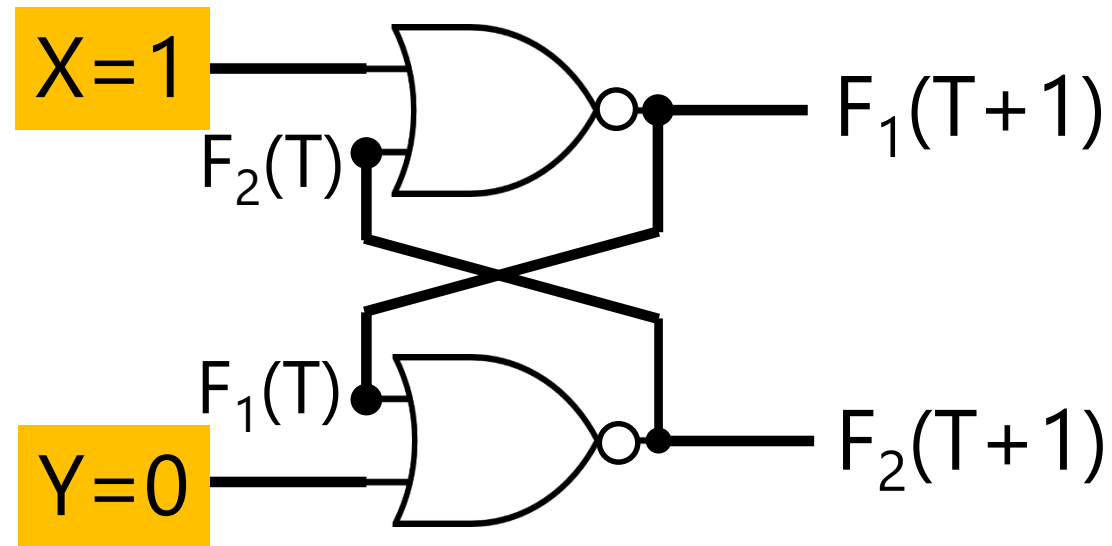

Reset Action

Reset State


Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0	1	1
0	1			0	1
1	0			1	0
1	1			0	0

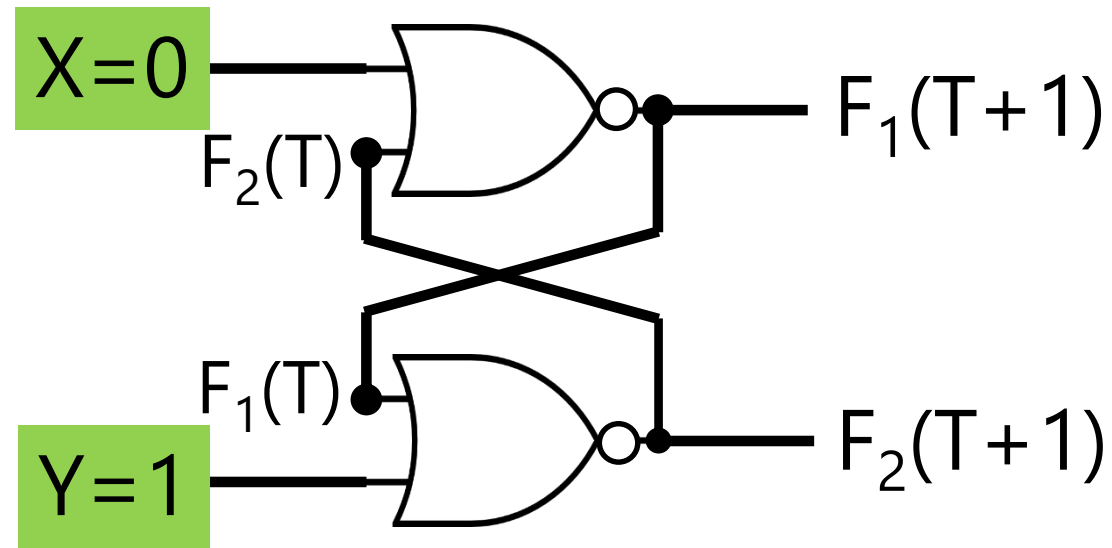

Set Action


Set State

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0	1	1
0	1			0	1
1	0			1	0
1	1			0	0

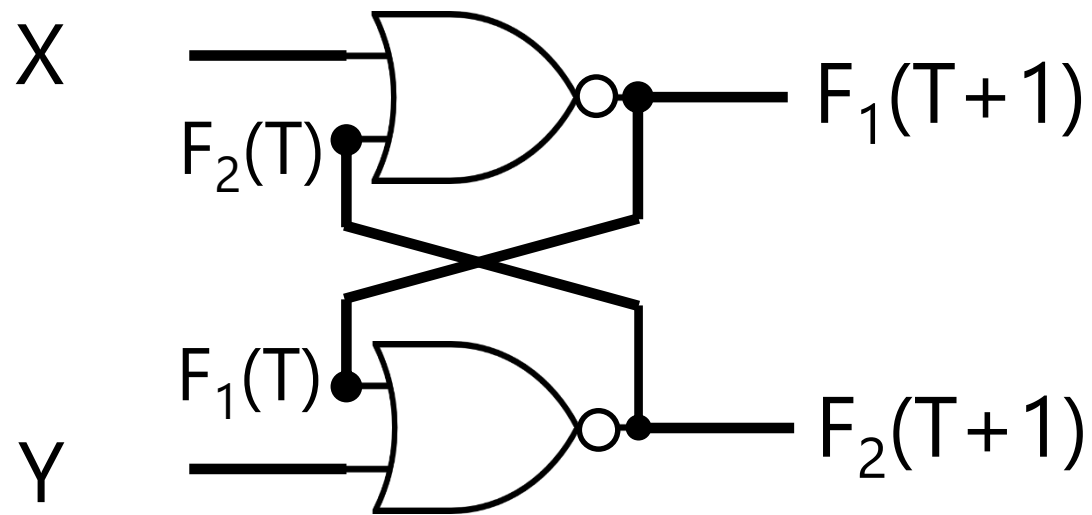


$F_1 = F'_2$


Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0	1	1
0	1			0	1
1	0			1	0
1	1			0	0

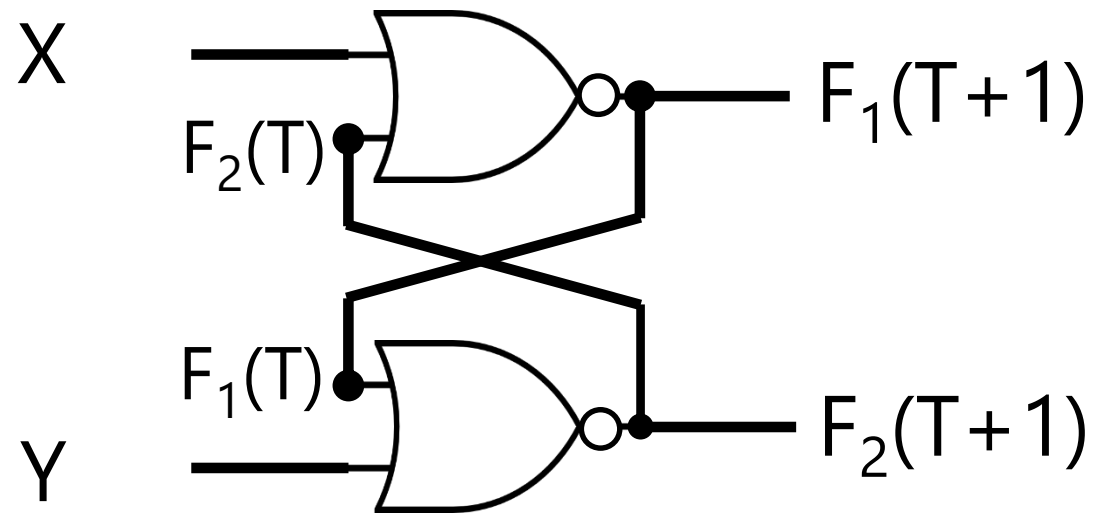

		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	1	$F'_2(T)$	$F'_1(T)$
0	1			0	$F'_1(T)$
1	0			$F'_2(T)$	0
1	1			0	0

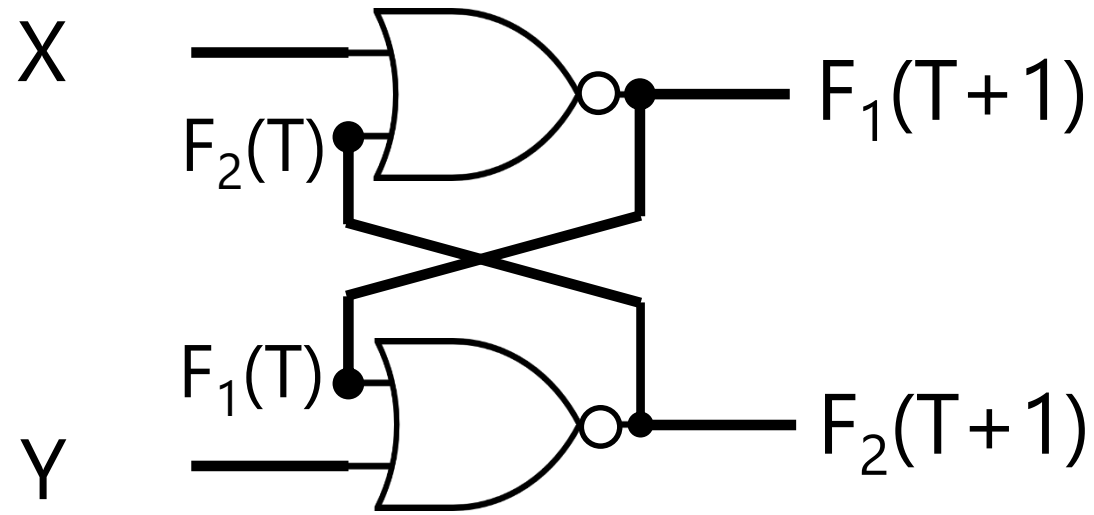


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	1	0	0
0	1			0	0
1	0			0	0
1	1			0	0

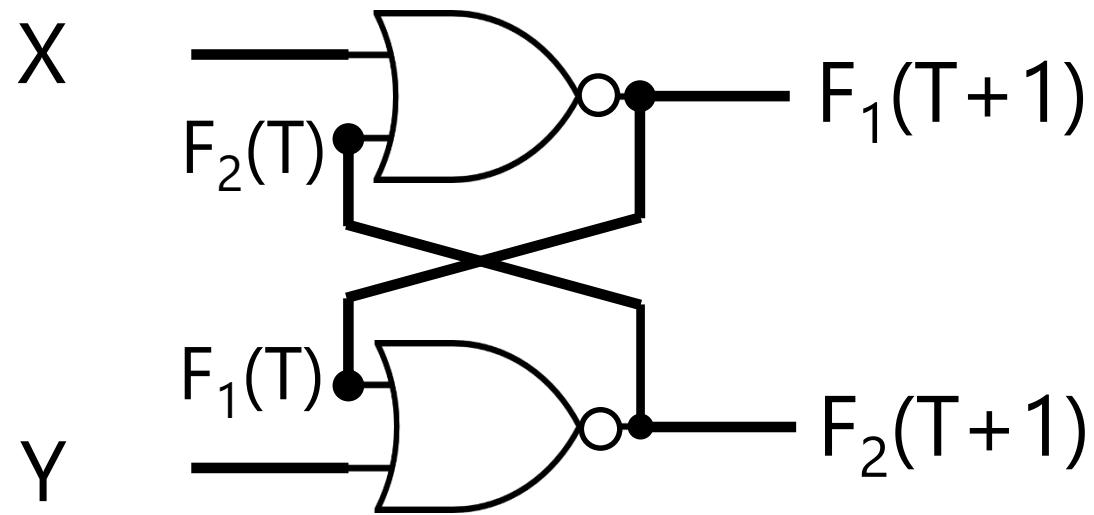


Default State

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	1	0	0
0	1				
1	0				
1	1				

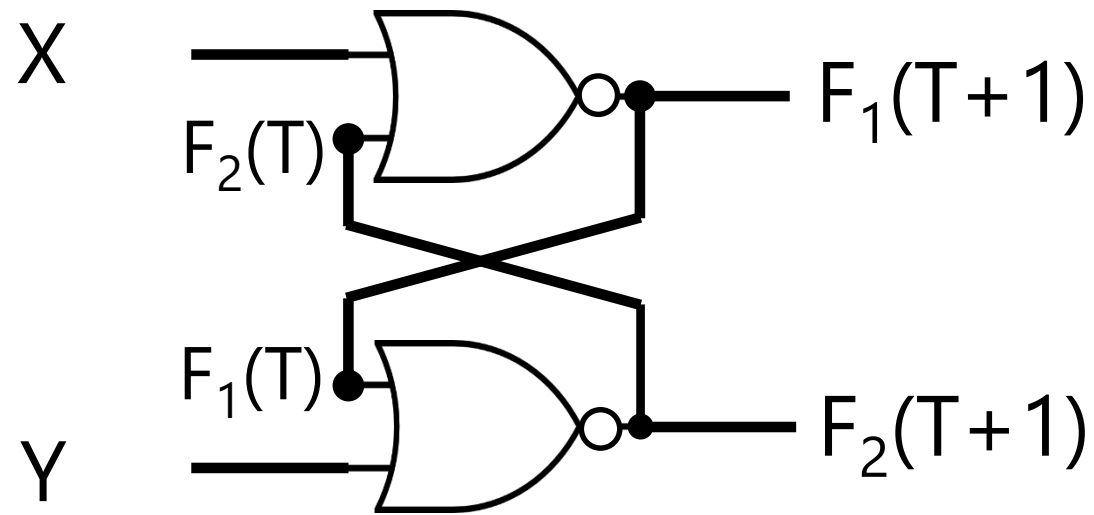


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	0	$F'_2(T)$	$F'_1(T)$
0	1			0	$F'_1(T)$
1	0			$F'_2(T)$	0
1	1			0	0

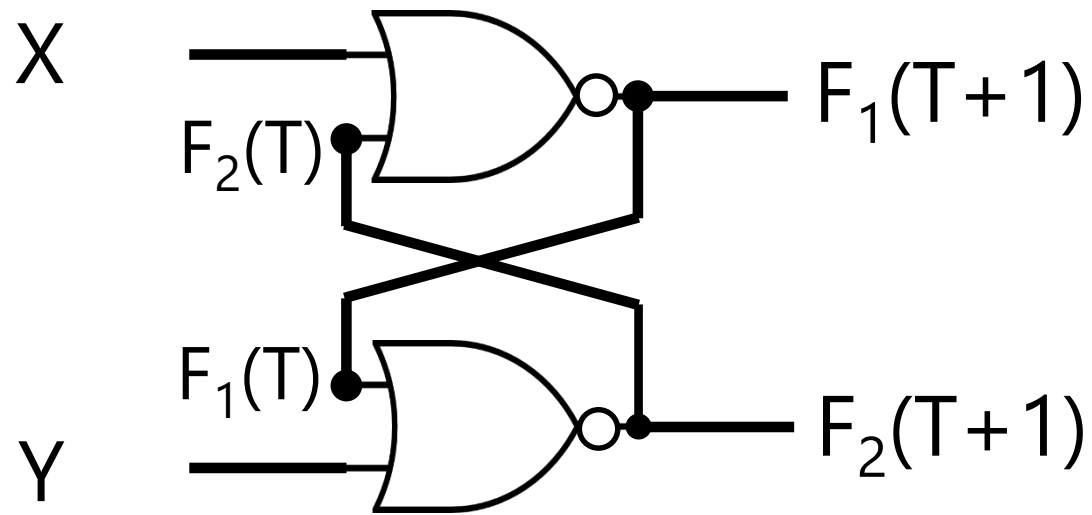


Set State

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	0	$F'_2(T)$	$F'_1(T)$
0	1			0	$F'_1(T)$
1	0			$F'_2(T)$	0
1	1			0	0

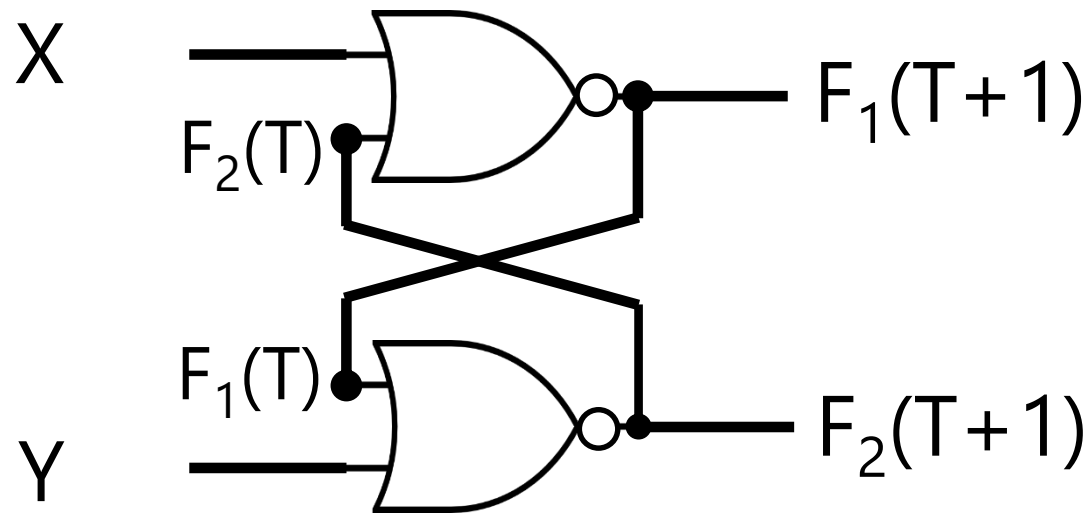


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	0	1	0
0	1			0	0
1	0			1	0
1	1			0	0

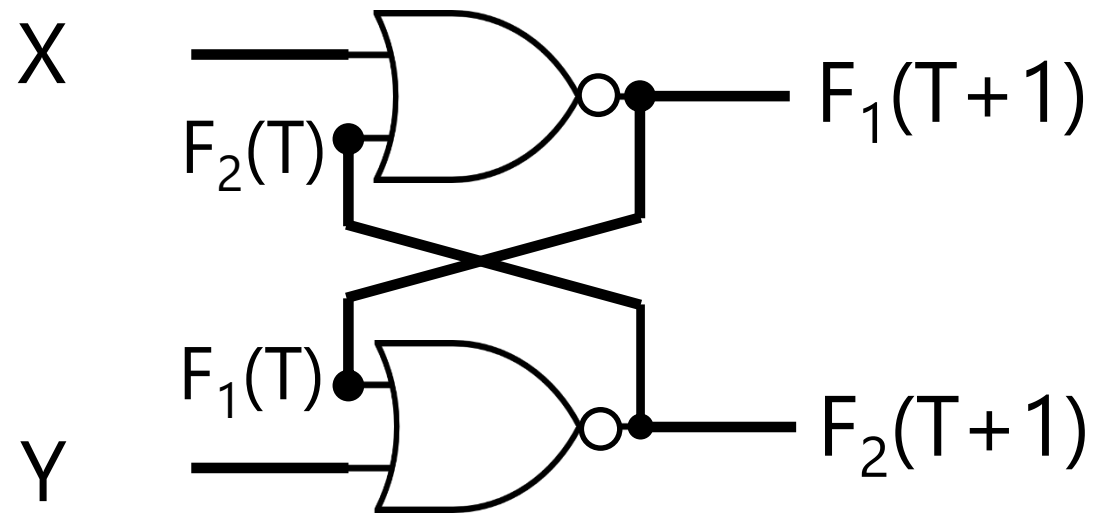


Store/Hold

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	0	1	0
0	1			0	0
1	0			1	0
1	1			0	0

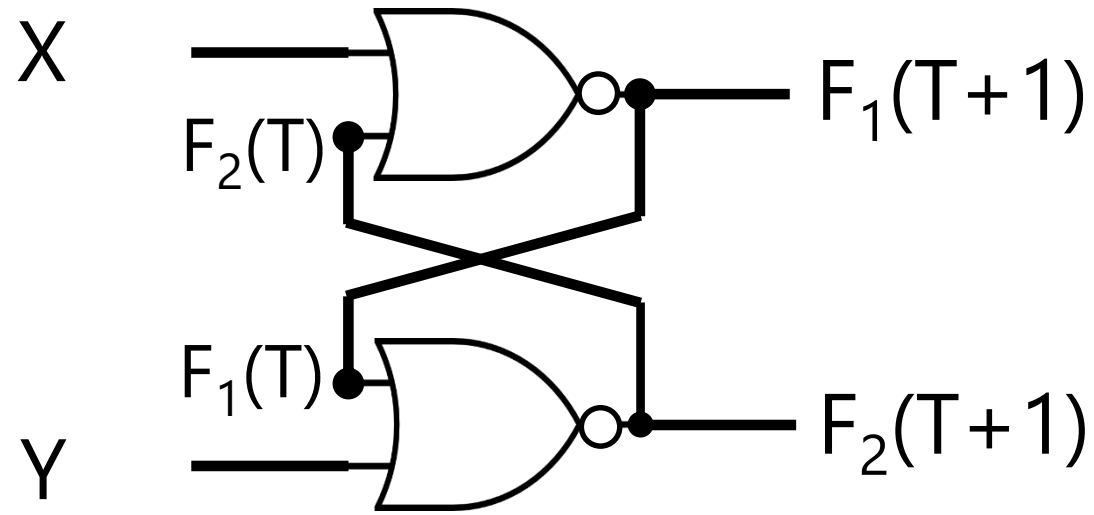

Set Action


Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	0	1	0
0	1			0	0
1	0			1	0
1	1			0	0

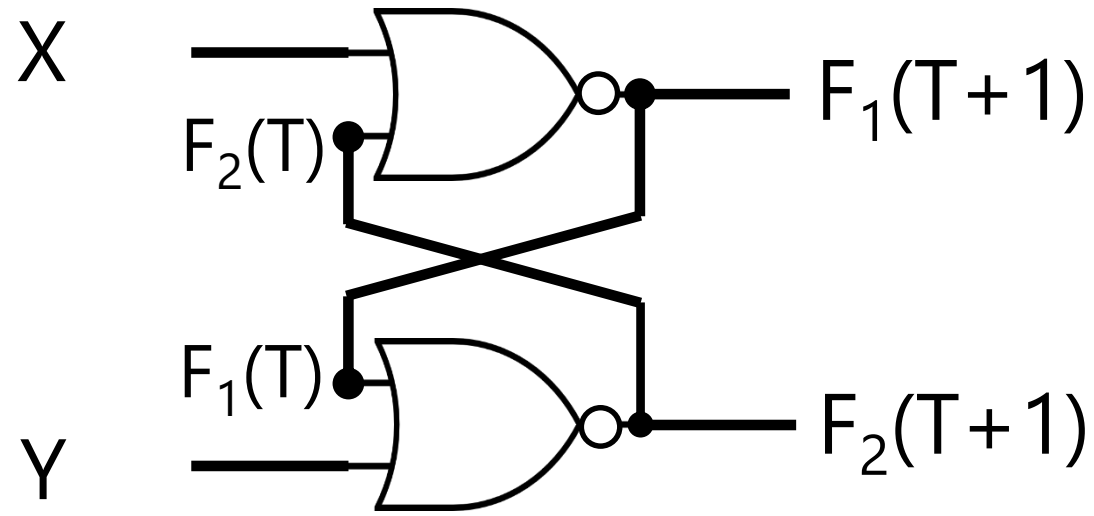

Reset Action

$F_1 \neq F'_2$

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	0	1	0
0	1			0	0
1	0			1	0
1	1			0	0

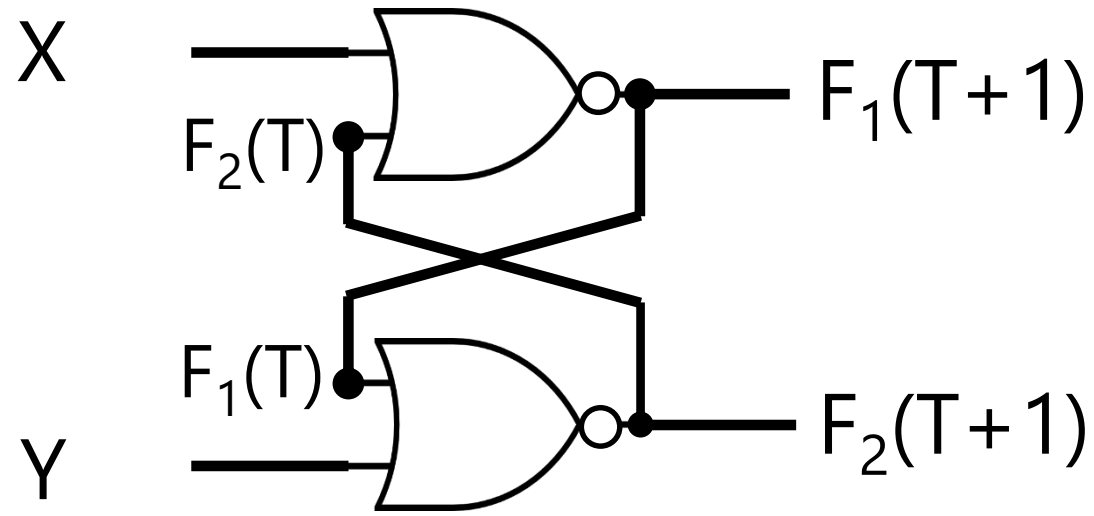


Reset Action


Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$	$F_1(T+2)$	$F_2(T+2)$
0	0	1	0	1	0	1	0
0	1			0	0	0	1
1	0			1	0	1	0
1	1			0	0	0	0

Reset Action


$F_1 = F'_2$

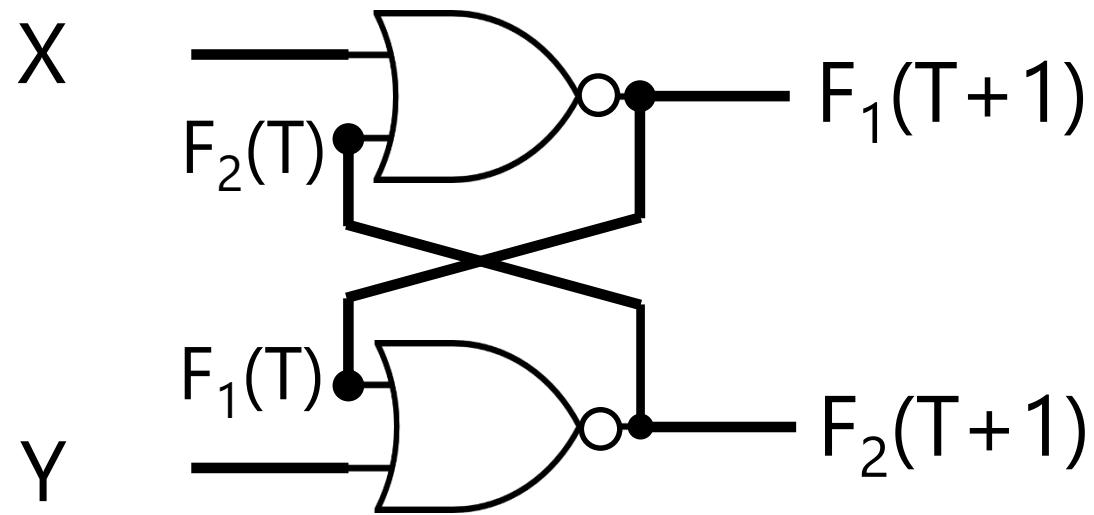

		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+2)$	$F_2(T+2)$
0	0	1	0	1	0
0	1			0	1
1	0			1	0
1	1			0	0

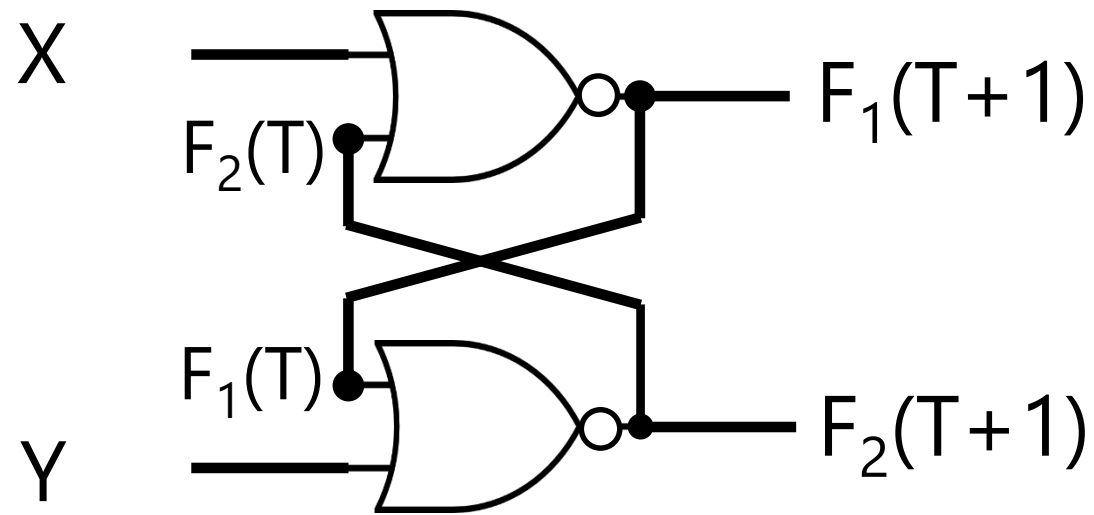


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	1	$F'_2(T)$	$F'_1(T)$
0	1			0	$F'_1(T)$
1	0			$F'_2(T)$	0
1	1			0	0

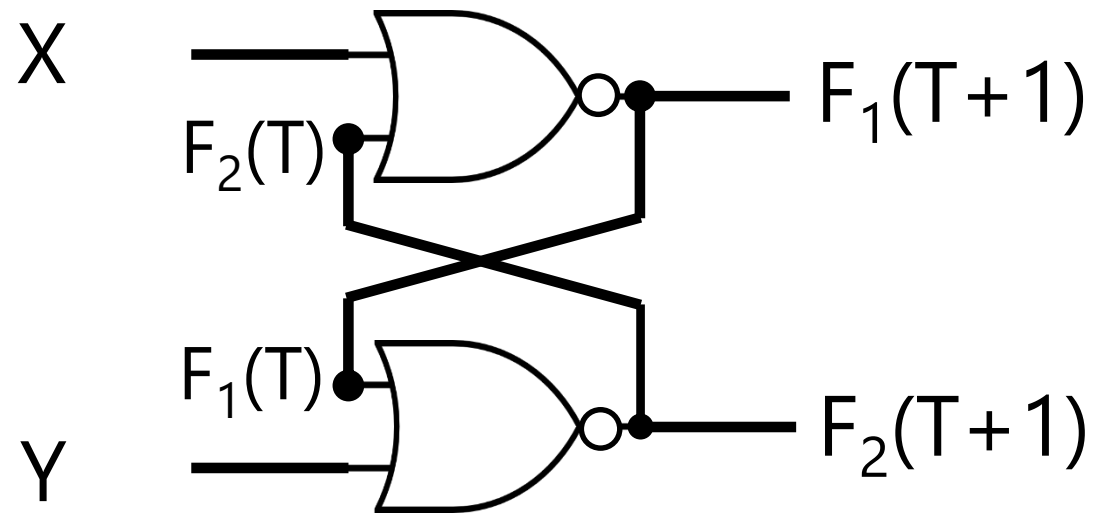


Reset State

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	1	$F'_2(T)$	$F'_1(T)$
0	1			0	$F'_1(T)$
1	0			$F'_2(T)$	0
1	1			0	0

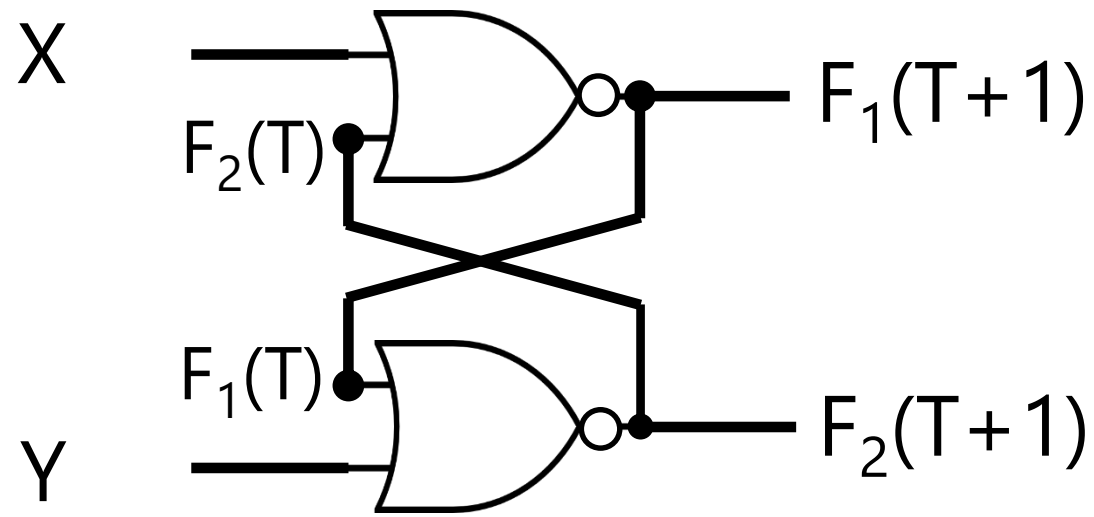


Store/Hold

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	1	0	1
0	1			0	1
1	0			0	0
1	1			0	0

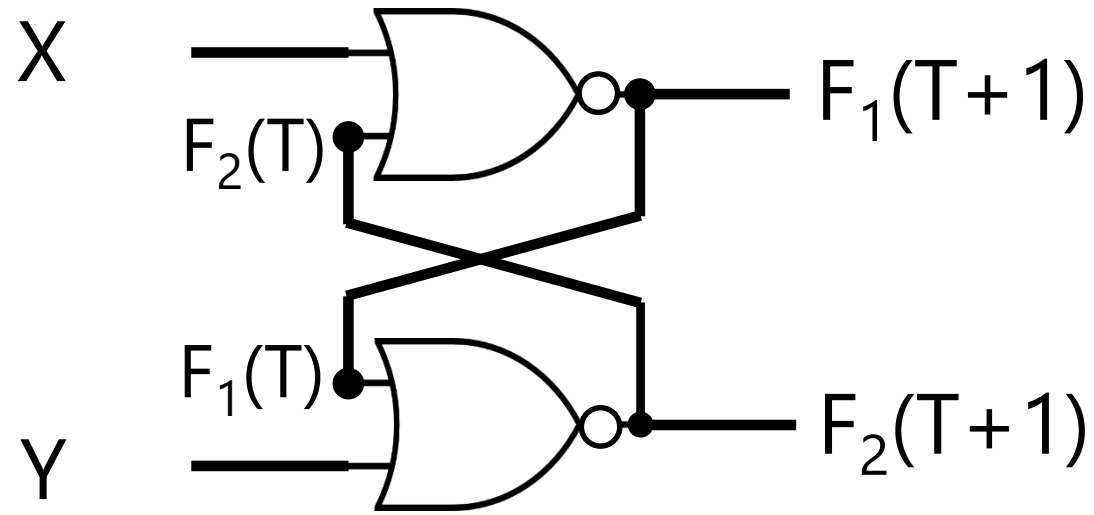


Reset Action

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	1	0	1
0	1			0	1
1	0			0	0
1	1			0	0

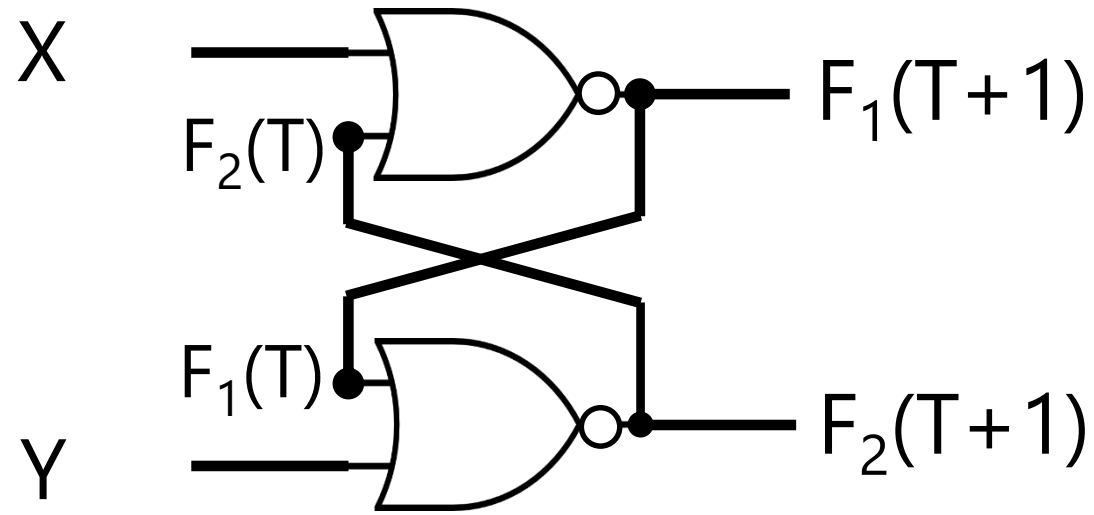


Set Action

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	1	0	1
0	1			0	1
1	0			0	0
1	1			0	0

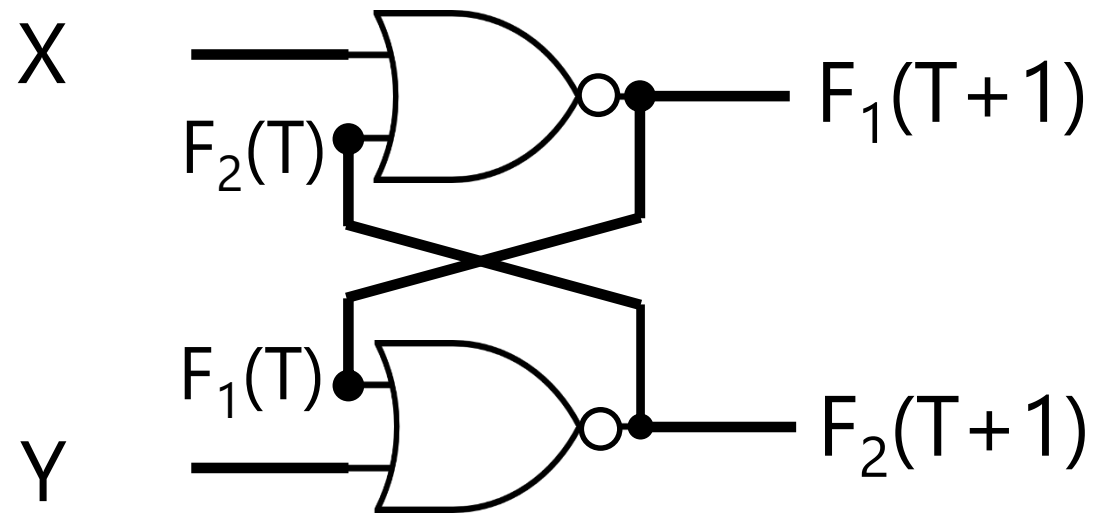


Set Action

Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$	$F_1(T+2)$	$F_2(T+2)$
0	0	0	1	0	1	0	1
0	1			0	1	0	1
1	0			0	0	1	0
1	1			0	0	0	0

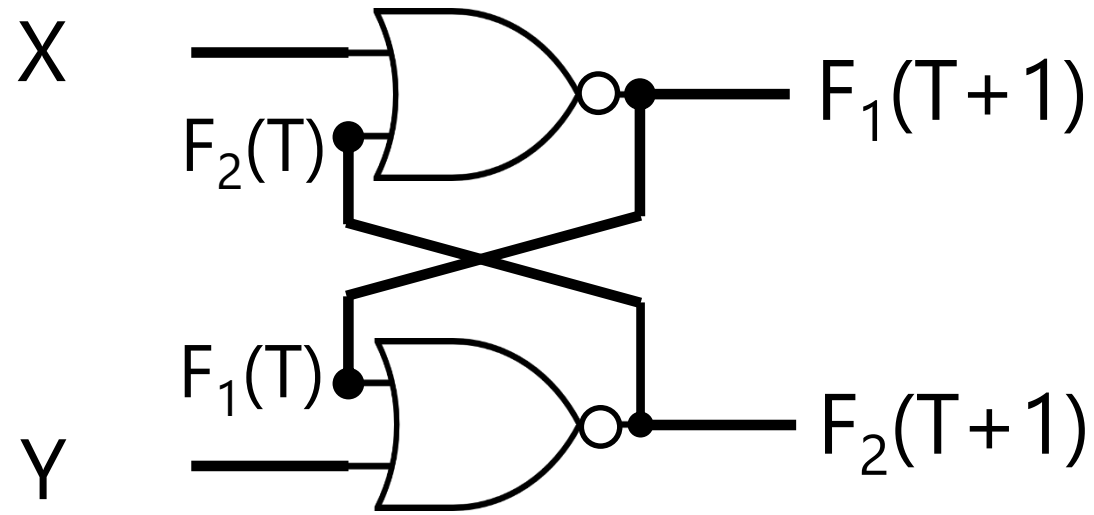


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+2)$	$F_2(T+2)$
0	0	0	1	0	1
0	1	0	1	0	1
1	0	0	1	1	0
1	1	0	1	0	0


Recap

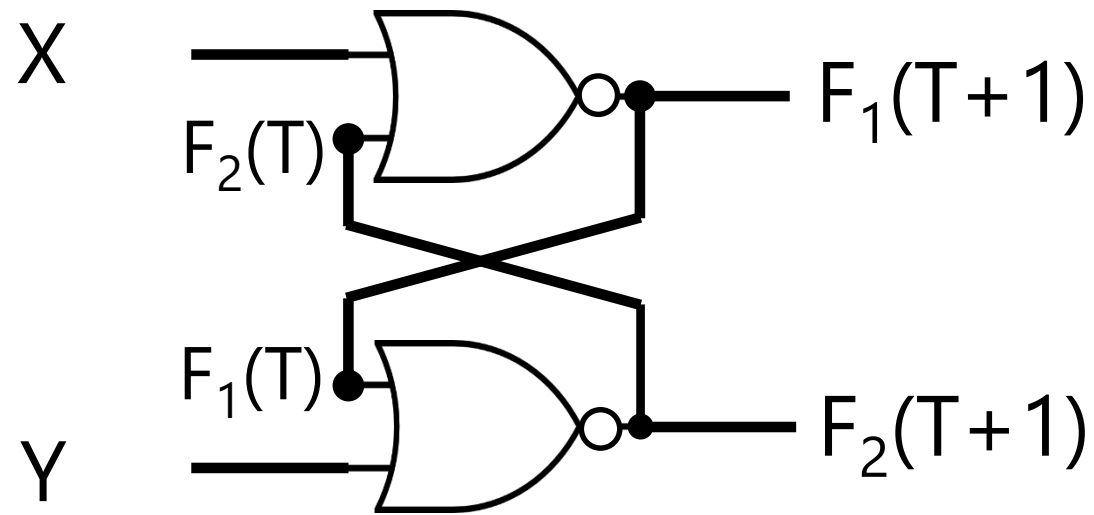


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	0	0	1	1
0	1			0	1
1	0			1	0
1	1			0	0

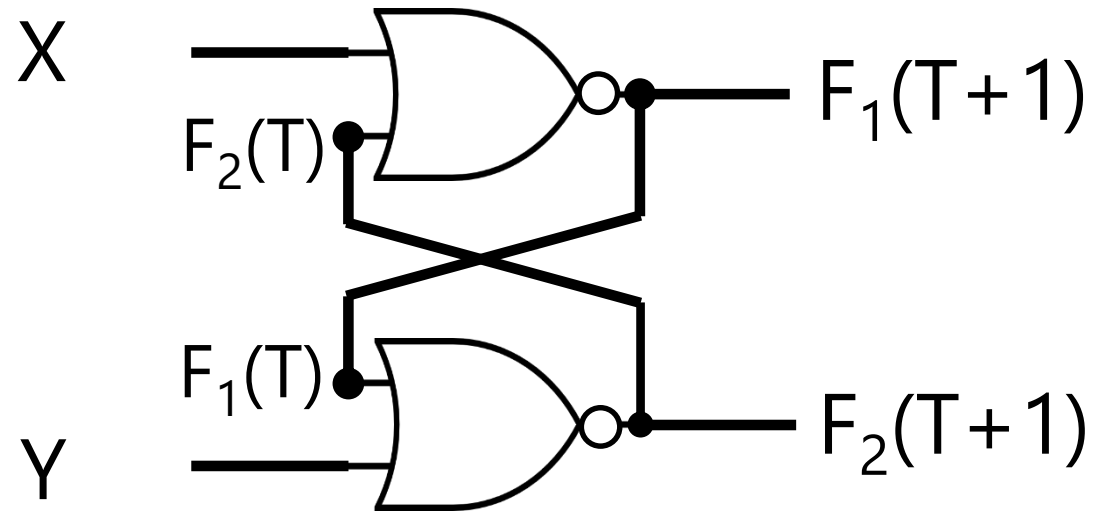


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$
0	0	1	1	0	0
0	1			0	0
1	0			0	0
1	1			0	0

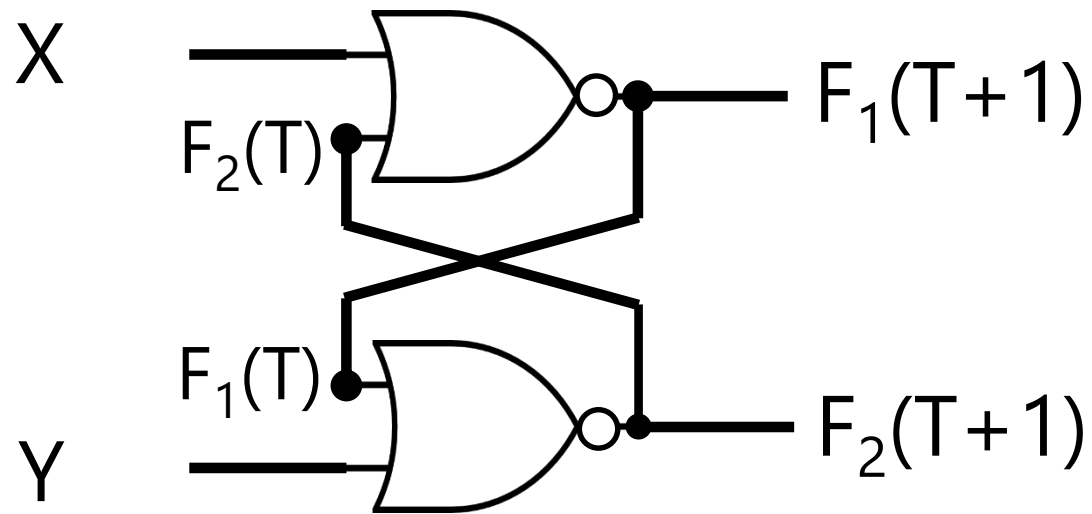


Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+1)$	$F_2(T+1)$	$F_1(T+2)$	$F_2(T+2)$
0	0	1	1	0	0	1	1
0	1					0	1
1	0					1	0
1	1					0	0

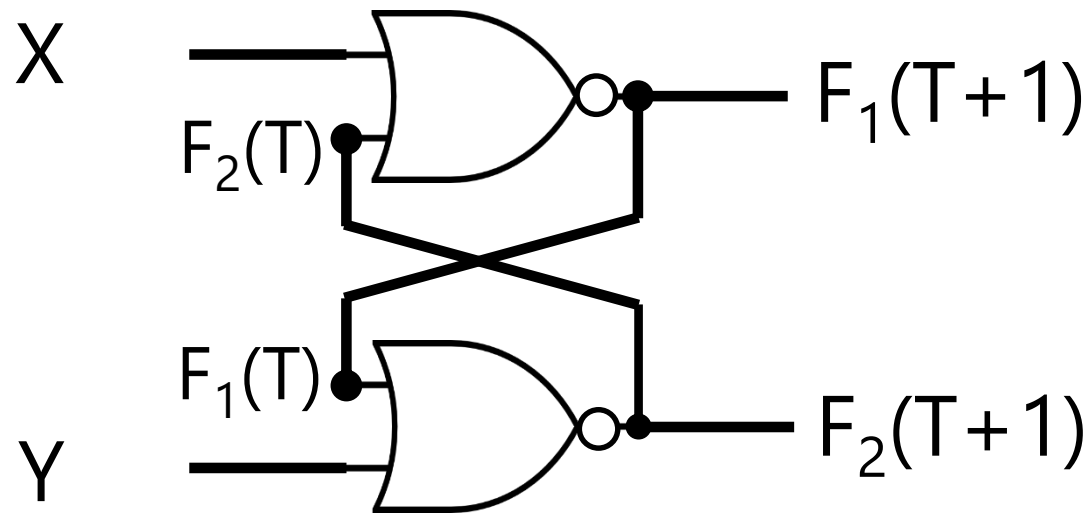


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+2)$	$F_2(T+2)$
0	0	1	0	1	0
0	1			0	1
1	0			1	0
1	1			0	0

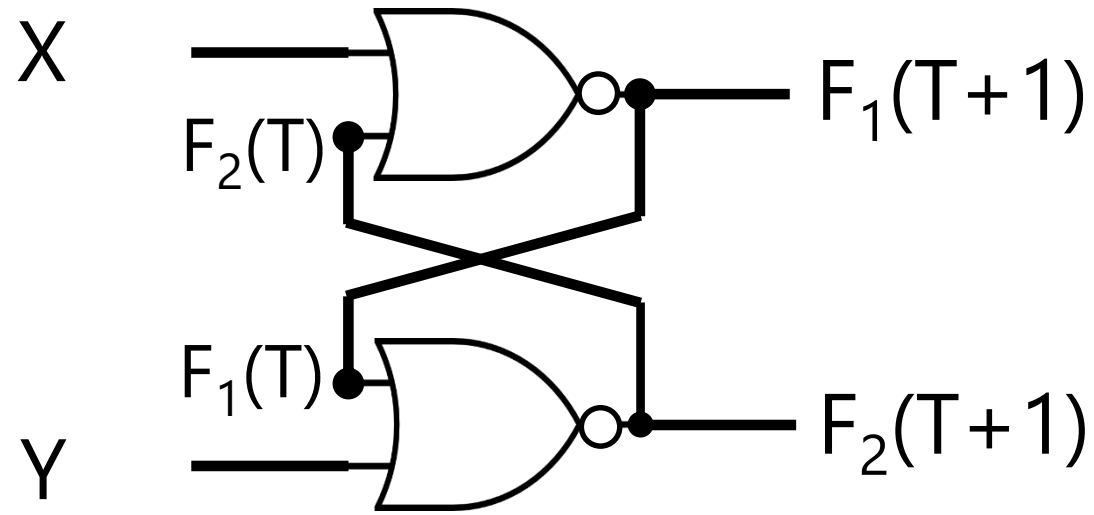


		Current State		Next State	
Y	X	$F_1(T)$	$F_2(T)$	$F_1(T+2)$	$F_2(T+2)$
0	0	0	1	0	1
0	1			0	1
1	0			1	0
1	1			0	0

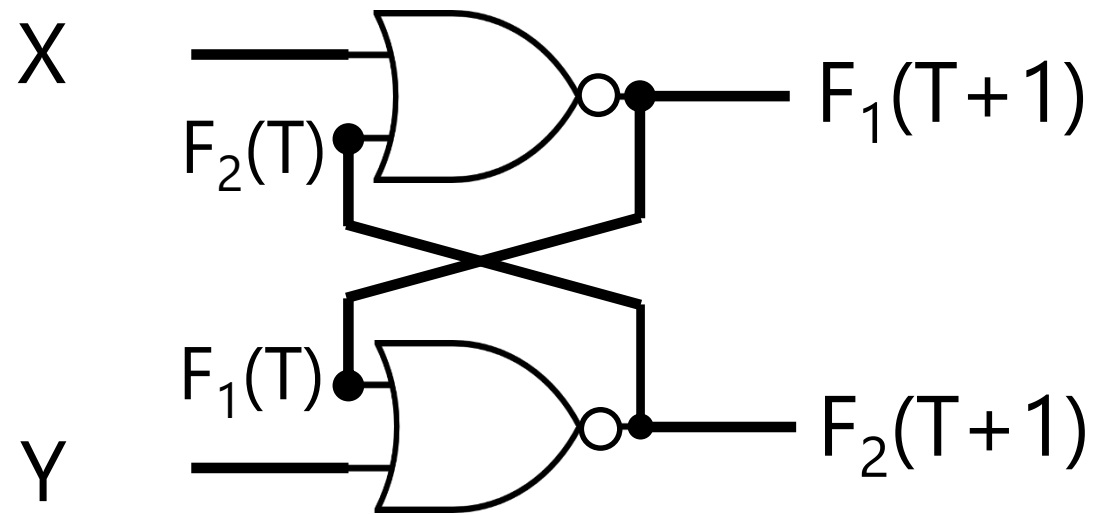


Y	X	$F_1(T+2)$	$F_2(T+2)$
0	0	$F_1(T)$	$F_2(T)$
0	1	0	1
1	0	1	0
1	1	\times	\times

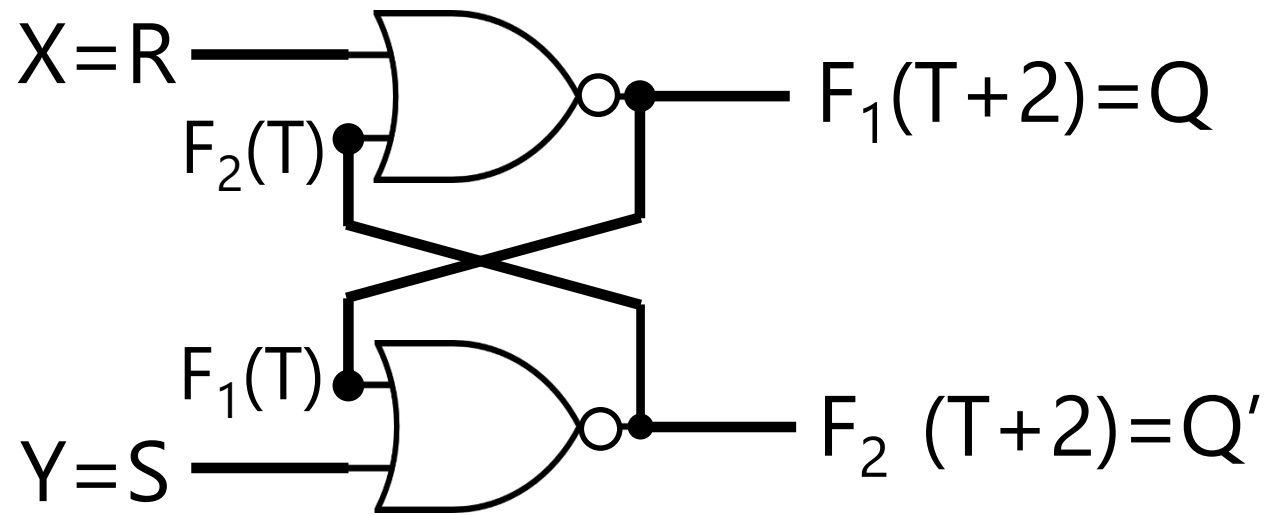


$Y=S$	$X=R$	$F_1(T+2)=Q$	$F_2(T+2)=Q'$
0	0	Q_t	Q'_t
0	1	0	1
1	0	1	0
1	1	\times	\times

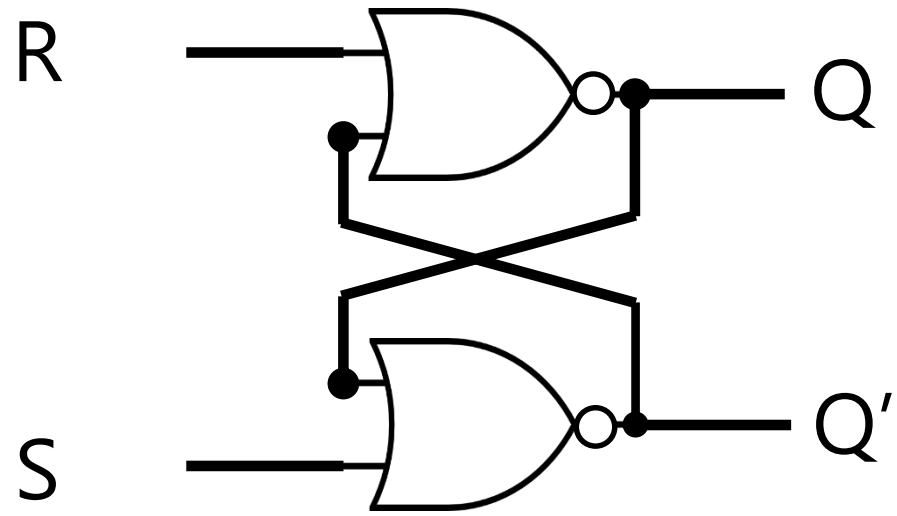

S	R	Q	Q'
0	0	Q_t	Q'_t
0	1	0	1
1	0	1	0
1	1	\times	\times


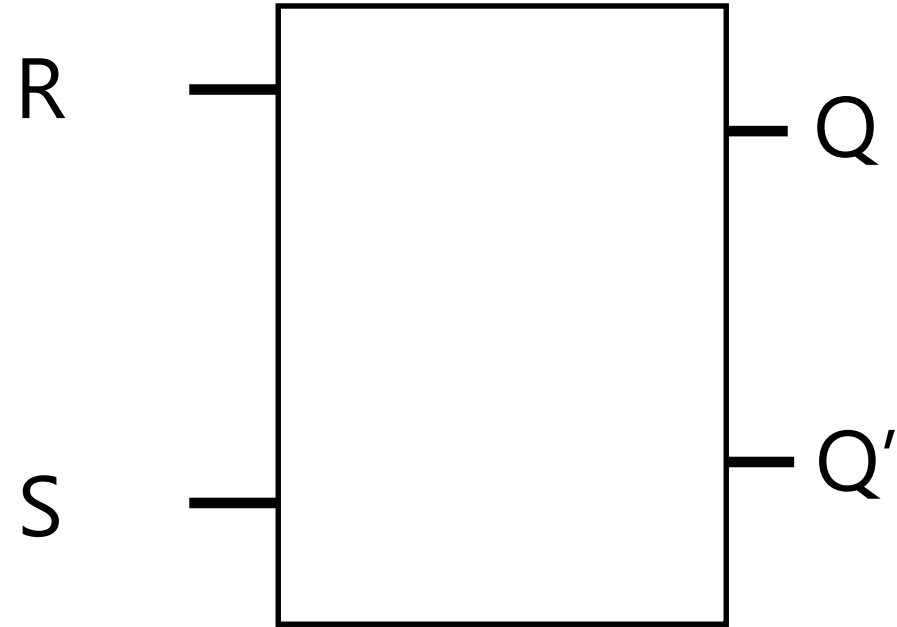


S	R	Q	Q'
0	0	Q_t	Q'_t
0	1	0	1
1	0	1	0
1	1	\times	\times

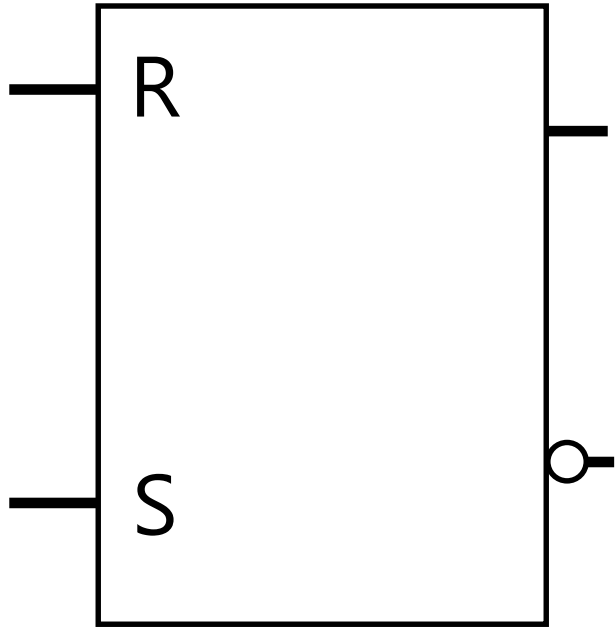



S	R	Q	Q'
0	0	Q_t	Q'_t
0	1	0	1
1	0	1	0
1	1	x	x

Voltage

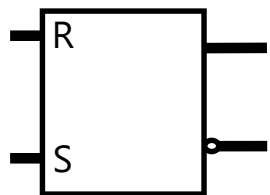
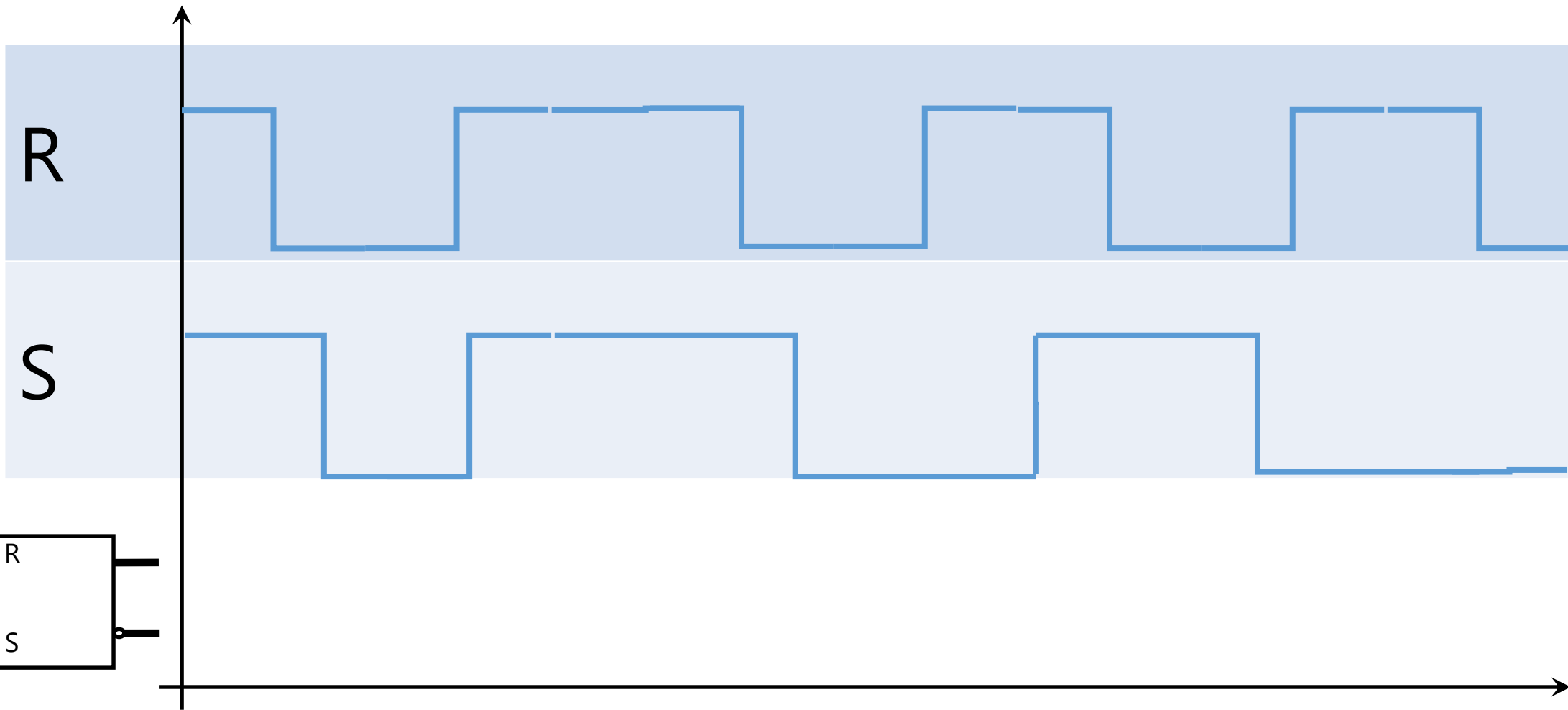


Time

Voltage

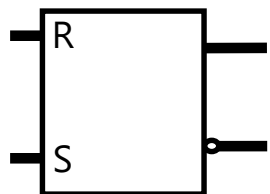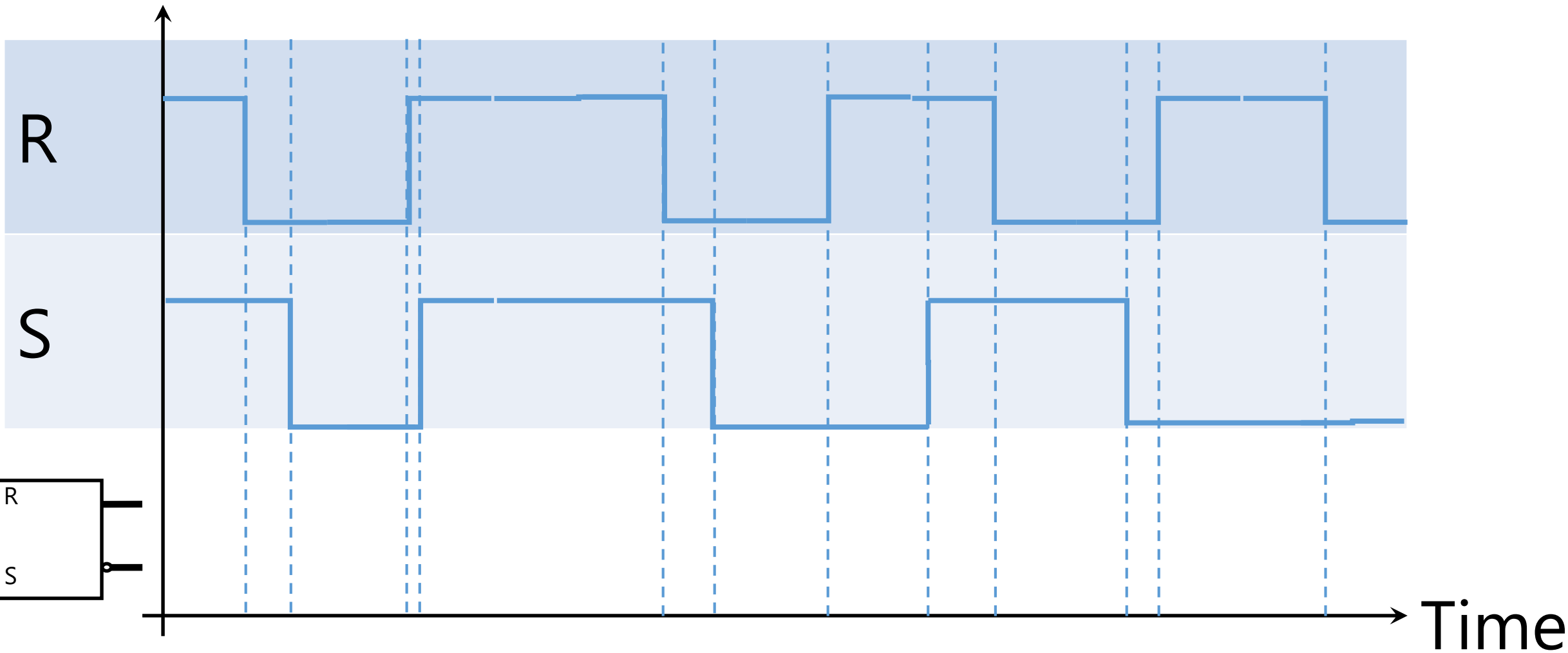


Voltage

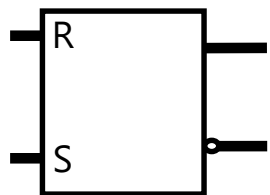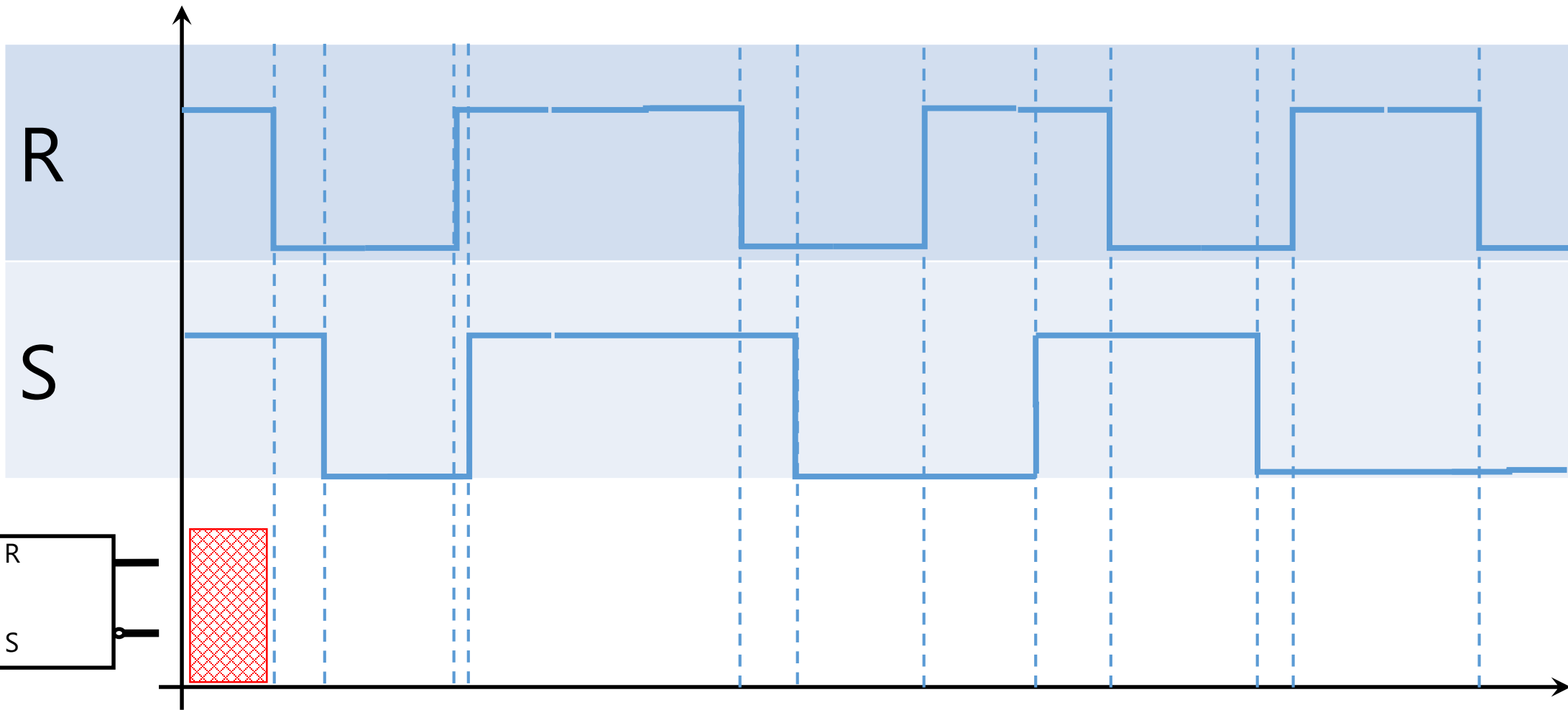


Time


Voltage

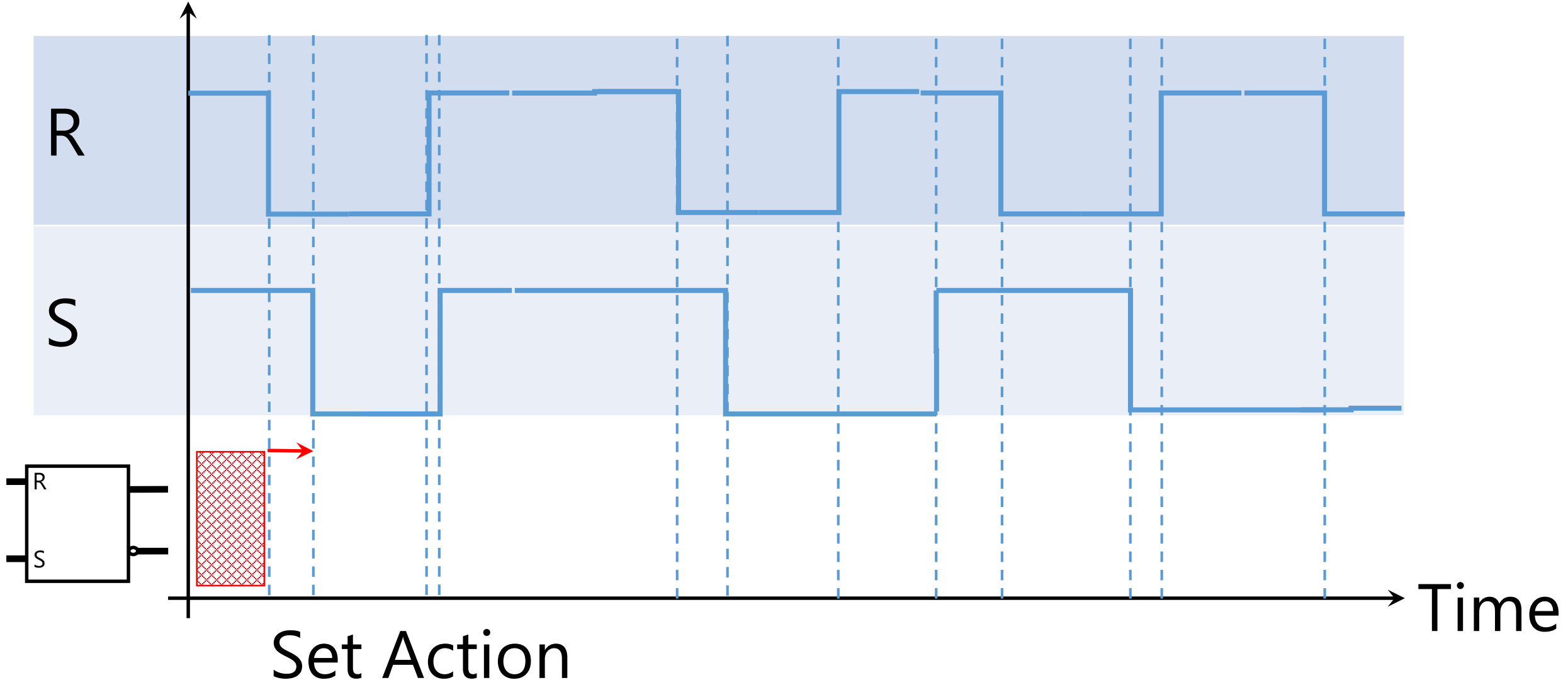




Voltage

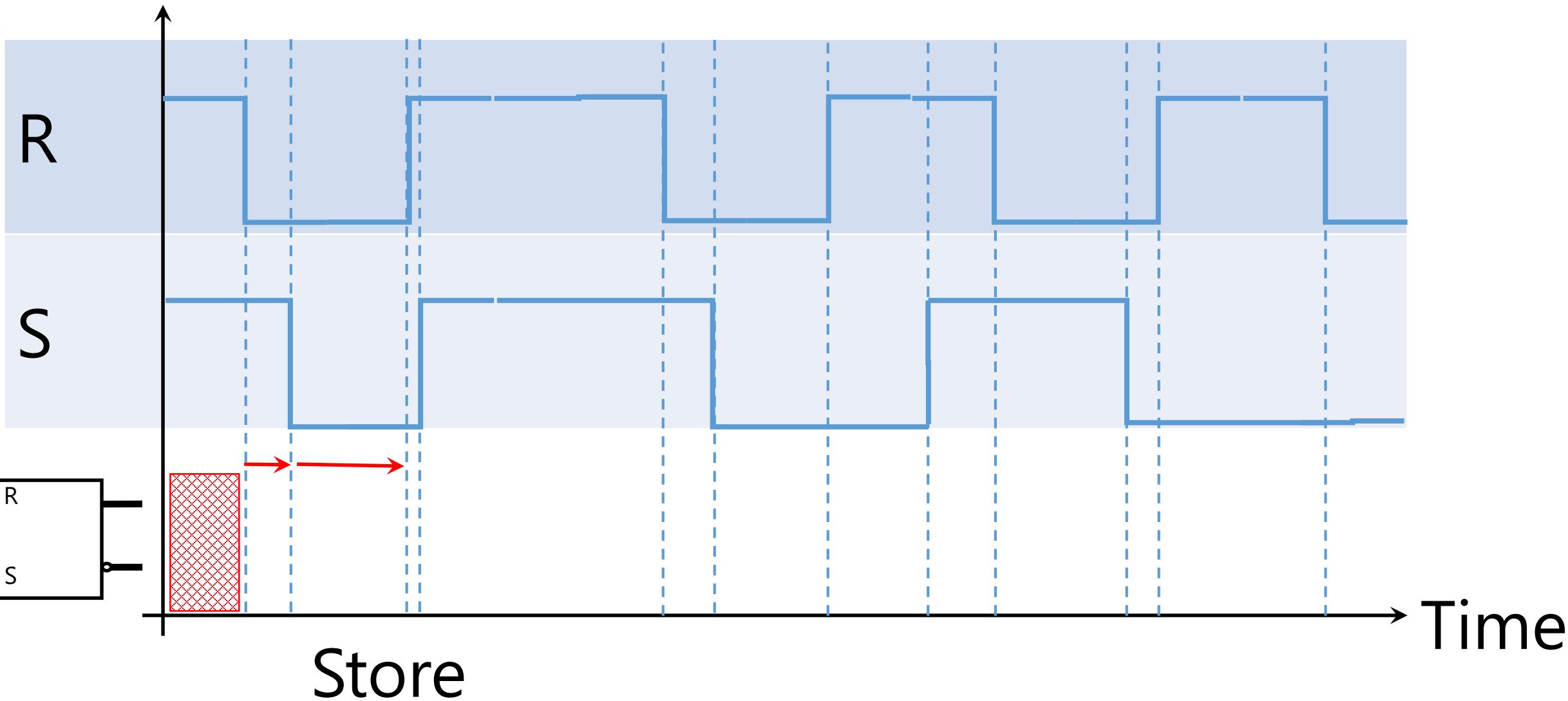

Voltage

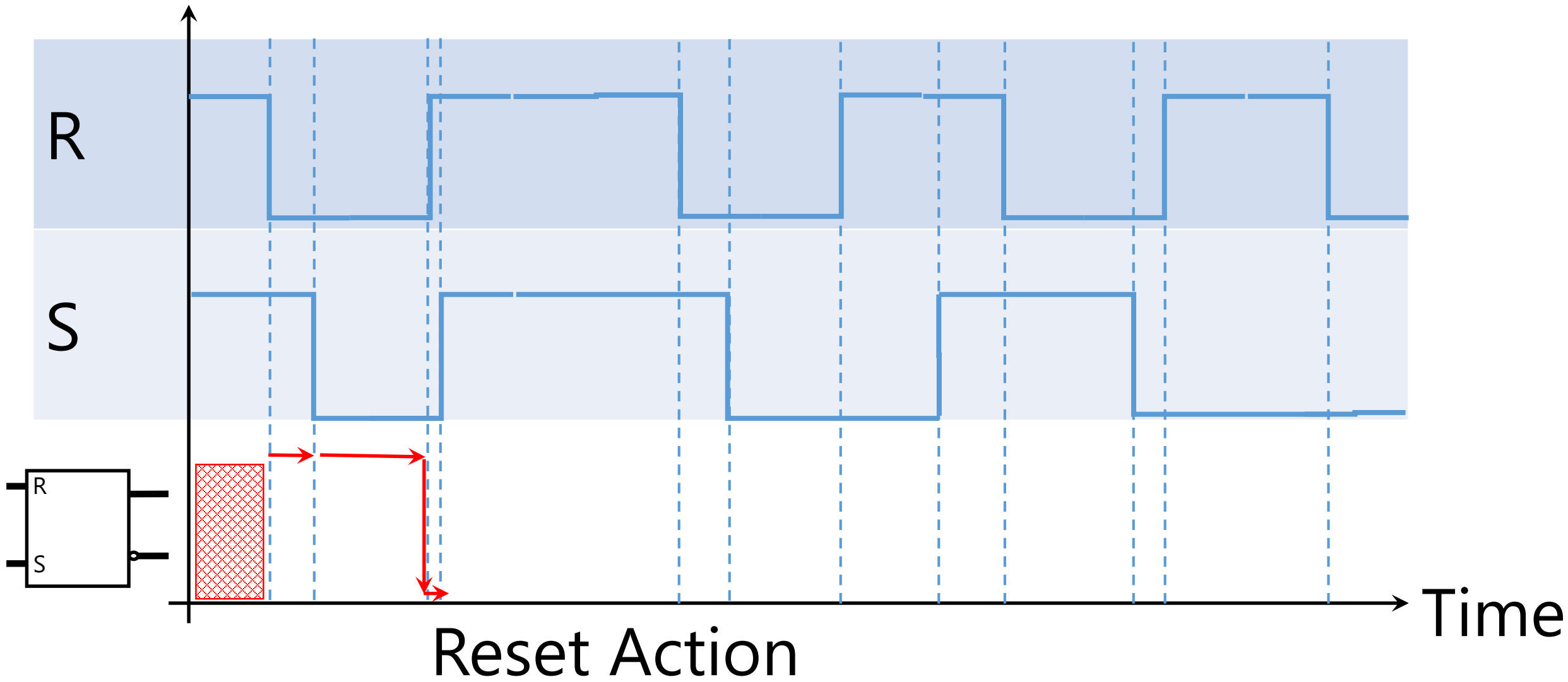


Voltage

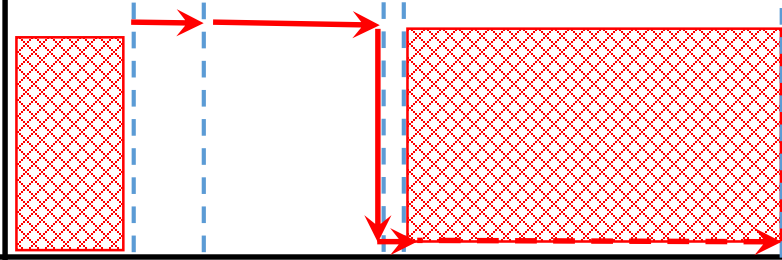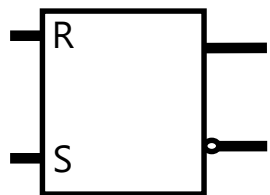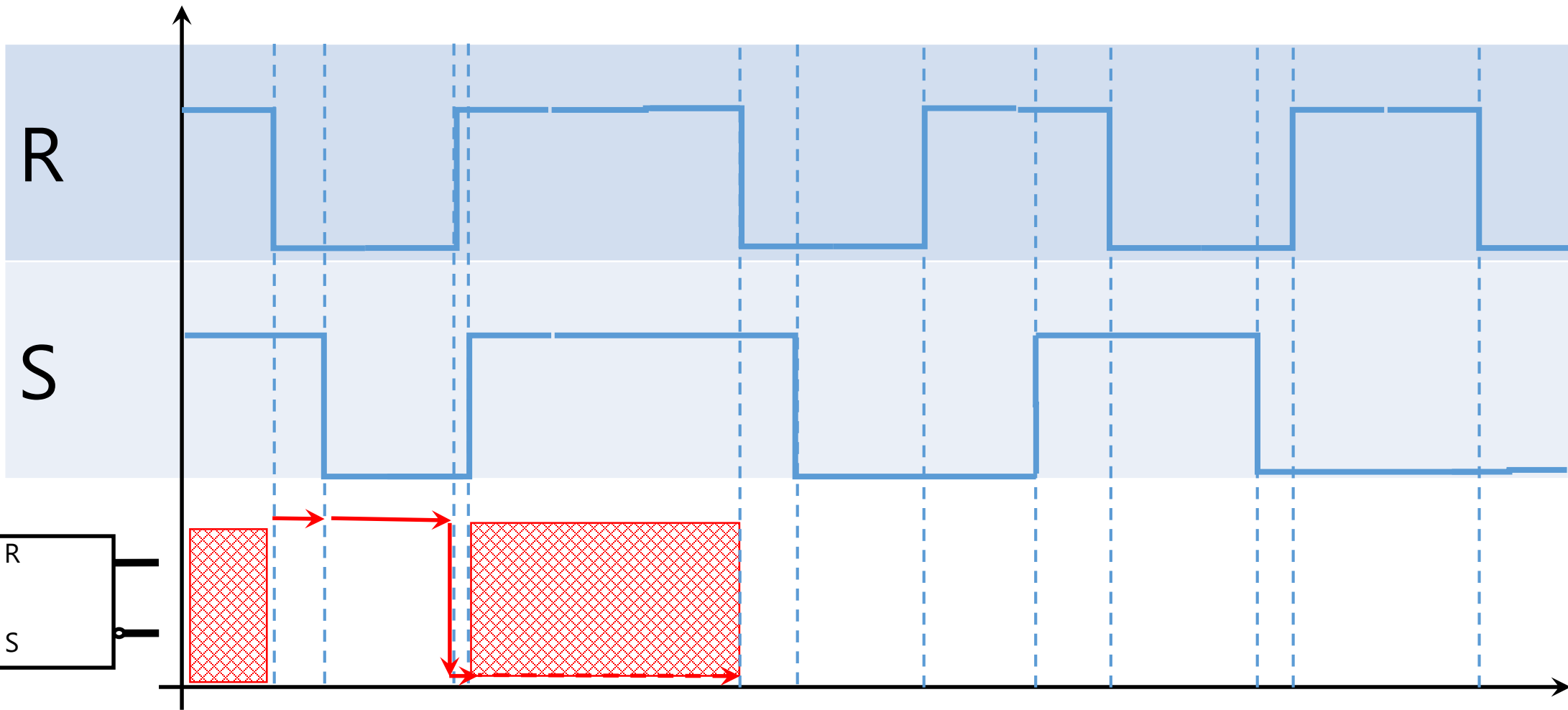

Forbidden

Time

Voltage

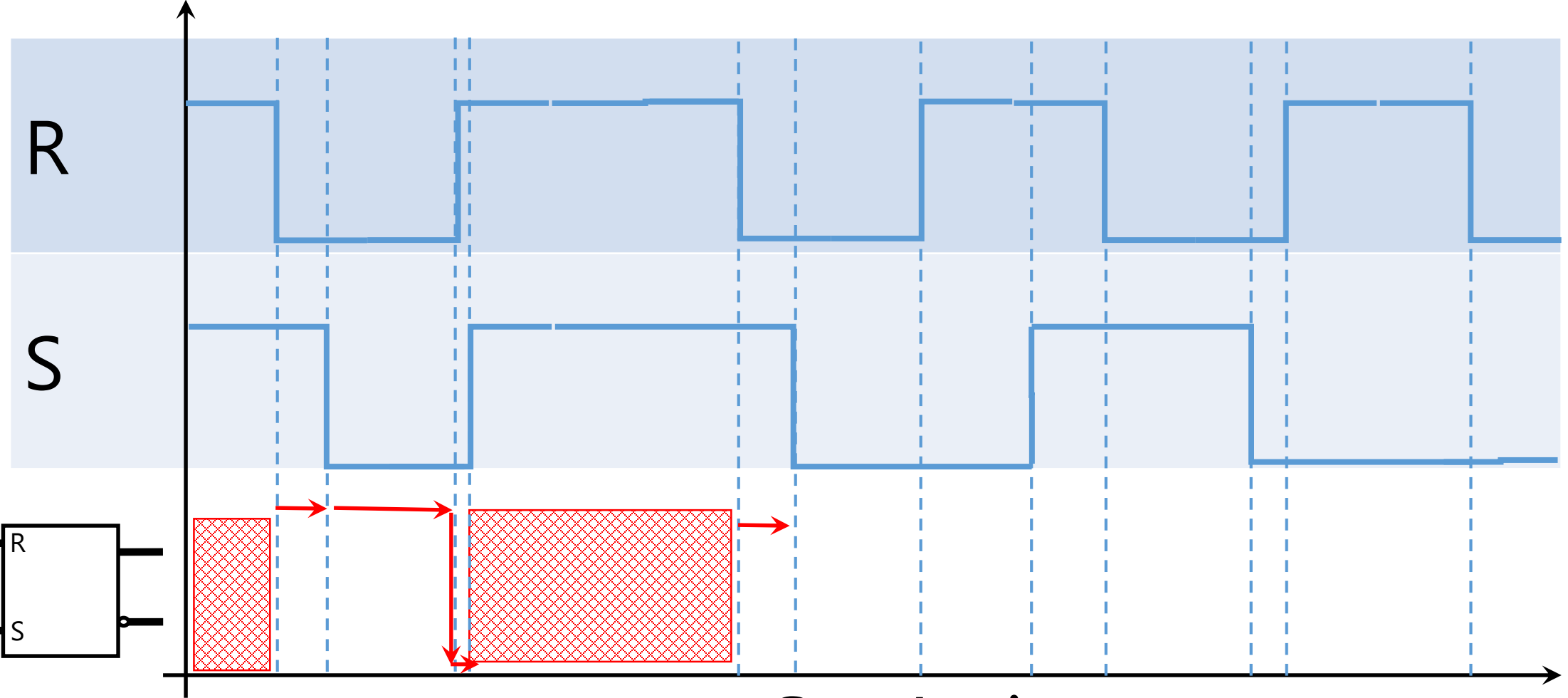


Set Action

Time

Voltage


R

S


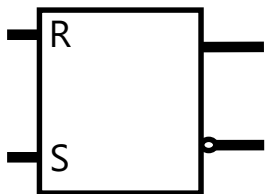


Store Action

Time

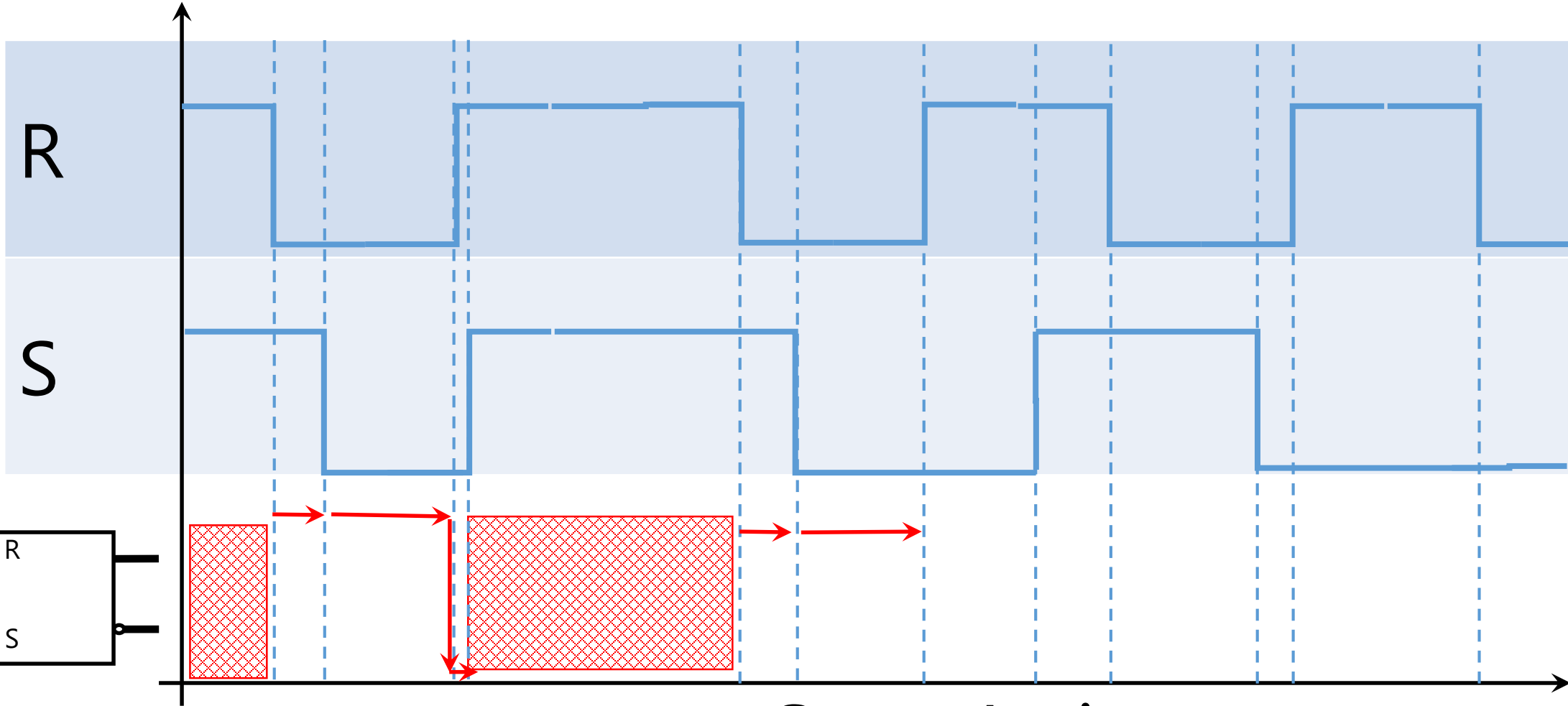



Voltage

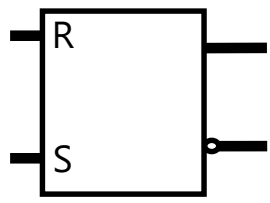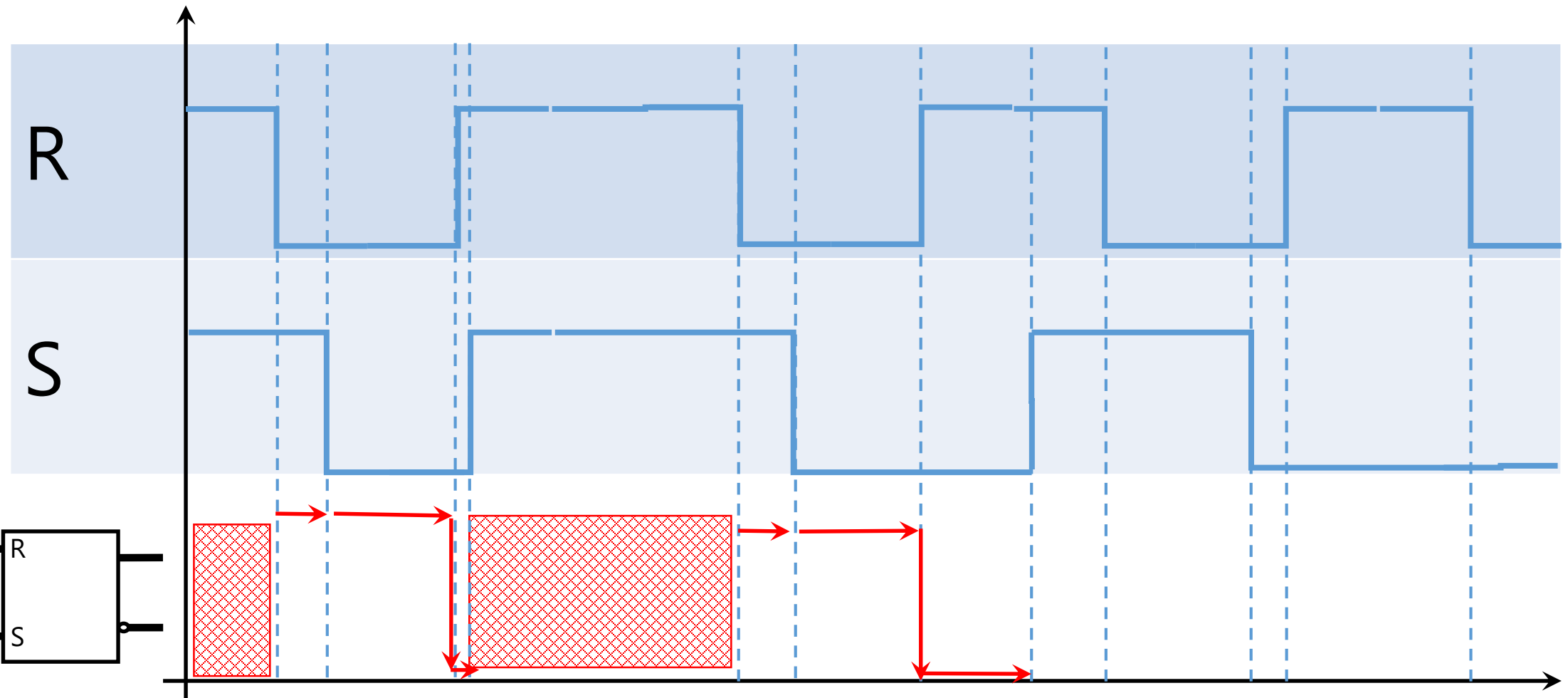

Reset Action

Time




Voltage

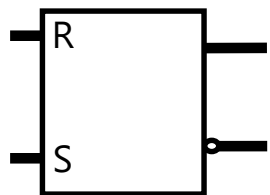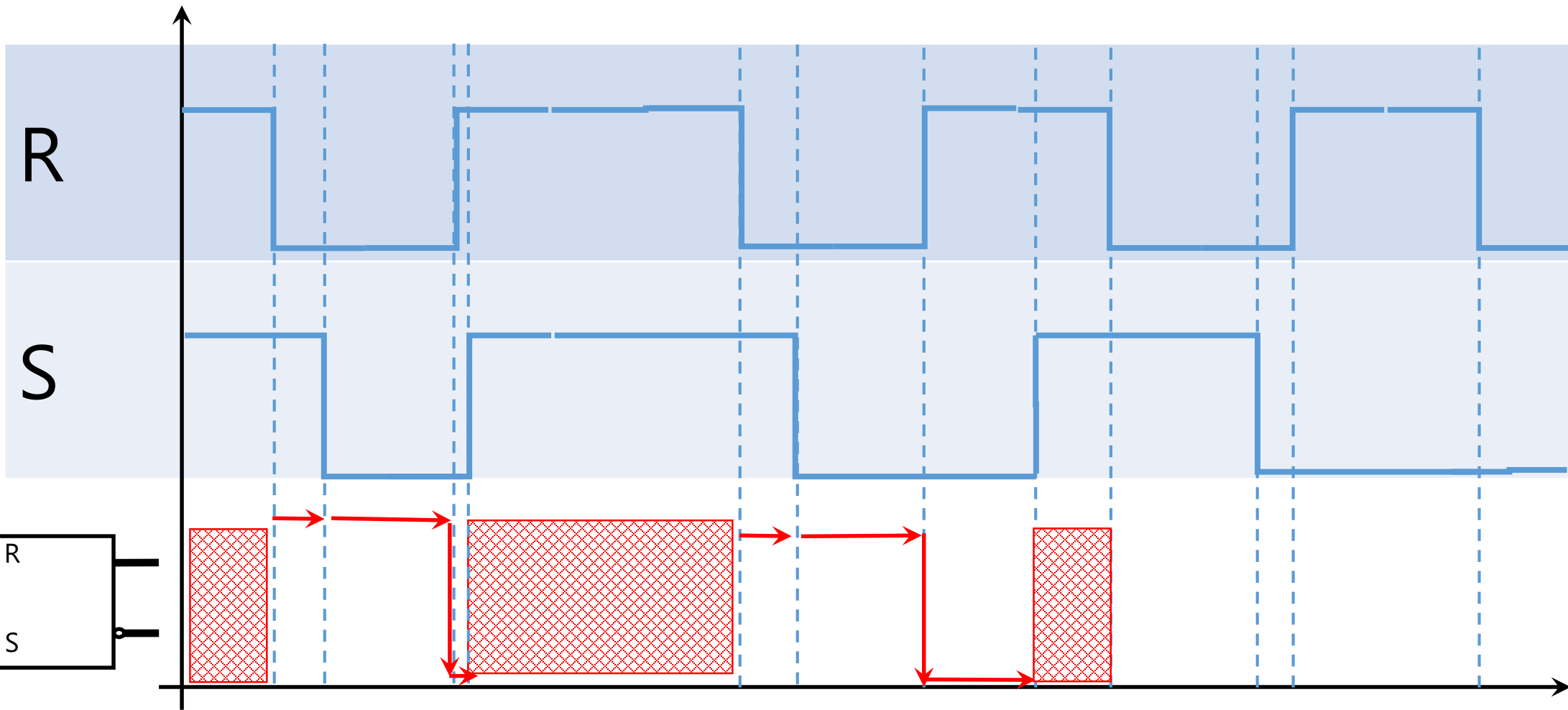

Forbidden




Time

Voltage

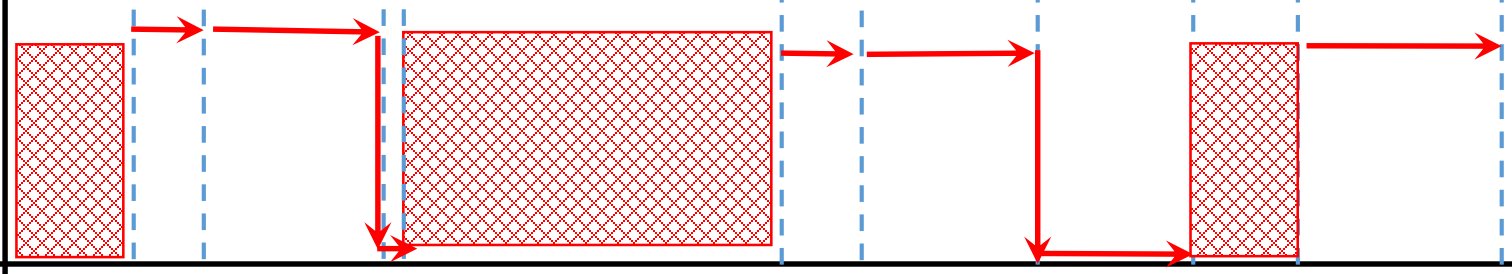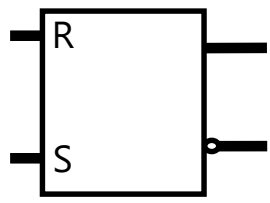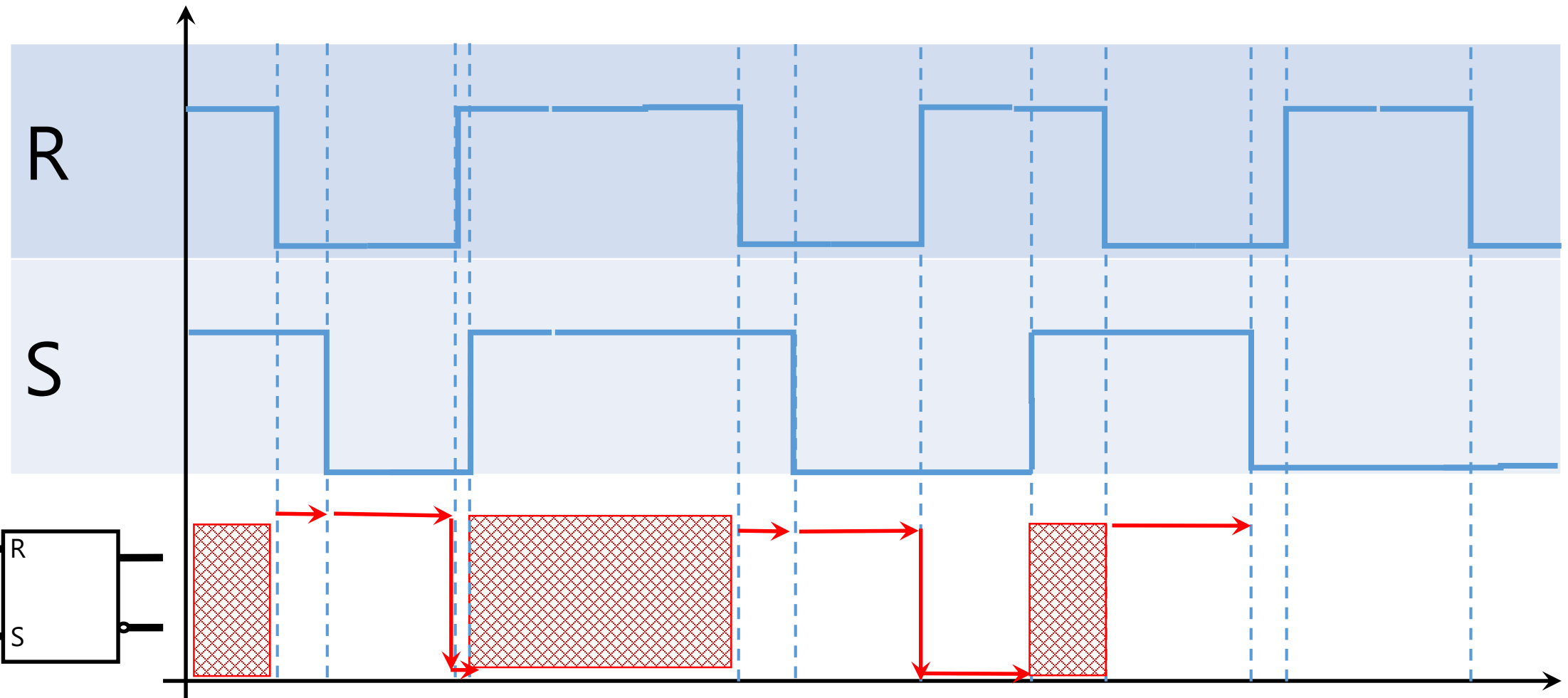

Set Action Time

Voltage

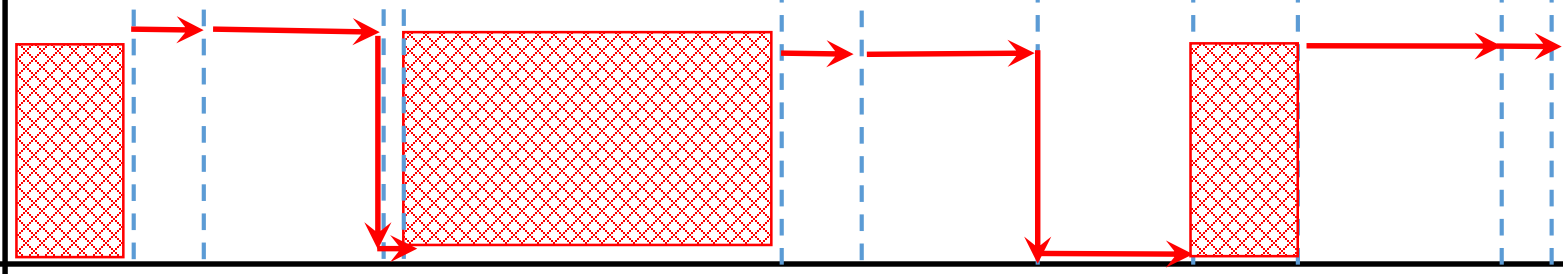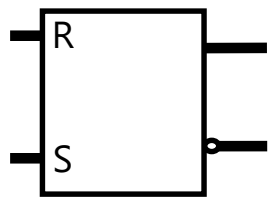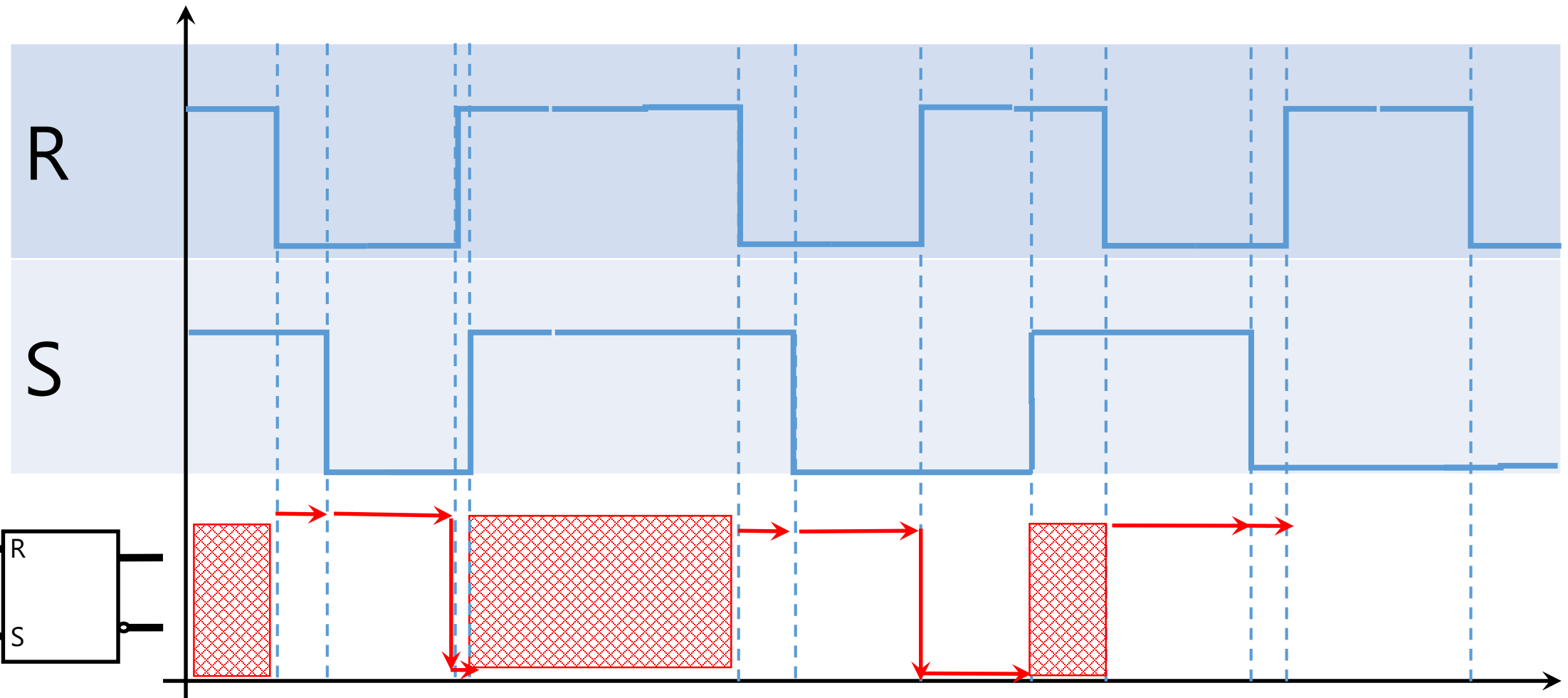


Time
Store Action

Voltage




R

S

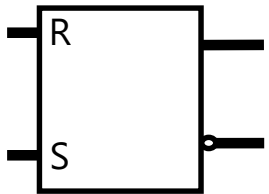

The diagram shows a horizontal timeline labeled "Time" with an arrow pointing to the right. A red double-headed arrow is positioned above the timeline, indicating a duration. Below the timeline, the text "Reset Action" is written.

Voltage

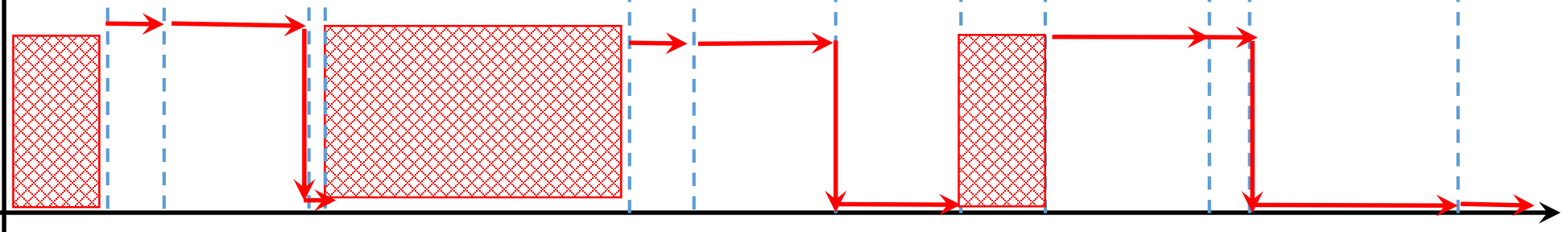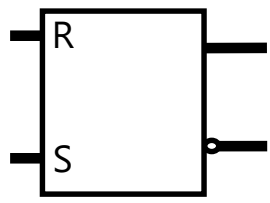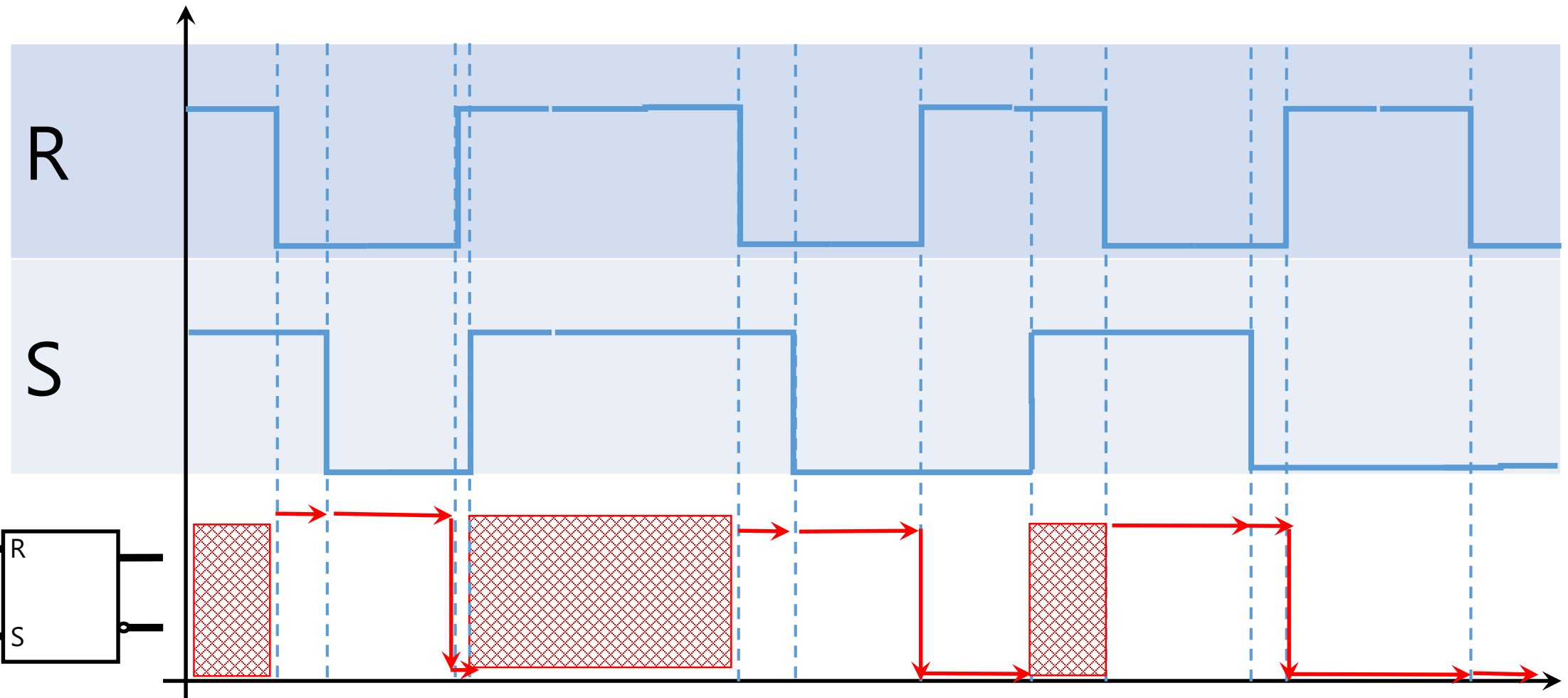

Time
Store Action