
MINIMIZATION

aka. Simplification

Claude Elwood Shannon

Mathematician
Electrical Engineer
Cryptographer

M.Sc. Thesis (1937)

A Symbolic Analysis of Relay and Switching Circuits

Switching Algebra!

2-valued Boolean algebra



SWITCHING ALGEBRA

- Given $S=\{0,1\}$
 - Given $\& = \times$ (AND), $+$ = $+$ (OR)
 - S is closed, commutative, and distributive w.r.t \times , $+$
 - $e_{\times} = 1$ and $e_{+} = 0$
 - Complement: for any $x \in S$, there is $y \in S$ such that
 - $0 \times 1 = e_{+} = 0$
 - $0 + 1 = e_{\times} = 1$
- We denote $0=1'$, $1=0'$
-

SWITCHING ALGEBRA IS-A BOOLEAN ALGEBRA

It satisfies all conditions of Boolean algebra!

Prove → Book: 2.3 axiomatic definition of Boolean algebra

Another sample of algebra in CS: Relational Algebra (SQL)

Is relational algebra a Boolean algebra? Check this when you take
COMP-3150: Database Management Systems!

BASIC THEOREMS

Prove by postulates

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x = 1 \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x = 1 \\ &= (X + X) (X + X') \text{ using complement property} \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x = 1 \\ &= (X + X) (X + X') \text{ using complement property} \\ &= X + (XX') \text{ using distributive property of } + \text{ over } \times \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x=1 \\ &= (X + X) (X+X') \text{ using complement property} \\ &= X + (XX') \text{ using distributive property of } + \text{ over } \times \\ &= X + 0 \text{ using complement property} \end{aligned}$$

$$X + X = X$$

$$X + X + X + \dots + X = X$$

$$\begin{aligned} X + X &= \\ &= (X + X) 1 \text{ using identity } e_x=1 \\ &= (X + X) (X+X') \text{ using complement property} \\ &= X + (XX') \text{ using distributive property of } + \text{ over } \times \\ &= X + 0 \text{ using complement property} \\ &= X \text{ using identity property of } e_+=0 \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \\ &= X + (1X') \text{ using distributive property of } + \text{ over } \times \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \\ &= X + (1X') \text{ using distributive property of } + \text{ over } \times \\ &= X + X' \text{ using identity } e_x = 1 \end{aligned}$$

$$X + 1 = 1$$

$$X + Y + Z + \dots + 1 = 1$$

$$\begin{aligned} X + 1 &= \\ &= (X + 1) 1 \text{ using identity } e_x = 1 \\ &= (X + 1) (X + X') \text{ using complement property} \\ &= X + (1X') \text{ using distributive property of } + \text{ over } \times \\ &= X + X' \text{ using identity } e_x = 1 \\ &= 1 \text{ using complement property} \end{aligned}$$

$$X + XY = X$$

$$X + XY + XZW + \dots + XWAD = X$$



Absorption

$$X + XY = X$$

$$X + XY + XZW + \dots + XWAD = X$$

$X + XY =$
= $X1 + XY$ using identity $e_x = 1$
= $X(1 + Y)$ using distributive property of \times over $+$
= $X1$ using previous theorem $x + 1 = 1$
= X using identity $e_x = 1$



Absorption

DUALITY

$\text{Dual}(F) = \text{OR} \Leftrightarrow \text{AND}, 1 \Leftrightarrow 0$

Dual(F) may or may not equal to F!

DUALITY

$$X+1 \rightleftharpoons X0$$

$$X+X' \rightleftharpoons XX'$$

$$(X+Y)' \rightleftharpoons (XY)'$$

DUALITY

A postulate or a proved theorem for F
Also a postulate or a proved theorem for $\text{Dual}(F)$

DUALITY

$$\{X+1=1\} \Leftrightarrow \{X0 = 0\}$$

$$\{X+X'=1\} \Leftrightarrow \{XX'=0\}$$

$$\{(X+Y)'=X'Y'\} \Leftrightarrow \{(XY)'=X'+Y'\}$$

$$X(X + Y) = X$$

$$X(X + Y)(X + Z) \dots (X + W) = X$$

$\{X(X + Y) = X\} \rightleftharpoons \{X + XY = X\}$
 \rightleftharpoons We proved the dual version
 \rightleftharpoons Using the duality property, this is also true!



Absorption

BASIC THEOREMS

prove by truth table

For equality proof, $F_1 = F_2$, for all possibility in the input variables (all rows), both side of equation must have equal value for same input variables.

For inequality proof, $F_1 \neq F_2$, find at least one possibility (a row) that have different values.

MINIMIZATION

- I) Boolean Algebra (algebraically)
aka. Algebraic Manipulation
-

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

4 × 3-input-AND

1 × 4-input-OR

$$F \equiv ZY'X' + ZYX + ZYX' + ZY'X$$

$$F = \Sigma (Y'X' + YX + YX' + Y'X)$$

$$F = Z(Y'X' + YX + YX' + Y'X)$$

$$F = Z(Y'(X' + X) + YX + YX')$$

$$F = Z(Y'(X' + X) + YX + YX')$$

$$F \equiv Z(Y'1 + YX + YX')$$

$$F \equiv Z(Y'1 + YX + YX')$$

$$F \equiv Z(Y' + YX + YX')$$

$$F \equiv Z(Y' + YX + YX')$$

$$F \equiv Z(Y' + Y(X + X'))$$

$$F \equiv Z(Y' + Y(X + X'))$$

$$F = Z(Y' + Y1)$$

$$F = Z(Y' + Y)$$

$$F = Z(Y' + Y)$$

$$F = Z1$$

$$F = Z$$

0 gates!

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

4 × 3-input-AND
1 × 4-input-OR

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

$$F = ZY'(X' + X) + ZYX + ZYX'$$

$$F \equiv ZY' (X' + X) + ZYX + ZYX'$$

$$F \equiv ZY' (X' + X) + ZY (X + X')$$

$$F \equiv ZY' (X' + X) + ZY (X + X')$$

$$F = ZY'1 + ZY1$$

$$F \equiv ZY' + ZY$$

$$F = Z(Y' + Y)$$

$$F = Z1$$

$$F = Z$$

0 gates!

$$F = ZY'X' + ZYX + ZYX' + ZY'X$$

4 × 3-input-AND
1 × 4-input-OR

$$F = ZY'X' + ZYX' + Z'Y'X$$

3 × 3-input-AND

1 × 3-input-OR

$$F = ZY'X' + ZYX' + Z'Y'X$$

$$F = ZX'(Y' + Y) + Z'Y'X$$

$$F = ZX' (Y' + Y) + Z'Y'X$$

$$F = ZX'1 + Z'Y'X$$

$$F = ZX' + Z'Y'X$$

1 × 2-input-AND

1 × 3-input-AND

1 × 2-input-OR

$$F = ZYX' + ZYX' + Z'Y'X$$

3 × 3-input-AND
1 × 3-input-OR

MINIMIZATION

I) Boolean Algebra (algebraically)

- Needs to be smart. It is hard due to guesswork (which rules to apply?)
- If the number of variables (ABCDEF...) and/or number of minterms (MAXTERMS) grows
- No Algorithm
- Is the result minimal?!

MINIMIZATION

II) Map (Karnaugh map, K-map)
aka. Graphical Manipulation

MINIMIZATION

II) Map (Karnaugh map, K-map) aka. Graphical Manipulation

Algorithm; Straightforward, up to six variables

Result is always minimal

TRUTH TABLE

Y	X	F
0	0	?
0	1	?
1	0	?
1	1	?


BOOLEAN FUNCTION

Algebraic Expression

$$F_{\text{SOP}}(Y,X) = \sum \text{minterms}$$

$$F_{\text{POS}}(Y,X) = \prod \text{MAXTERMS}$$

LOGIC CIRCUIT

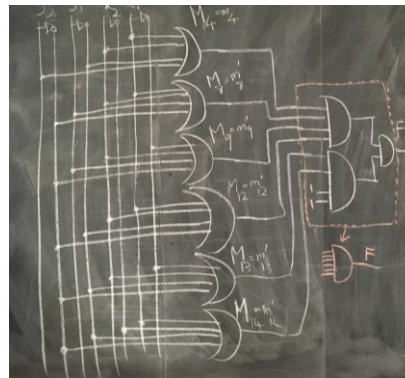


Maurice Karnaugh

Physicist
Mathematician
Inventor

Bell Labs (1954)

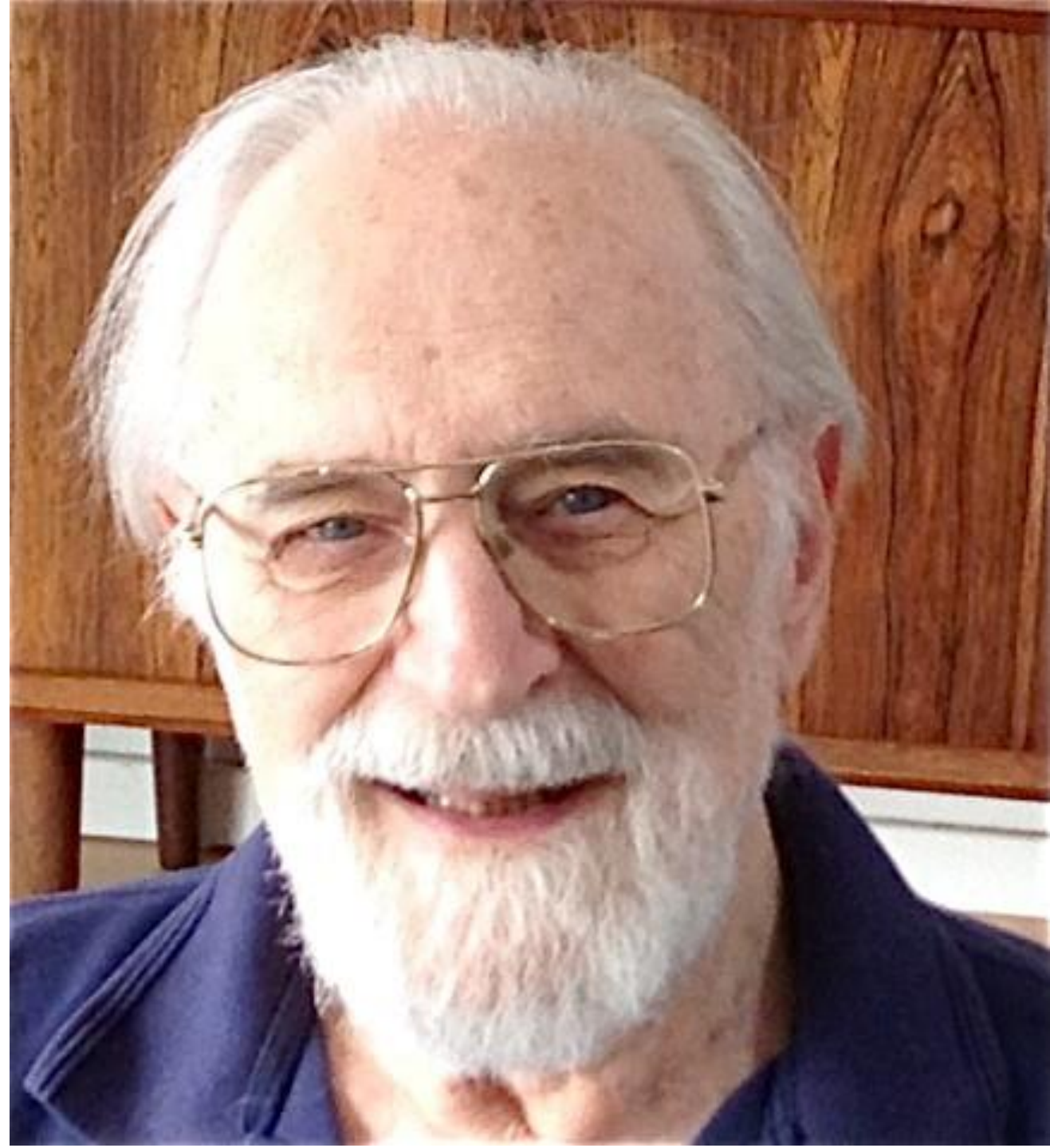"The Map Method for Synthesis of
Combinational Logic Circuits"



KARNAUGH MAP

/'kɑ:rnɔ:/

1-Variable KARNAUGH MAP

X	F
0	m_0
1	m_1


X	
0	1
m_0	m_1

2-Variable KARNAUGH MAP

Y	X	F
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

		X	
		0	1
Y	0	m_0	m_1
	1	m_2	m_3

Y	X	F
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

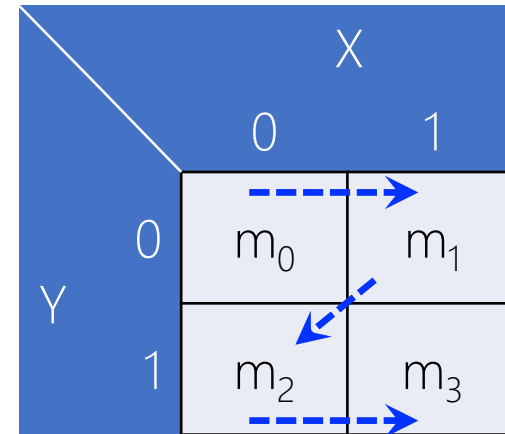

Y	X	F
0	0	1
0	1	0
1	0	0
1	1	0

$$F(Y,X) = m_0 = Y'X'$$

		X	
		0	1
Y	0	1	0
	1	0	0

$$F(Y,X) = Y'X'$$

Y	X	F
0	0	0
0	1	1
1	0	0
1	1	0

$$F(Y,X) = m_1 = Y'X$$

		X	
		0	1
Y	0	0	1
	1	0	0

$$F(Y,X) = Y'X$$

Y	X	F
0	0	0
0	1	0
1	0	1
1	1	0

$$F(Y,X) = m_2 = YX'$$

		X	
		0	1
Y	0	0	0
	1	1	0

$$F(Y,X) = YX'$$

Y	X	F
0	0	0
0	1	0
1	0	0
1	1	1

$$F(Y,X) = m_3 = YX$$

		X	
		0	1
Y	0	0	0
	1	0	1

$$F(Y,X) = YX$$

Y	X	F
0	0	1
0	1	1
1	0	0
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 \\
 &= Y'X' + Y'X \\
 &= Y'(X' + X) \\
 &= Y'
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	0	0

$$F(Y,X) = Y'$$

Y	X	F
0	0	0
0	1	0
1	0	1
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_2 + m_3 \\
 &= YX' + YX \\
 &= Y(X' + X) \\
 &= Y
 \end{aligned}$$

		X	
		0	1
Y	0	0	0
	1	1	1

$$F(Y,X) = Y$$

Y	X	F
0	0	0
0	1	1
1	0	0
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_1 + m_3 \\
 &= Y'X + YX \\
 &= X(Y' + Y) \\
 &= X
 \end{aligned}$$

		X	
		0	1
Y	0	0	1
	1	0	1

$$F(Y,X) = X$$

Y	X	F
0	0	1
0	1	0
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_2 \\
 &= Y'X' + YX' \\
 &= X'(Y' + Y) \\
 &= X'
 \end{aligned}$$

		X	
		0	1
Y	0	1	0
	1	1	0

$$F(Y,X) = X'$$

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 \\
 &= Y'X' + Y'X + YX' \\
 &= Y'(X' + X) + YX' \\
 &= Y' + YX'
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	0

$$F(Y,X) = Y' + YX'$$

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 \\
 &= Y'X' + Y'X + YX' \\
 &= X'(Y' + Y) + Y'X \\
 &= X' + Y'X
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	0

$$F(Y,X) = X' + Y'X$$

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 \\
 &= Y'X' + Y'X + YX' \\
 &= Y'X' + Y'X' + Y'X + YX' \\
 &= Y'(X' + X) + Y'X' + YX' \\
 &= Y' + Y'X' + YX' \\
 &= Y' + X'(Y' + Y) \\
 &= Y' + X'
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	0

$$F(Y,X) = Y' + X'$$

Y	X	F
0	0	1
0	1	1
1	0	1
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 + m_3 \\
 &= Y'X' + Y'X + YX' + YX \\
 &= Y'(X' + X) + Y(X' + X) \\
 &= Y' + Y \\
 &= 1
 \end{aligned}$$

		X	
		0	1
Y	0	1	1
	1	1	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_1 + m_2 + m_3 \\
 &= 1
 \end{aligned}$$

Y	X	F
0	0	0
0	1	1
1	0	1
1	1	0

$$\begin{aligned}
 F(Y,X) &= m_1 + m_2 \\
 &= Y'X + YX'
 \end{aligned}$$

		X	
		0	1
Y	0	0	1
	1	1	0

$$\begin{aligned}
 F(Y,X) &= m_1 + m_2 \\
 &= Y'X + YX'
 \end{aligned}$$

Y	X	F
0	0	1
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_2 \\
 &= Y'X' + YX
 \end{aligned}$$

		X	
		0	1
Y	0	1	0
	1	0	1

$$\begin{aligned}
 F(Y,X) &= m_0 + m_2 \\
 &= Y'X' + YX
 \end{aligned}$$

3-Variable KARNAUGH MAP

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7



		X	
		0	1
Y	0	m_0	m_1
	1	m_2	m_3

		X	
		0	1
Y	0	m_0	m_1
	1	m_2	m_3




		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

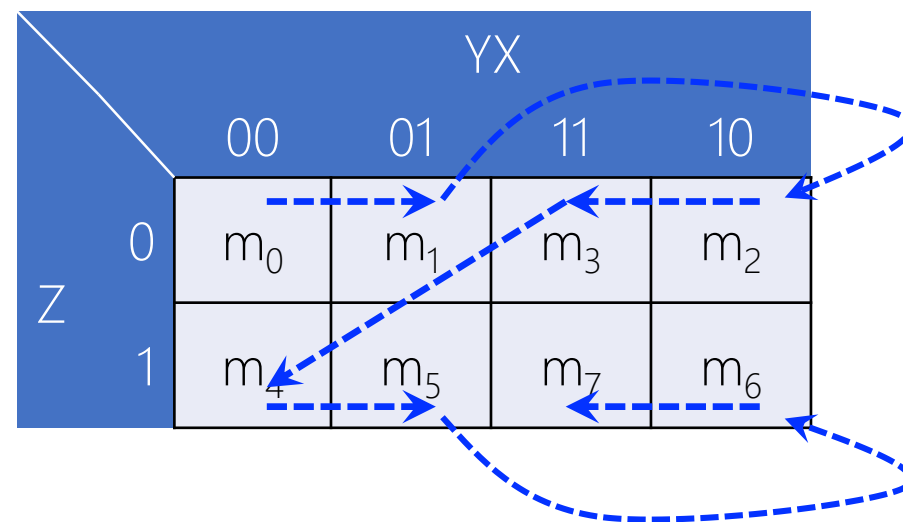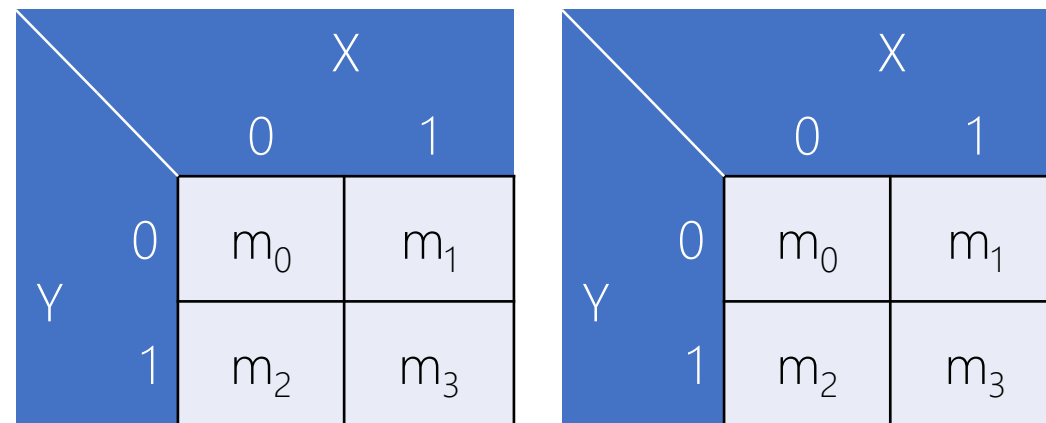

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7


		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6

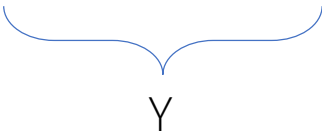

Y

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7


		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6



 Y'

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6



X

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6


X' ?

Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

		YX			
		00	01	11	10
Z	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6



Z	Y	X	F
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

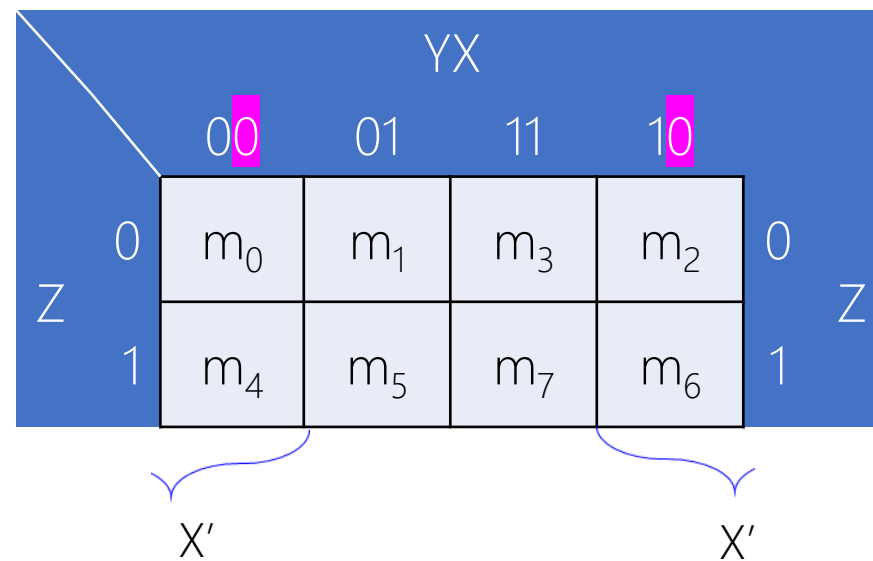

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' +
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' + ZY
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' + Y
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= (Z' + Y + X) (Z' + Y + X') \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= ?
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= (Z' + Y + X) (Z' + Y + X') \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	0	0	0	0
	1	1	1	0	0

$$\begin{aligned}
 F'(Y,X) &= \sum m(4,5) \\
 &= ZY'
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= (Z' + Y + X) (Z' + Y + X') \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= (F')' \\
 &= (ZY')' \\
 &= Z' + Y
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z'Y'X' + Z'Y'X + Z'YX' + Z'YX + ZYX' + ZYX \\
 &= ?
 \end{aligned}$$

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= (Z' + Y + X) (Z' + Y + X') \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,1,2,3,6,7) \\
 &= Z' + Y
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	1	1	1
	1	0	0	1	1

$$\begin{aligned}
 F(Y,X) &= \prod M(4,5) \\
 &= (F')' \\
 &= (ZY')' \\
 &= Z' + Y
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		YX			
		00	01	11	10
Z	0	1	0	0	1
	1	1	0	0	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,2,4, 6) \\
 &= Z'Y'X' + Z'YX' + ZY'X' + ZYX' \\
 &= ?
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$\begin{aligned}
 F(Y,X) &= \sum m(0,2,4, 6) \\
 &= Z'Y'X' + Z'YX' + ZY'X' + ZYX' \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	0	0	1
	1	1	0	0	1

$$\begin{aligned}
 F(Y,X) &= \sum m(0,2,4, 6) \\
 &= X'
 \end{aligned}$$

Z	Y	X	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

$$\begin{aligned}
 F(Y,X) &= \prod M(1,3,5,7) \\
 &= (Z+Y+X')(Z+Y'+X')(Z'+Y+X')(Z'+Y'+X') \\
 &= ?
 \end{aligned}$$

		YX			
		00	01	11	10
Z	0	1	0	0	1
	1	1	0	0	1

$$\begin{aligned}
 F(Y,X) &= \prod M(1,3,5,7) \\
 &= (X)' \\
 &= X'
 \end{aligned}$$

4-Variable KARNAUGH MAP
